



SEM I

Program: Computer Engineering

SAP ID: 60004200132

Basic Electrical and Electronics Engineering

Expt. No.	Title of the Experiment	Date of Expt.	Date of Submission	CO	Signature
1	DC circuit analysis	06/03/21	13/03/21	1	
2	Mesh and nodal analysis	13/03/21	20/03/21	1	
3	Superposition theorem	20/03/21	26/03/21	2	
4	Thevenin's and Norton's theorem	27/03/21	02/04/21	2	
5	R-L and R-C circuit analysis	03/04/21	09/04/21	3	
6	Rectifier circuits	10/04/21	16/04/21	5	
7	Clipper and Clampers	17/04/21	23/04/21	5	

a



First Year (Semester I) B.Tech.

Basic Electrical and Electronics Engineering

Experiment No. : 01
DC Circuit Analysis

Name : Ayush Jain

SAP No. : 60004200132

Date of performance : 6/3/2021

Signature of teacher-in-charge : _____



Aim:	To determine resistor, voltage and current value in a circuit.
Apparatus :	Online simulation tools (Tinkercad)
Theoretical Analysis:	<p>X —————— 2 ohm —————— 4 ohm —————— 2 ohm —————— Y</p> <p> </p> <p> 6 ohm</p> <p> </p> <p> 6 ohms</p> <p> </p> <p> 7 ohm</p> <p>read</p> <p>Fig. 1(a) Resistor equivalent across X and Y</p> <p>Theoretical Calculations:</p> <p>Resistor equivalent across X and Y</p> <p>Converting Delta comprising of 4Ω, 6Ω and 2Ω into an equivalent star.</p> <p>\Rightarrow $\frac{2\Omega}{12} = 0.67\Omega$</p> <p>$\Rightarrow$ $\frac{12}{12} = 1\Omega$</p> <p>\Rightarrow $\frac{24}{12} = 2\Omega$</p> <p>$\therefore R_{xy} = 8.67\Omega$</p>



First Year (Semester I) B.Tech.

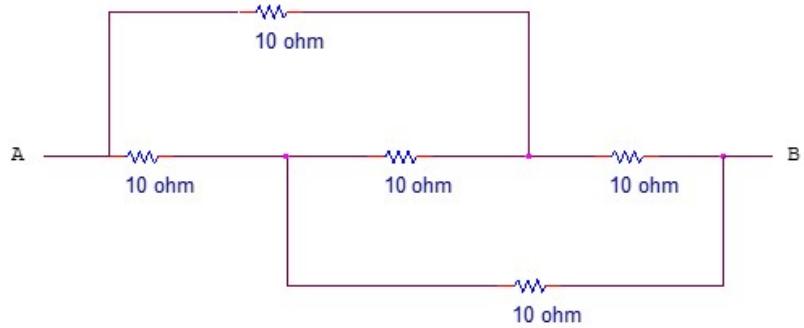
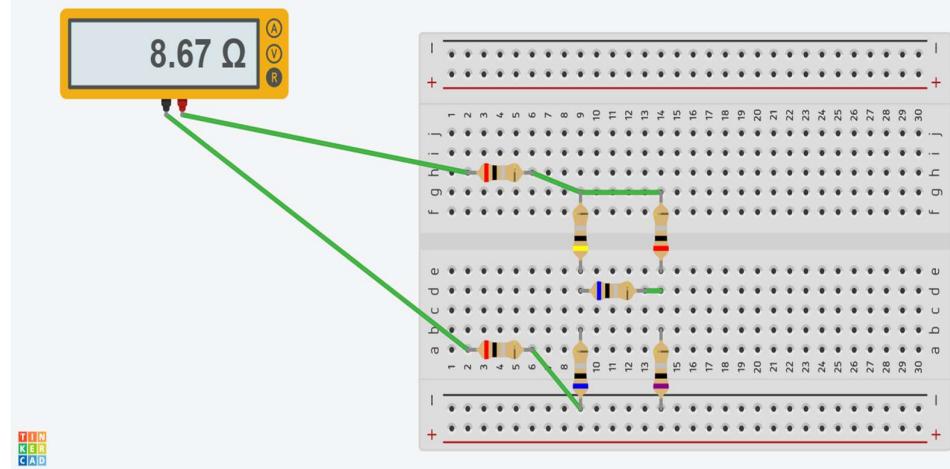


Fig. 1(b) Resistor equivalent across A and B

Theoretical Calculations:

Resistor equivalent across A and B

Converting delta comprising of 10, 10 and 10Ω into star,

$$\Rightarrow \frac{100}{30} \text{ and } \frac{100}{30} \text{ in series}$$
$$\Rightarrow \frac{400}{30} \text{ and } \frac{100}{30} \text{ in series}$$
$$\Rightarrow R_{AB} = \frac{100}{30} + \frac{200}{30} = \frac{300}{30} = 10 \Omega$$



First Year (Semester I) B.Tech.

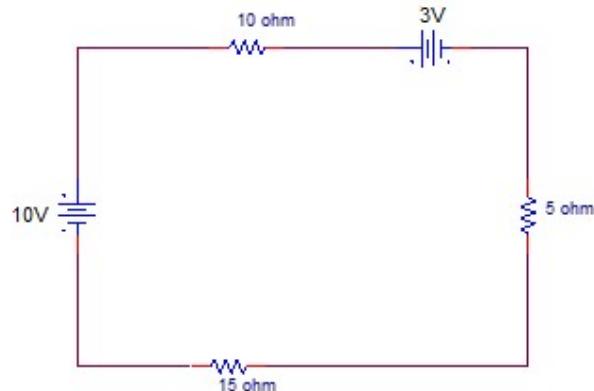
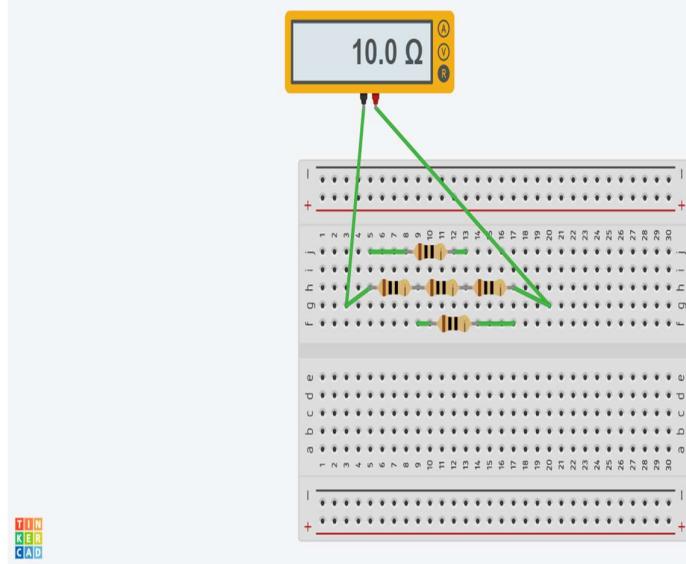


Fig. 1(c) Current in the circuit

Theoretical Calculations:



Current in the circuit

Applying KVL in loop,

$$10 - 10I - 3 - 5I - 15I = 0$$
$$-30I + 7 = 0$$
$$\therefore \frac{7}{30} = 0.233A$$



First Year (Semester I) B.Tech.

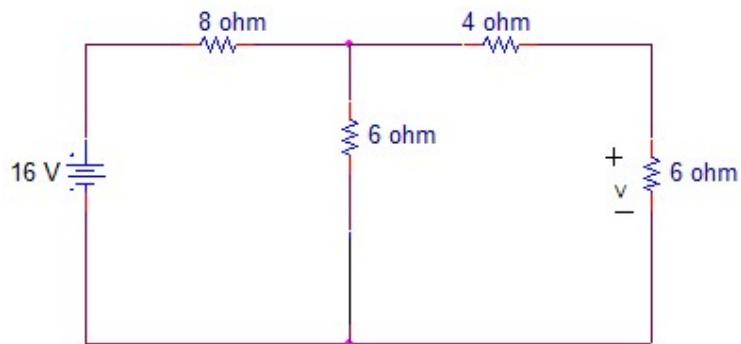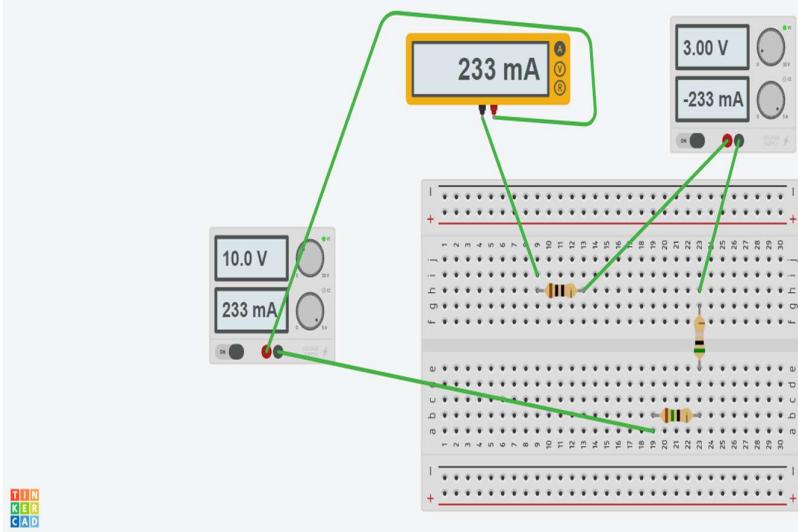

Theoretical Calculations:

Voltage across 6ohm

Handwritten notes for the theoretical calculations:

Applying KVL in mesh 1,

$$16 - 14I_1 + 6I_2 = 0 \quad \dots \quad (1)$$


Now,

Applying KVL in mesh 2,

$$-16I_2 + 6I_1 = 0 \quad \dots \quad (2)$$
$$\therefore I_1 = 1.36 \text{ A}, I_2 = 0.51 \text{ A}$$
$$\therefore V_{6\Omega} = I_2 R = 0.51 \times 6 = 3.06 \text{ V}$$



First Year (Semester I) B.Tech.

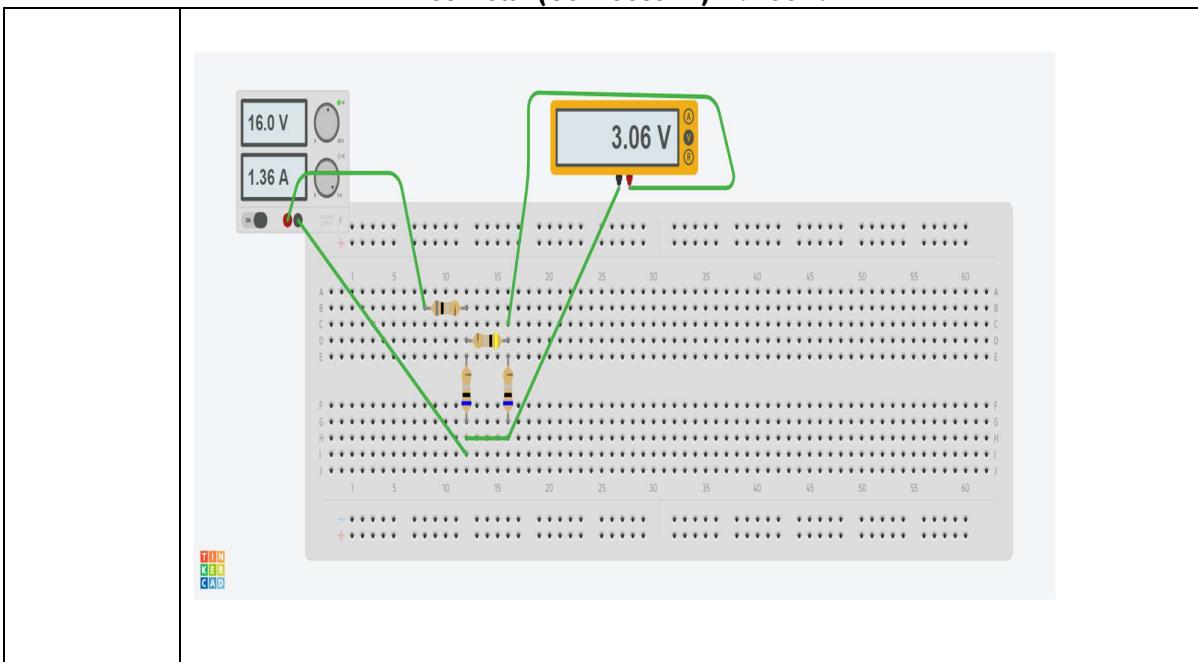

		Theoretical values	Practical values
Observation Table	Equivalent resistor R_{XY} (Fig 1.a)	8.67 Ω	8.67 Ω
	Equivalent resistor R_{AB} (Fig 1.b)	10 Ω	10 Ω
	Current in the circuit I (Fig 1.c)	0.233A	0.233A
	Voltage $V_{6Ω}$ (Fig 1.d)	3.06V	3.06V

Conclusion:

1. We used Star-Delta transformation to simplify the circuit.
2. The practical values has been attained using an online simulator tool, Tinkercad
3. The theoretical values and practical values are equal to each other.



First Year (Semester I) B.Tech.

Basic Electrical and Electronics Engineering

Experiment No. : 02
Mesh and Nodal Analysis

Name : Ayush Jain

SAP No. : 600004200132

Date of performance : 13-03-2021

Signature of teacher-in-charge : _____



First Year (Semester I) B.Tech.

Aim:	To determine mesh currents and nodal voltages in the given circuit.
Apparatus :	Online simulation tools (Suggested Tinkercad)
Theoretical Analysis:	<p>Fig. 1(a) Mesh Analysis</p> <p>The circuit diagram shows a rectangular loop with a vertical center node. A 20V DC voltage source is connected across the left vertical branch. A 40 ohm resistor is in the top horizontal branch. A 20 ohm resistor is in the central vertical branch. A 60 ohm resistor is in the right horizontal branch. A 6V DC voltage source is connected across the right vertical branch. Two clockwise loops are defined: loop i_1 encloses the 20V source and the 40 ohm resistor; loop i_2 encloses the 6V source and the 60 ohm resistor.</p> <p>Theoretical Calculations:</p> <p>Handwritten notes show the circuit setup with resistors labeled 40 ohm, 60 ohm, and 20 ohm. Loop currents I_1 and I_2 are indicated for the two loops. Below the circuit, handwritten equations are provided:</p> <p>For loop 1,</p> $20 - 60I_1 + 20I_2 = 0 \quad (1)$ $-60I_1 + 20I_2 = -20 \quad (1)$ <p>For loop 2,</p> $-80I_2 + 20I_1 - 6 = 0 \quad (2)$ $20I_1 - 80I_2 = 6 \quad (2)$ <p>Solving these equations, we find:</p> $I_1 = 336 \text{ mA}$ $I_2 = 9.09 \text{ mA}$



First Year (Semester I) B.Tech.

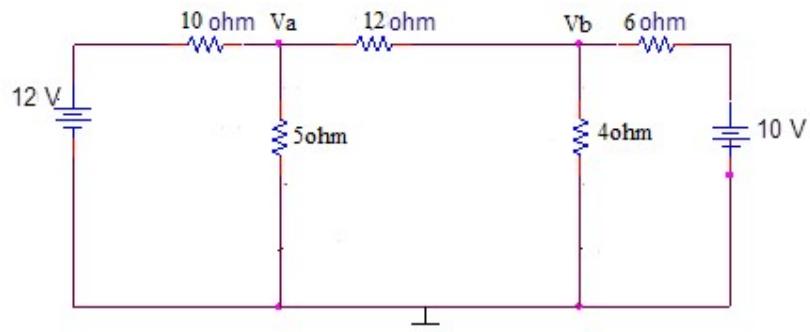
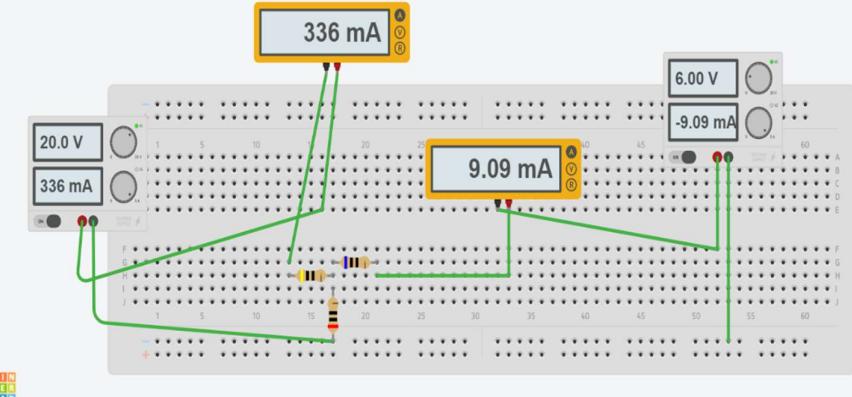


Fig. 1(b) Nodal Analysis

Theoretical Calculations:

Handwritten circuit diagram showing the same network as the diagram above, with nodes V_A and V_B labeled. Below it, handwritten equations for KCL and KVL are shown:

KCL at A,
 $\frac{12}{10} + \frac{V_A}{5} + \frac{V_A - V_B}{12} = 0$

$6V_A - 72 + 12V_A + 5V_A - 5V_B = 0$
 $23V_A - 5V_B = 72 \quad \text{--- (1)}$

KCL at B,
 $\frac{V_B - V_A}{12} + \frac{V_B}{4} + \frac{V_B - 10}{6} = 0$

$2V_B - 2V_A + 3V_B + 2V_B - 20 = 0$
 $-2V_A + 7V_B = 20 \quad \text{--- (2)}$

$V_A = V_B = 4V$



First Year (Semester I) B.Tech.

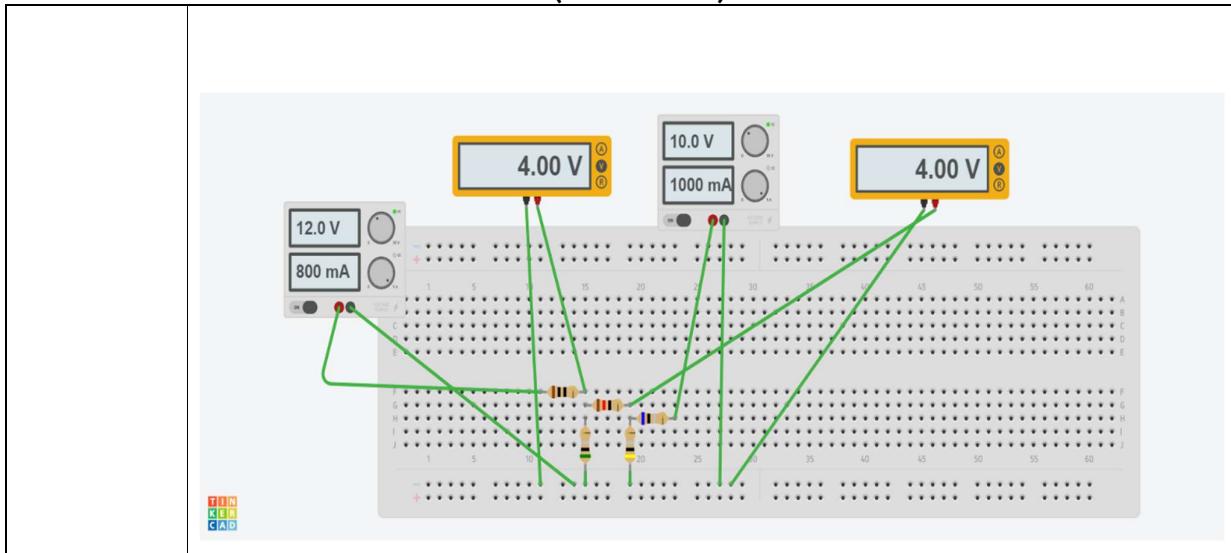


Table	Mesh currents	Theoretical Values	Observation Values
	i1 (A)	336 mA	336 mA
	i2 (A)	9.09 mA	9.09 mA

Table	Nodal voltages	Theoretical Values	Observation Values
	Va (V)	4 V	4 V
	Vb (V)	4 V	4 V

Conclusion:

1. We used Mesh analysis to find the values of current .
2. We used Nodal analysis to find the values of voltages .
3. For calculating the practical values ; we used an online simulation tool called Tinkercad
4. The Practical and Theoretical values when measured were found to be equal.



First Year (Semester I) B.Tech.

Basic Electrical and Electronics Engineering

Experiment No. : 03
Superposition Theorem


Name : Ayush Jain

SAP No. : 60004200132

Date of performance : 20/3/2021

Signature of teacher-in-charge : _____

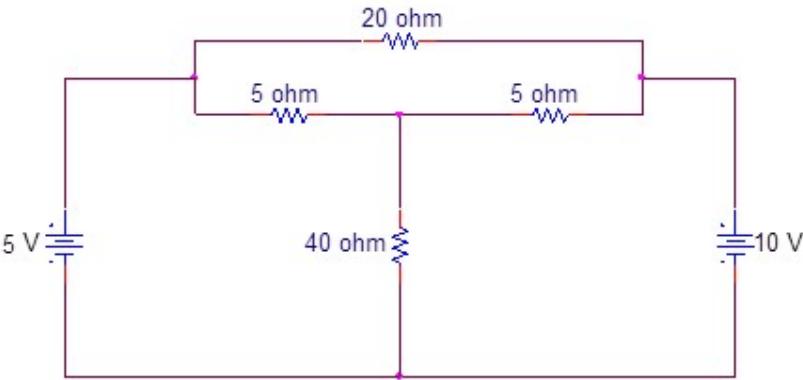


Aim:	To determine current and voltage value in a circuit using superposition theorem.
Apparatus :	Online simulation tools (Suggested Tinker cad)
Theoretical Analysis:	 <p>Fig. 1(a) Current across 40ohm resistor</p> <p>Theoretical Calculations: Current through 40ohm resistor</p>



First Year (Semester I) B.Tech.

Fig 1(a): Current across 40Ω resistor

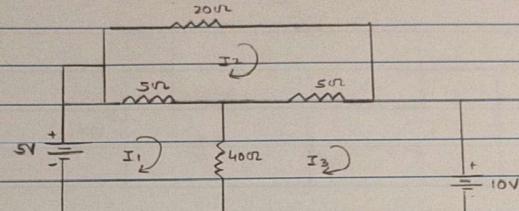

KVL in loop 1,

$$5 - 45I_1 + 5I_2 + 40I_3 = 0$$

$$\therefore -9I_1 + I_2 + 8I_3 = -1 \quad (i)$$

KVL in loop 2,

$$-30I_2 + 5I_1 + 5I_3 = 0$$

$$\therefore I_1 - 6I_2 + I_3 = 0 \quad (ii)$$

KVL in loop 3,

$$-45I_3 + 40I_1 + 5I_2 - 10 = 0$$


$$8I_1 + I_2 - 9I_3 = 2 \quad (iii)$$

On solving eq. (i), (ii) and (iii)

$$I_1 = -0.662 \text{ A}, I_2 = -0.25 \text{ A}, I_3 = -0.838 \text{ A}$$

$$\therefore i_{40\Omega} = I_3 - I_1 = 0.838 - 0.662 = 0.176 \text{ A}$$

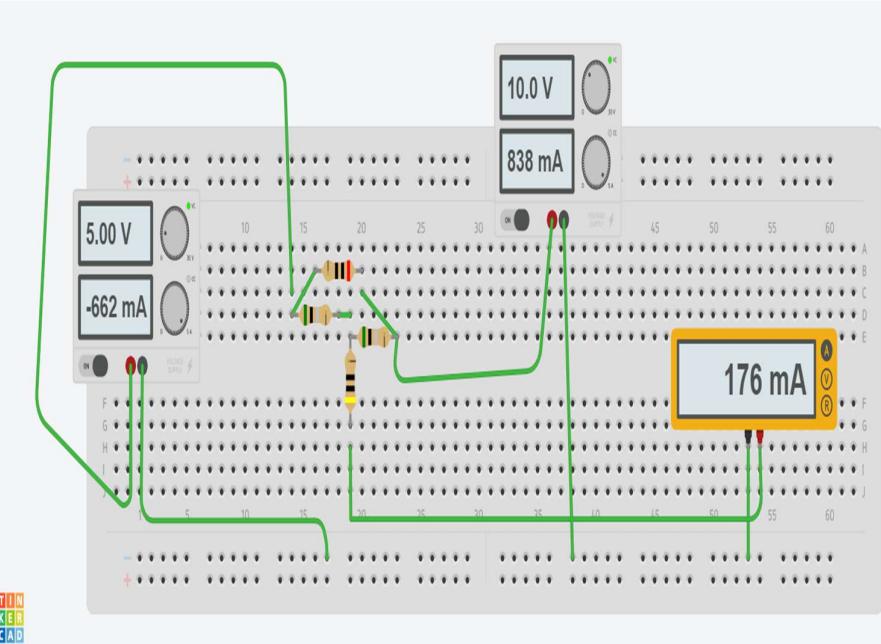
$$\therefore I_{40\Omega} = 176 \text{ mA.}$$





First Year (Semester I) B.Tech.

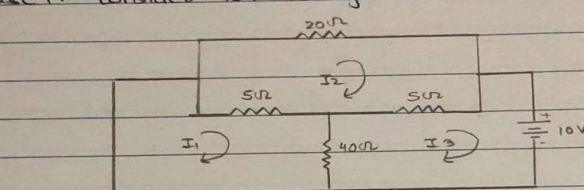Case 1: Consider 10V voltage source active.



KVL to loop 1,

$$-45I_1 + 5I_2 + 40I_3 = 0$$

$$\therefore -9I_1 + I_2 + 8I_3 = 0 \quad (1)$$

KVL to loop 2,

$$-30I_2 + 5I_1 + 5I_3 = 0$$

$$\therefore I_1 - 6I_2 + I_3 = 0 \quad (2)$$

KVL to loop 3,

$$-45I_3 + 40I_1 + 5I_2 - 10 = 0$$


$$\therefore 8I_1 + I_2 - 9I_3 = 2 \quad (3)$$

On solving (1), (2) and (3),

$$I_1 = -1.441 \text{ A}, I_2 = -0.5 \text{ A}, I_3 = -1.559 \text{ A}$$

$$\therefore I_{40\Omega} = I_2 - I_1 = 1.559 - 1.441 = 0.118 \text{ A}$$

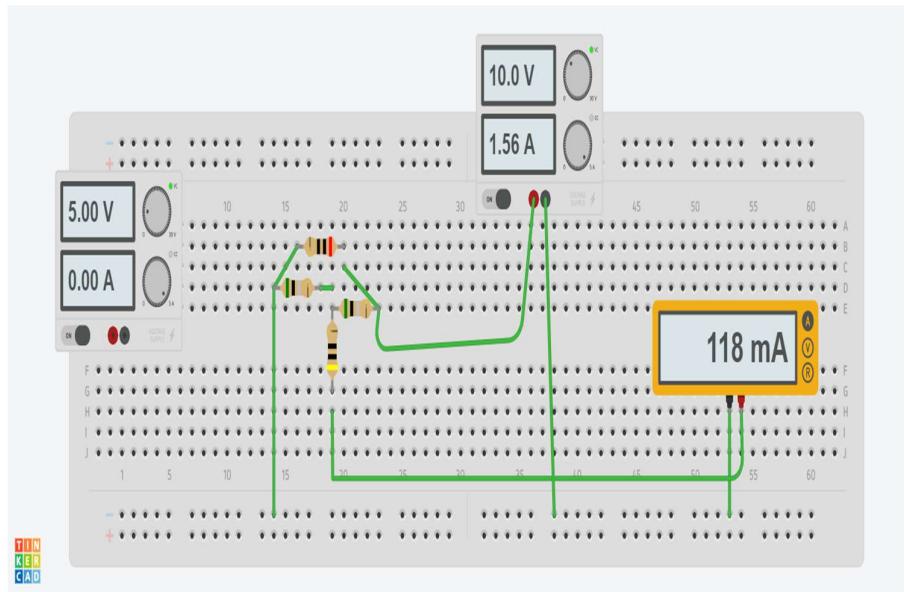
$$\therefore I_{40\Omega} = 118 \text{ mA } (\checkmark)$$





First Year (Semester I) B.Tech.

Case 2: 5V source is active.

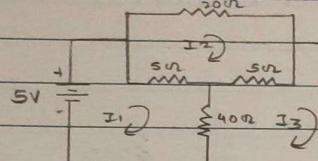

KVL in loop 1,

$$-45I_1 + 5 + 5I_2 + 40I_3 = 0$$

$$-9I_1 + I_2 + 8I_3 = -1 \quad (1)$$

KVL in loop 2,

$$-30I_2 + 5I_1 + 5I_3 = 0$$

$$\therefore I_1 - 6I_2 + I_3 = 0 \quad (2)$$

KVL in loop 3,

$$-45I_3 + 40I_1 + 5I_2 = 0$$


$$8I_1 + I_2 - 9I_3 = 0 \quad (3)$$

Solving (1), (2) and (3),

$$I_1 = 0.779 \text{ A}, I_2 = 0.25 \text{ A}, I_3 = 0.720 \text{ A}$$

$$I'_{40\Omega} = i_1 - i_3 = 0.059 \text{ A}$$
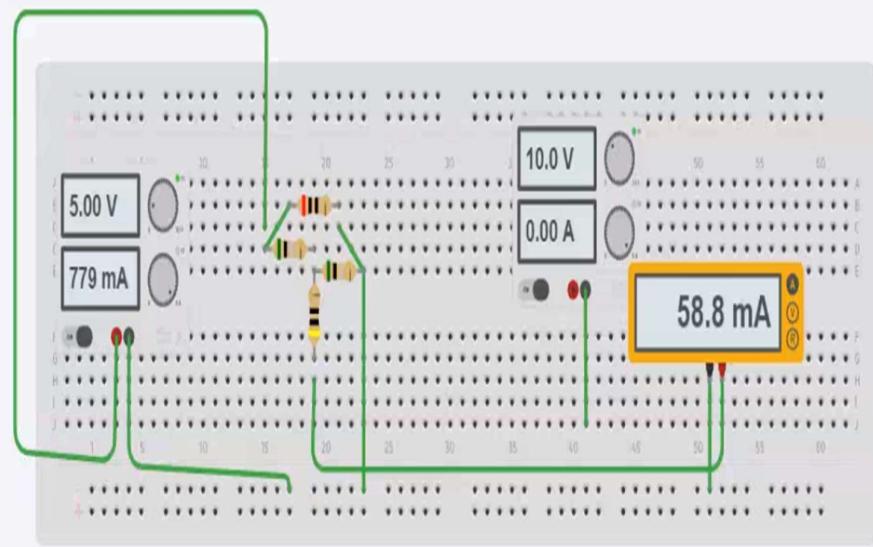
$$\therefore I'_{40\Omega} = 59 \text{ mA } (\downarrow)$$





First Year (Semester I) B.Tech.

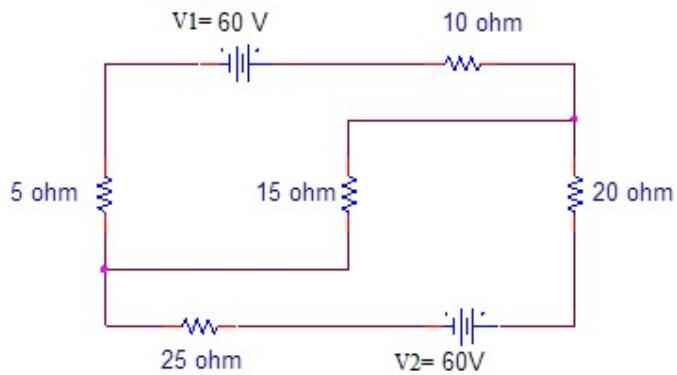


Fig. 1(b) Voltage across 15 ohm resistor


Theoretical Calculations:

Voltage across 15ohm resistor



First Year (Semester I) B.Tech.

Frg 1(b) Voltage across 15Ω resistor,

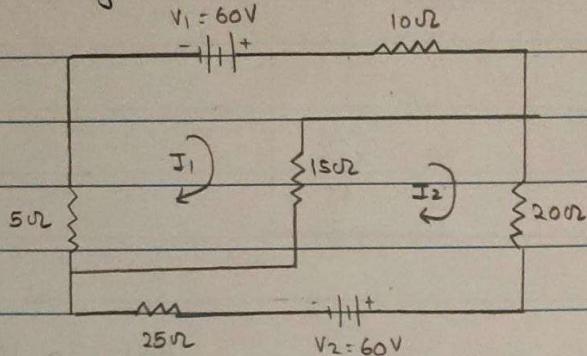

KVL in loop 1,

$$-30I_1 + 15I_2 + 60 = 0$$

$$\therefore -2I_1 + I_2 + 4 = 0$$

$$\therefore 2I_1 - I_2 = 4 \quad \text{--- (1)}$$

KVL in loop 2,

$$-60I_2 + 15I_1 - 60 = 0$$

$$\therefore -4I_2 + I_1 - 4 = 0$$

$$I_1 - 4I_2 = 4 \quad \text{--- (2)}$$


Solving (1) and (2)

$$\therefore I_1 = 1.714 \text{ A}, \quad I_2 = -0.571 \text{ A}$$

$$\therefore I_{15\Omega} = I_1 - I_2 = 2.285 \text{ A}$$

$$V_{15\Omega} = I_{15\Omega} \cdot 15 = 34.3 \text{ V}$$

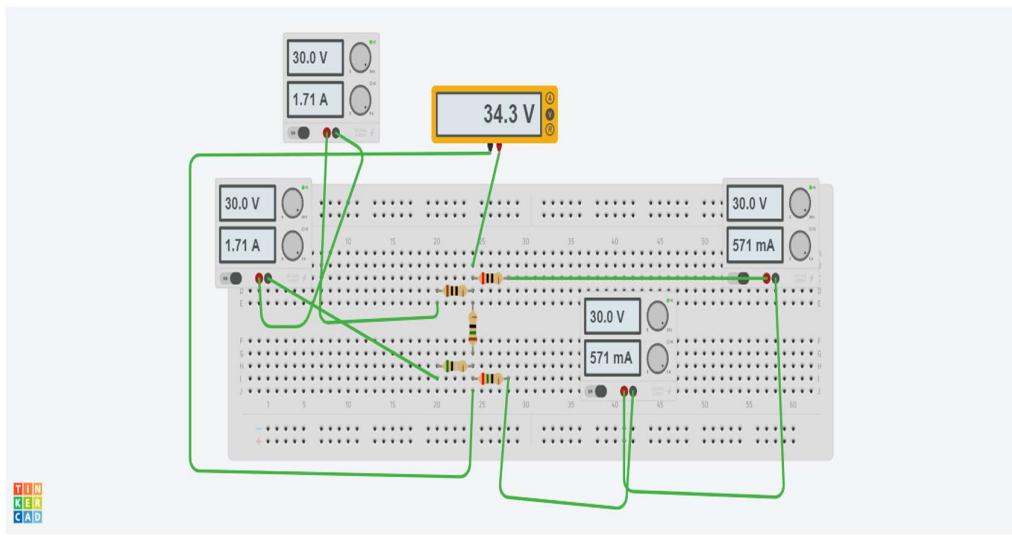
$$\therefore V_{15\Omega} = 34.3 \text{ V}$$





First Year (Semester I) B.Tech.

Consider 60 V marked V_2 as active.

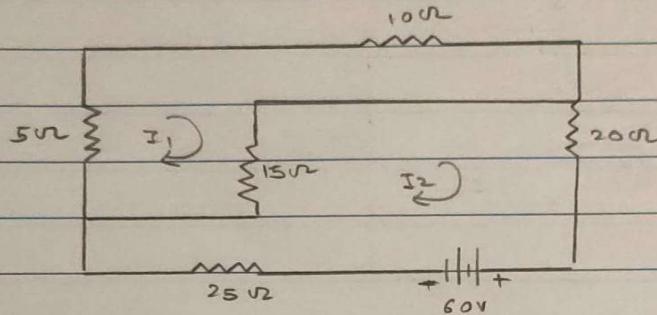

KVL in loop 1,

$$-30I_1 + 15I_2 = 0$$

$$-2I_1 + I_2 = 0 \quad \text{--- (1)}$$

KVL in loop 2,

$$-60I_2 + 15I_1 = 60$$

$$I_1 - 4I_2 = 4 \quad \text{--- (2)}$$


∴ On solving (1) and (2),

$$I_1 = -0.571 \text{ A} \quad , \quad I_2 = -1.142 \text{ A}$$

$$\therefore I_{15\Omega} = I_2 - I_1 = 0.571 \text{ A}$$

$$\therefore V'_{15\Omega} = I_{15\Omega} \times 15 = 0.571 \times 15$$

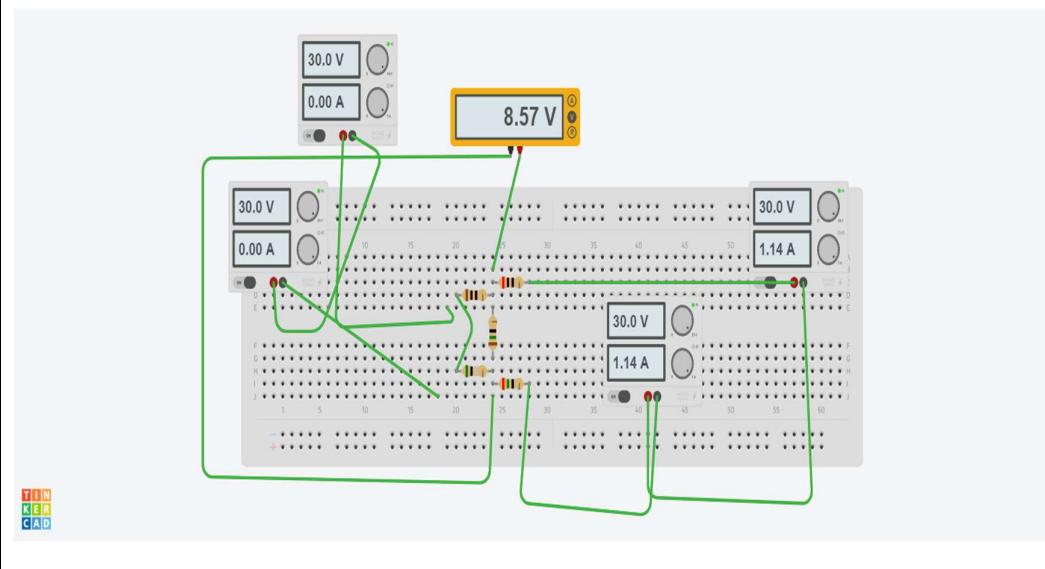
$$\therefore V_{15\Omega} = 8.57 \text{ V}$$





First Year (Semester I) B.Tech.

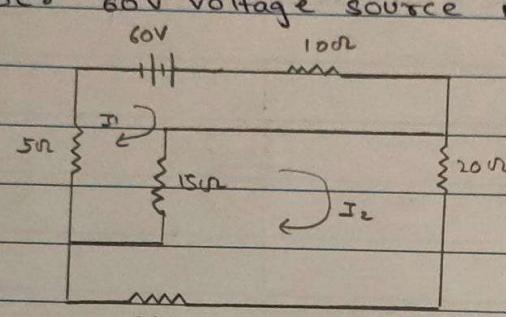
Consider 60V voltage source marked V_1 as active.



KVL in loop 1,

$$-30I_1 + 15I_2 + 60 = 0 \quad \text{(i)}$$

KVL in loop 2
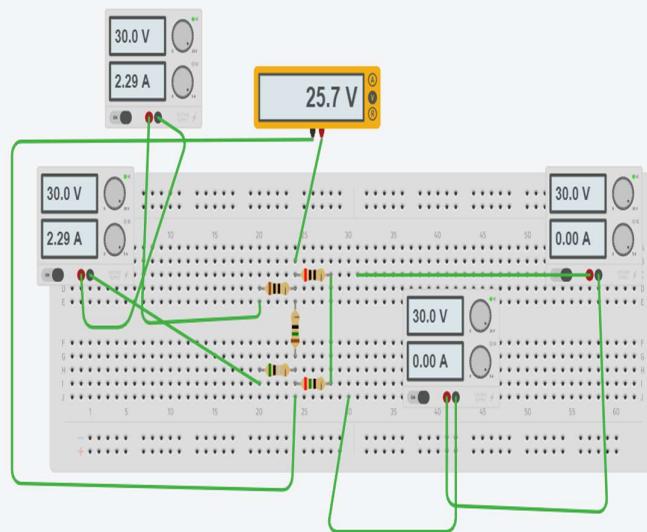
$$-60I_2 + 15I_1 = 0 \quad \text{(ii)}$$
$$\therefore 2I_1 - I_2 = 4 \quad \text{(i)}$$
$$\therefore I_1 - 4I_2 = 0 \quad \text{(ii)}$$
$$I_1 = 2.286 \text{ A} \quad , \quad I_2 = 0.571$$
$$\therefore V''_{15\Omega} = 2.286 - 0.571 = 1.715 \text{ A}$$
$$\therefore V''_{15\Omega} = 1.715 \times 15 = 25.7 \text{ V}$$
$$\therefore V''_{15\Omega} = 25.7 \text{ V}$$




First Year (Semester I) B.Tech.

	Active Voltage source	Theoretical values, $I_{40\Omega}$	Practical values, $I_{40\Omega}$
Observation Table	When 5V active	59 mA	58.8mA =59mA
	When 10V active	118mA	118mA

	Active Voltage source	Theoretical values, $V_{15\Omega}$	Practical values, $V_{15\Omega}$
Observation Table	When V1 active	25.7 V	25.7 V
	When V2 active	8.57 V	8.57 V

Conclusion:

- The Practical values have been attained by using online simulation tool Tinkercad.
- We used Superposition theorem to find the theoretical value of voltage and current.
- The theoretical and practical values are equal to each other.



First Year (Semester I) B.Tech.

Basic Electrical and Electronics Engineering

Experiment No. : 04
Thevenins and Nortons Theorem

Name : Ayush Jain

SAP No. : 60004200132

Date of performance : 27/03/2021

Signature of teacher-in-charge : _____




First Year (Semester I) B.Tech.

Aim:	To determine resistor, voltage and current value in a circuit.
Apparatus :	Online simulation tools (Suggested Tinkercad)
Theoretical Analysis:	<p>Thevenin's Theorem</p> <p>1</p> <p>Fig. 1(a) Voltage across R_L load resistor value 10ohm, 20ohm, 30ohm</p> <p>Theoretical Calculations:</p> <p>KVL in loop 1, $-100I_1 + 100I_2 + 10 = 0$ $10I_1 - 10I_2 = 1 \quad \text{--- (i)}$</p> <p>KVL in loop 2, $-190I_2 + 100I_1 = 0$ $10I_1 - 19I_2 = 0 \quad \text{--- (ii)}$</p> <p>On solving (i) and (ii) $I_1 = 0.211A$ $I_2 = 0.111A$</p> <p>KVL to find V_{TH}, $V_A + 20(I_1 - I_2) - 40I_2 - V_B = 0$ $V_A - V_B = 2.44$ $\therefore V_{TH} = V_{AB} = 2.44 V$</p>




First Year (Semester I) B.Tech.

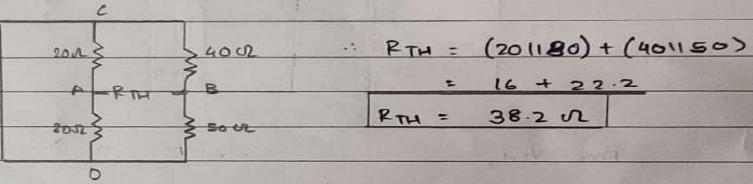NOW, for calculating R_{TH} , we short 10V source.



∴ Thevenin's equivalent circuit,

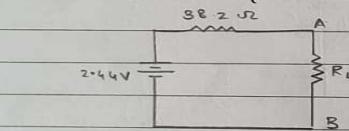

when $R_L = 10\Omega$


$$V_{10\Omega} = \frac{2.44 \times 10}{48.2} = 0.507V = 507mV$$

when $R_L = 20\Omega$,

$$V_{20\Omega} = \frac{2.44 \times 20}{58.2} = 0.838V = 838mV$$



when $R_L = 30\Omega$,
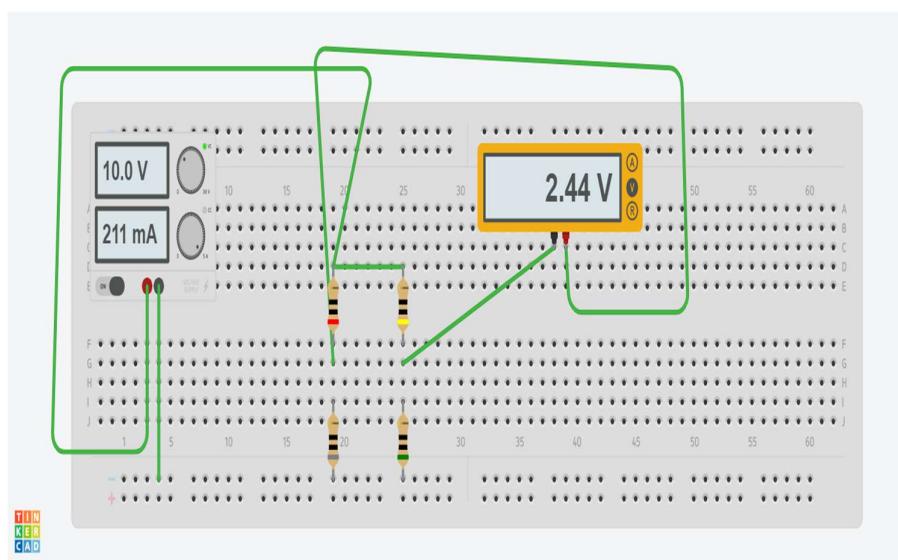
$$V_{30\Omega} = \frac{2.44 \times 30}{58.2} = 1.07V$$





First Year (Semester I) B.Tech.

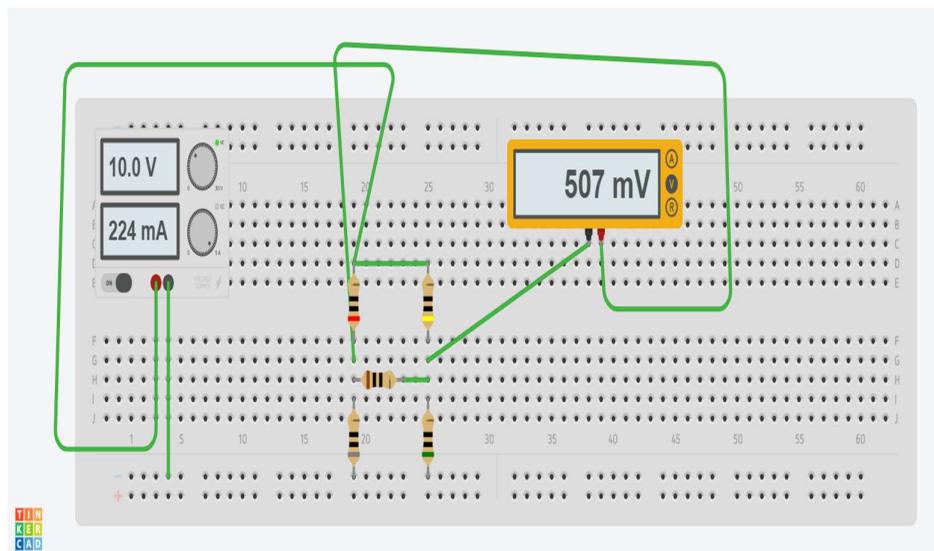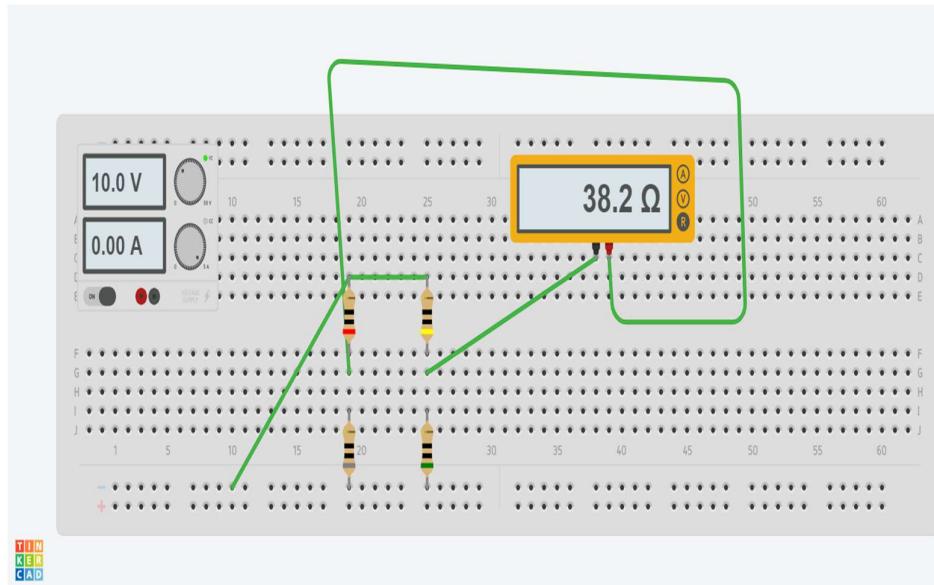



First Year (Semester I) B.Tech.

Nortons Theorem

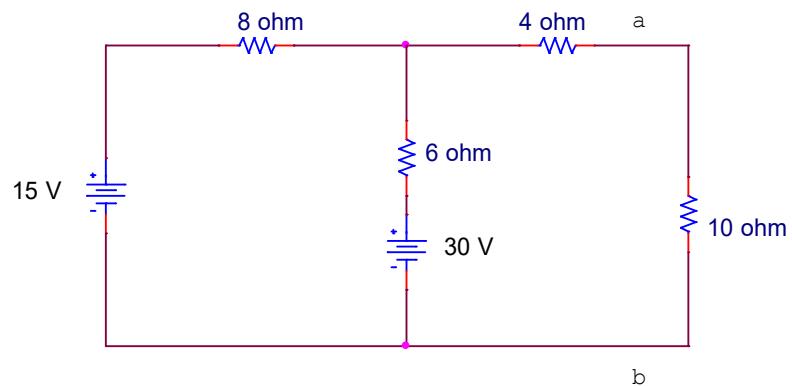


Fig. 1(b) Voltage across across a and b


Theoretical Calculations:

$$\text{KVL in loop 1, } -14I_1 + 6I_2 + 15 - 30 = 0$$
$$\therefore -14I_1 + 6I_2 = 15 \quad (1)$$
$$\text{Solving (1) and (2)}$$
$$\therefore I_1 = 0.286 \text{ A}$$
$$\text{KVL in loop 2, } -10I_2 + 6I_1 + 30 = 0$$
$$\therefore 6I_1 - 10I_2 = -30 \quad (2)$$
$$I_2 = 3.17 \text{ A}$$
$$\therefore I_{\text{IN}} = 3.17 \text{ A}$$



First Year (Semester I) B.Tech.


For R_N , short 15V and 30V sources.

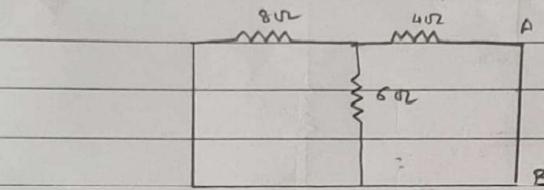

$$\therefore R_N = (8\parallel 6) + 4 = 7.43 \Omega$$


$$\therefore R_N = 7.43 \Omega$$

\therefore Norton's equivalent circuit,

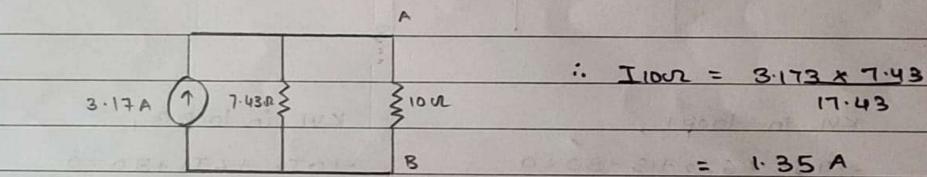



\therefore Voltage across A and B = $V_{AB} = 1.35 \times 10$

$$\therefore V_{AB} = 13.5 V$$

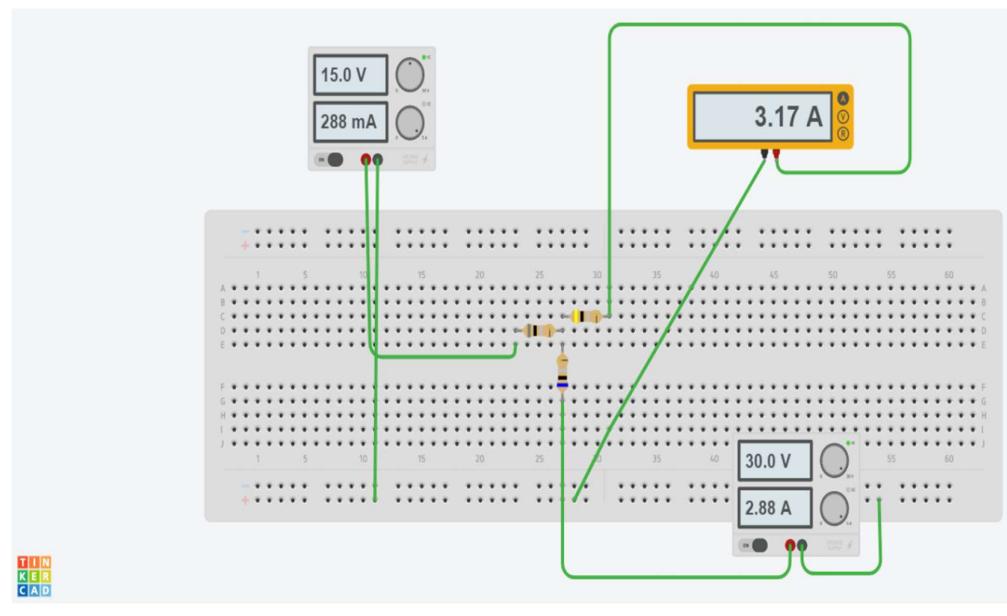



First Year (Semester I) B.Tech.

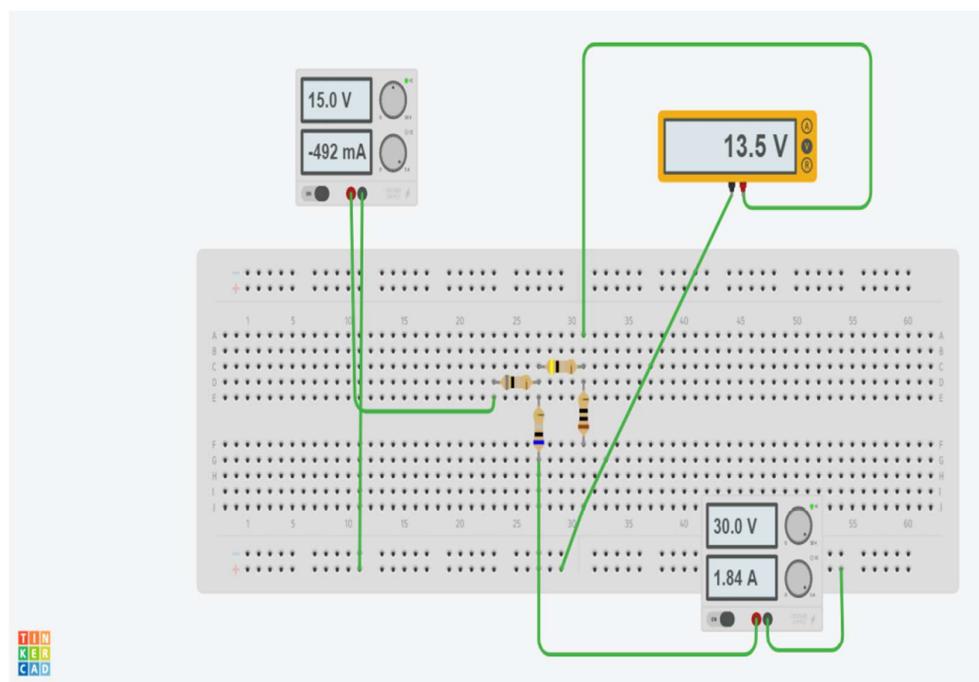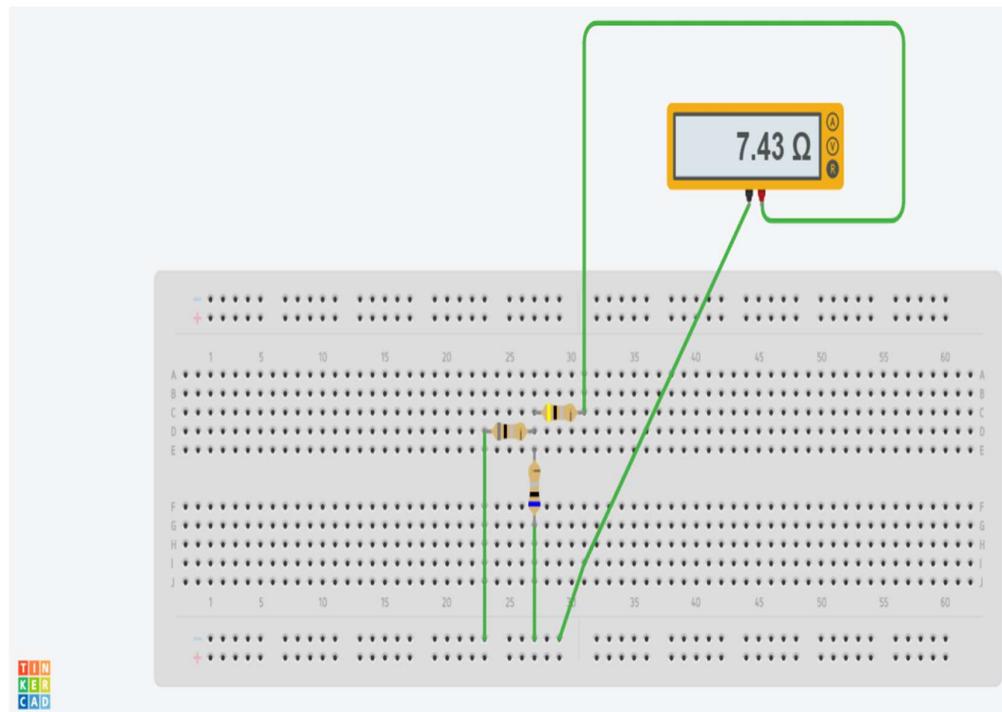



First Year (Semester I) B.Tech.

--	--

		Theoretical values	Practical values
Observation Table	Thevenins Voltage, V_{TH}	2.44V	2.44V
	Equivalent resistor, R_{TH}	38.2 ohm	38.2 ohm
	Voltage $V_{10\Omega}$	507 mV	507mV
	Voltage $V_{20\Omega}$	838 mV	838 mV
	Voltage $V_{30\Omega}$	1.07 mV	1.07 mV

		Theoretical values	Practical values
Observation Table	Nortons Current, I_N	3.17 A	3.17 A
	Equivalent resistor, R_N	7.43 ohm	7.43 ohm
	Voltage $V_{10\Omega}$	13.5 V	13.5 V

Conclusion:

- The Practical values has been attained using online simulation tool Tinkercad.
- Thevenins and Nortons Theorems are used to determine the values of current,resistance and voltage.
- The Theoretical and Practical values are equal to each other

Basic Electrical and Electronics Engineering


Experiment No. : 05
AC Circuit Analysis

Name : Ayush Jain

SAP No. : 60004200132

Date of performance : 03 |04 |2021

Signature of teacher-in-charge : _____

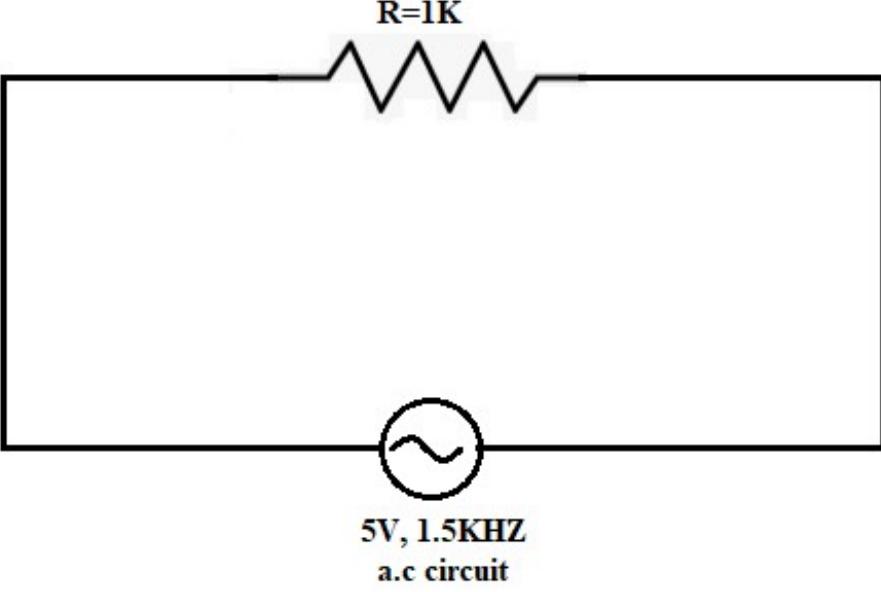Aim:	A.C through 1) Resistor 2) R-L Series circuit 3) R-C Series circuit										
Apparatus:	Online simulation tools (Suggested Tinkercad)										
Theoretical Analysis:	 <p style="text-align: center;">5V, 1.5KHZ a.c circuit</p> <p><i>Fig. 1(a) A.C through resistor</i></p> <p>Theoretical Calculations:</p> <p>$V=IZ$</p> <p>Since $Z=R$</p> <p>$I=V/R$</p> <p>Table 1</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="text-align: center; padding: 2px;">Sr. No.</th> <th style="text-align: center; padding: 2px;">Frequency</th> <th style="text-align: center; padding: 2px;">Current</th> <th style="text-align: center; padding: 2px;">Voltage</th> <th style="text-align: center; padding: 2px;">Resistance</th> </tr> </thead> <tbody> <tr> <td style="text-align: center; padding: 2px;">1.</td> <td style="text-align: center; padding: 2px;">1000Hz</td> <td style="text-align: center; padding: 2px;">1mA</td> <td style="text-align: center; padding: 2px;">5V</td> <td style="text-align: center; padding: 2px;">1K ohm</td> </tr> </tbody> </table>	Sr. No.	Frequency	Current	Voltage	Resistance	1.	1000Hz	1mA	5V	1K ohm
Sr. No.	Frequency	Current	Voltage	Resistance							
1.	1000Hz	1mA	5V	1K ohm							

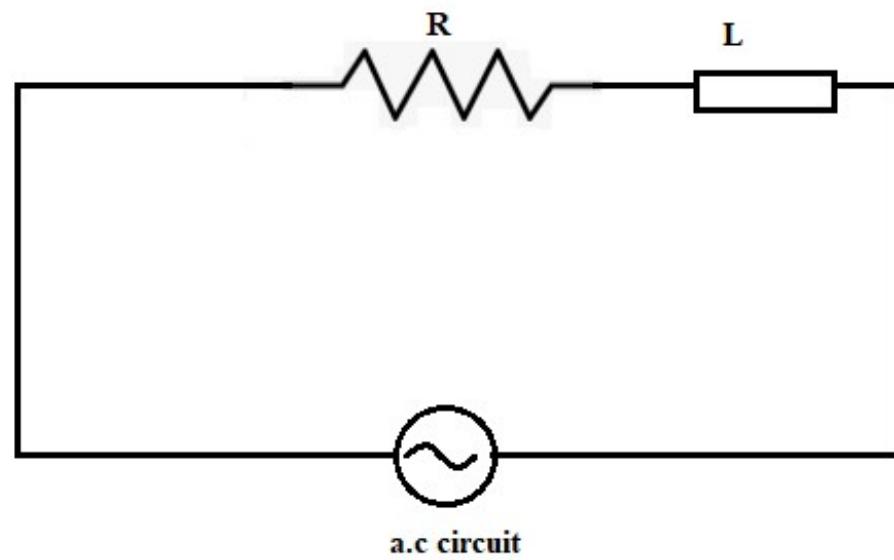
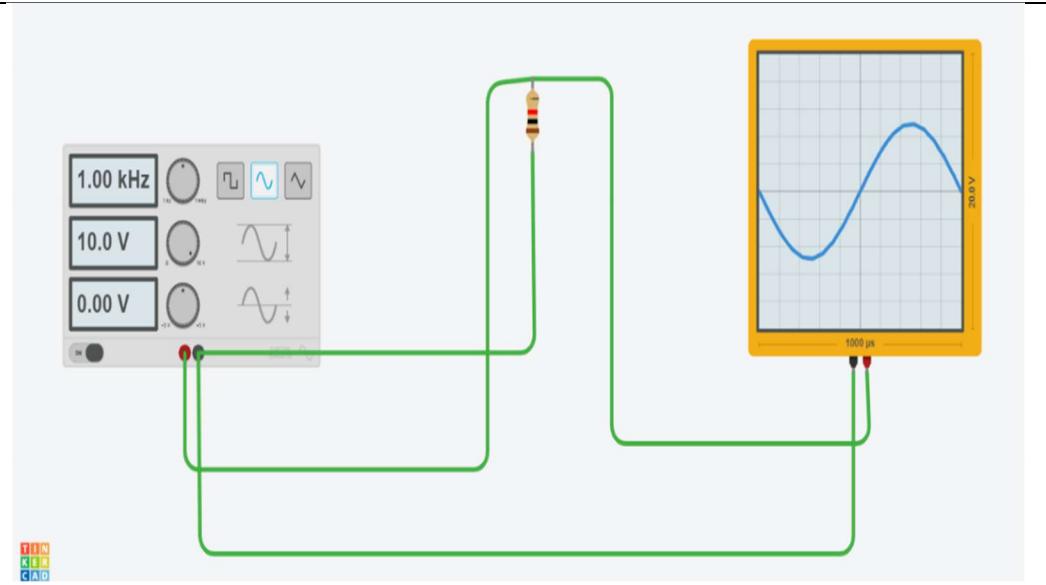


Fig. 1(b) R-L Series circuit

Theoretical Calculations:

R-L series circuit. ($L = 100 \text{ mH}$, $f = 50 \text{ Hz}$, $V = 5 \text{ V}$)						
Theoretical Table						
Sr. No.	R (Ω)	Z (Ω)	I (A)	V_R (V)	V_L (V)	V_T (V)
1.	100 Ω	104.82	0.048	4.8	1.51	5
2.	50 Ω	59.05	0.085	4.25	2.67	5
3.	10 Ω	32.97	0.152	1.52	4.78	5

Theoretical calculations:

i) When $R = 100 \Omega$, ii) when $R = 50 \Omega$

$$Z = \sqrt{R^2 + X_L^2} = 104.82 \Omega \quad Z = \sqrt{R^2 + X_L^2} = 59.05 \Omega$$

$$V_R = IR = 4.8 \text{ V} \quad V_R = IR = 4.25 \text{ V}$$

$$V_L = IX_L = 1.51 \text{ V} \quad V_L = IX_L = 2.67 \text{ V}$$

$$V_T = \sqrt{V_R^2 + V_L^2} = 5 \text{ V} \quad V_T = \sqrt{V_R^2 + V_L^2} = 5 \text{ V}$$

iii) when $R = 10 \Omega$

$$Z = \sqrt{R^2 + X_L^2} = 32.97 \Omega$$

$$V_R = IR = 1.52 \text{ V}$$

$$V_L = IX_L = 4.78 \text{ V}$$

$$V_T = \sqrt{V_R^2 + V_L^2} = 5 \text{ V}$$

Practical Calculations Table:

Sr. No.	Resistance	Current	V_R	V_L	V_T
1.	100 ohm	47 mA	4.7 V	1.5 V	4.93 V
2.	50 ohm	82 mA	4.1 V	2.5 V	4.80 V
3.	10 ohm	150 mA	1.4 V	4.4 V	4.63 V

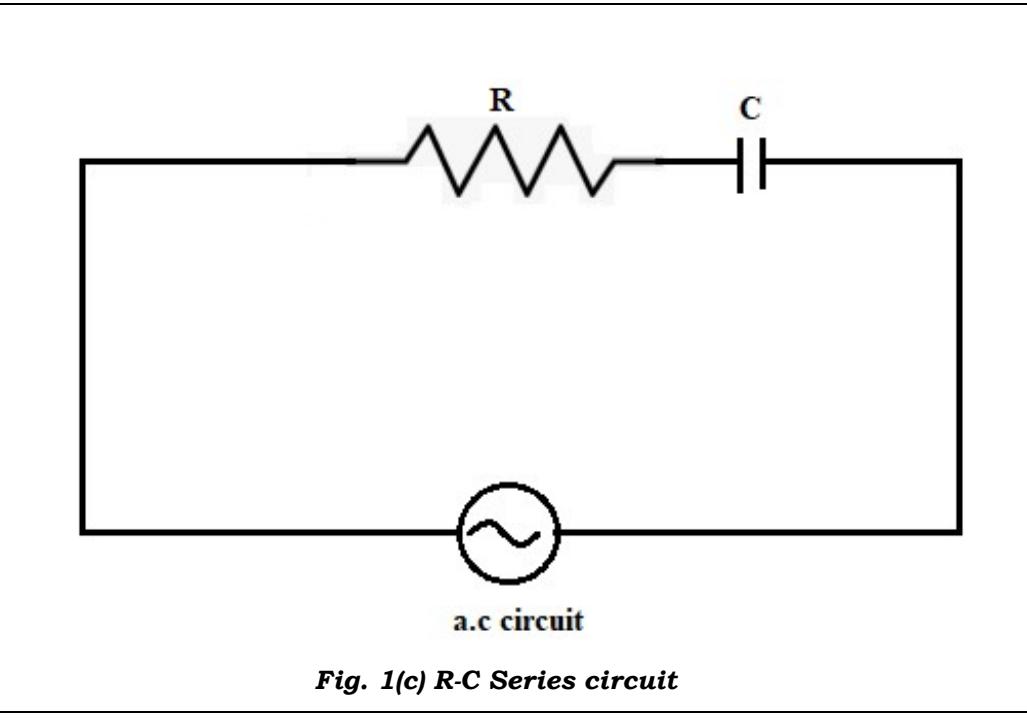
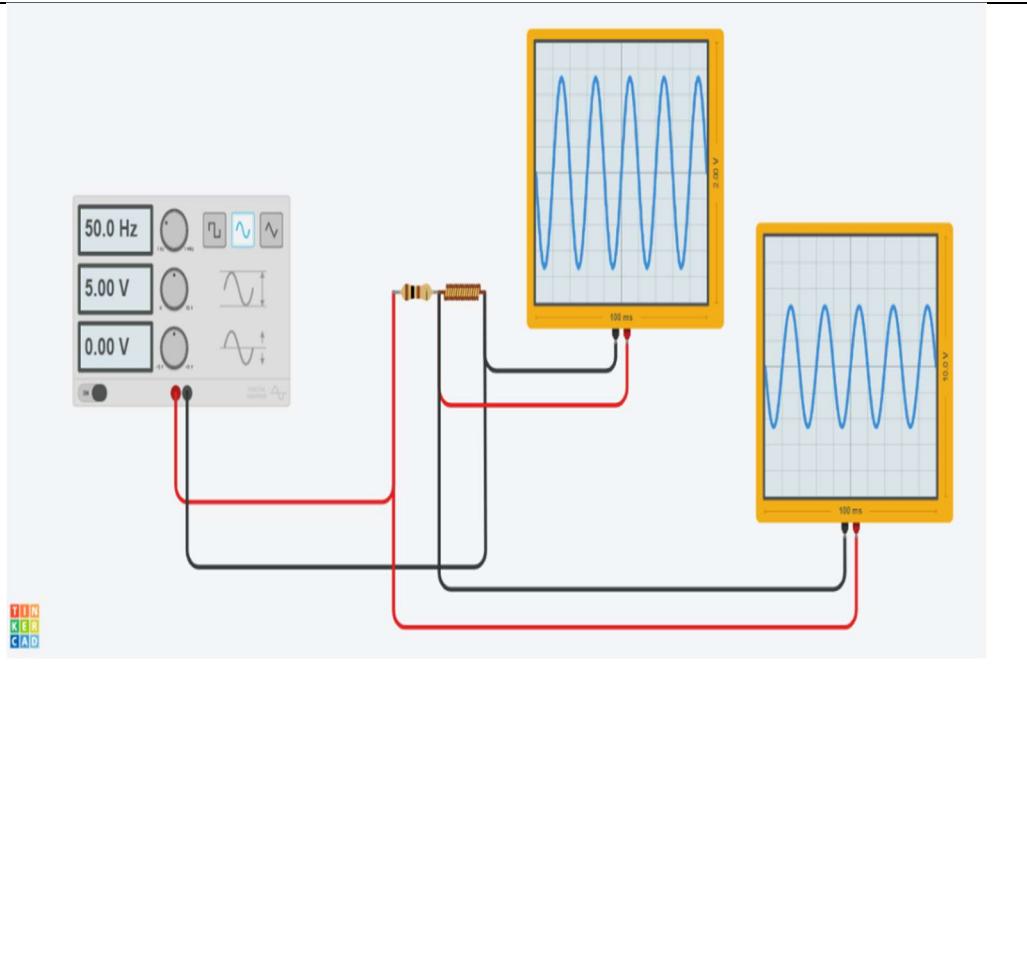


Fig. 1(c) R-C Series circuit

R-C series circuit.

$$[C = 0.1 \mu F, f = 50 \text{ Hz}, V = 5 \text{ V}]$$

$$X_C = 1/2\pi f C = 3183.1 \Omega$$

Table

Sr. No.	R	Z	I	V _R	V _C	V _T
	(Ω)	(Ω)	(mA)	(V)	(V)	(V)
1.	100 kΩ	104943	0.0476	4.76	1.52	5
2.	50 kΩ	59272	0.0844	4.22	2.69	5
3.	10 kΩ	33365	0.1499	1.50	4.77	5

Theoretical calculations:

1) When R = 100 kΩ

$$Z = \sqrt{R^2 + X_C^2} = 104943 \Omega$$

$$V_R = IR = 4.76 \text{ V}$$

$$V_C = IX_C = 1.52 \text{ V}$$

$$V_T = \sqrt{V_R^2 + V_C^2} = 5 \text{ V}$$

2) When R = 50 kΩ

$$Z = \sqrt{R^2 + X_C^2} = 59272 \Omega$$

$$V_R = IR = 4.22 \text{ V}$$

$$V_C = IX_C = 2.69 \text{ V}$$

$$V_T = \sqrt{V_R^2 + V_C^2} = 5 \text{ V}$$

3) When R = 10 kΩ

$$Z = \sqrt{R^2 + X_C^2} = 33365 \Omega$$


$$V_R = IR = 1.50 \text{ V}$$

$$V_C = IX_C = 4.77 \text{ V}$$

$$V_T = \sqrt{V_R^2 + V_C^2} = 5 \text{ V}$$

Practical Calculations Table:

Sr. No.	Resistance	Current	V _R	V _C	V _T
1.	100 K ohm	0.045 mA	4.5 V	1.44 V	4.72 V
2.	50 K ohm	0.084 mA	4.2 V	2.7 V	4.99 V
3.	10 K ohm	0.146 mA	1.46 V	4.6 V	4.826 V

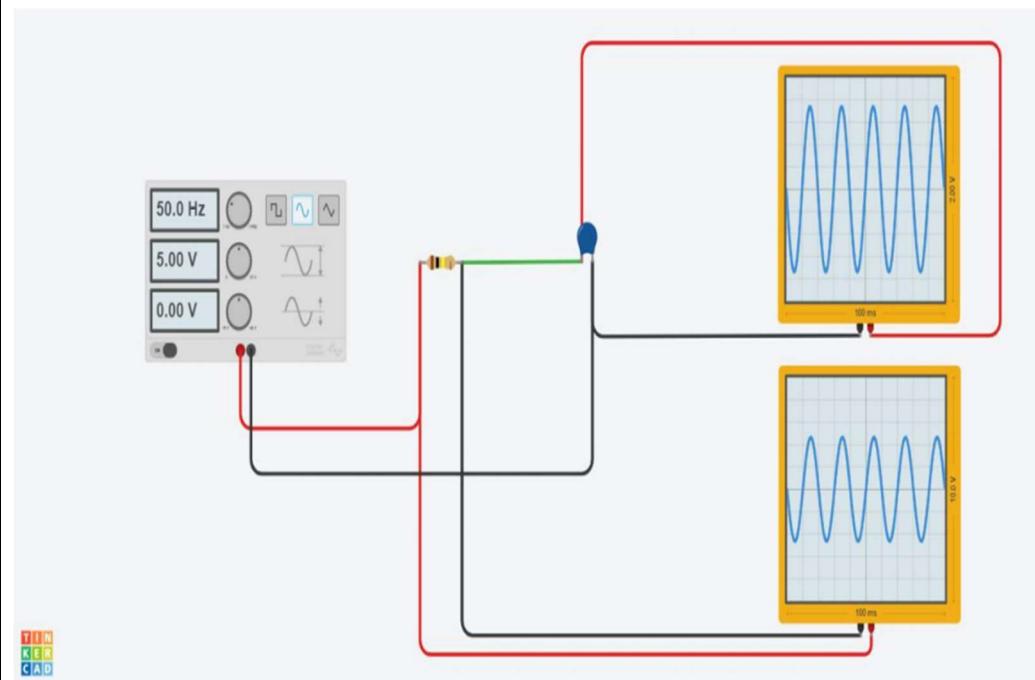

Conclusion:

- We applied properties and formulae of pure R,series R-L and series R-C circuit for theoretical calculations.
- The practical values have been attained using an online simulation tool, Tinkercad.
- The theoretical and measured values are almost equal to each other.



First Year (Semester I) B.Tech.

Basic Electrical and Electronics Engineering

Experiment No : 06
Rectifier Circuit

Name : Ayush Jain



SAP No. : 60004200132

Date of performance : 10/04/2021

Signature of teacher-in-charge : _____



First Year (Semester I) B.Tech.

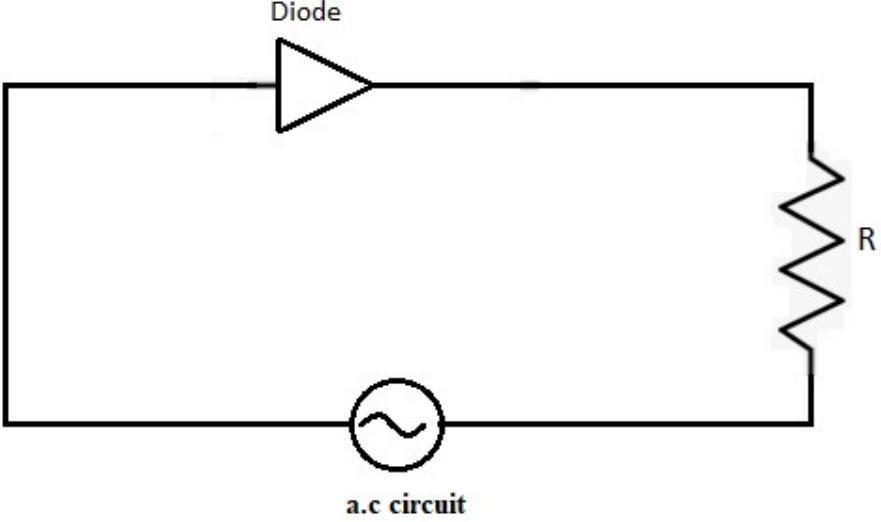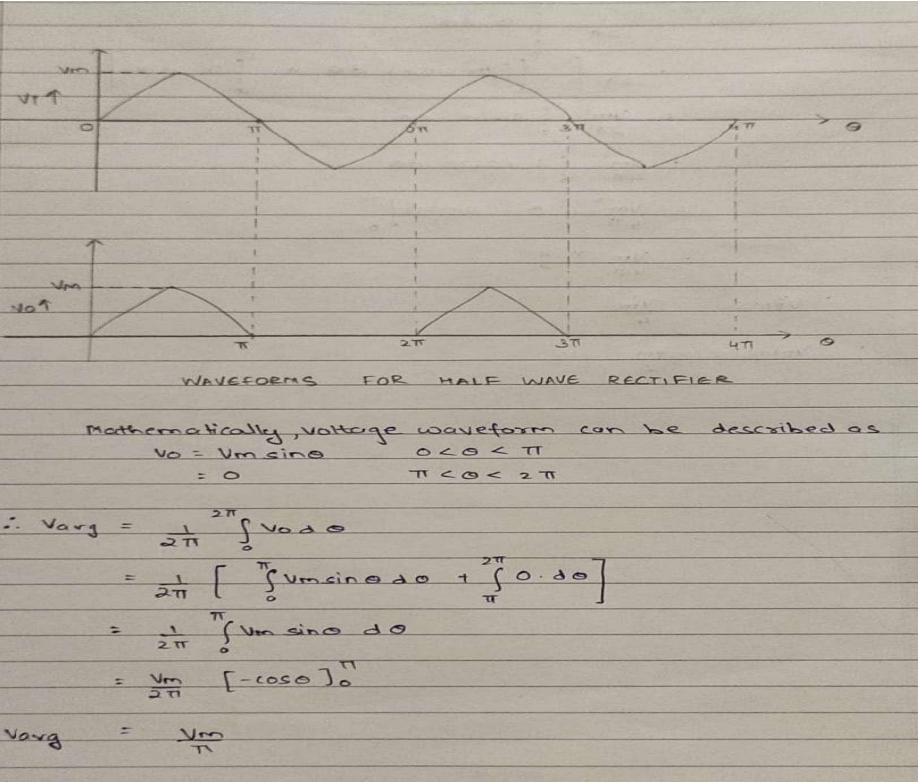
Aim:	To design Half wave and full wave rectifier.
Apparatus:	Online simulation tools (Suggested Tinkercad)
Theoretical Analysis:	<p><u>Half Wave Rectifier</u></p> <p><u>Circuit Diagram</u></p>  <p style="text-align: center;">a.c circuit</p> <p>Fig LCR series resonance</p> <p><u>Theoretical Calculations:</u></p> <p>RMS and Average Value of a voltage (derivation)</p> 



First Year (Semester I) B.Tech.

$$\begin{aligned} (V_{RMS})^2 &= \frac{1}{2\pi} \int_0^{2\pi} V_o^2 d\theta \\ &= \frac{1}{2\pi} \left[\int_0^{\pi} (V_m \sin\theta)^2 d\theta + \int_{\pi}^{2\pi} 0^2 d\theta \right] \\ &= \frac{V_m^2}{2\pi} \int_0^{\pi} \sin^2\theta d\theta \\ &= \frac{V_m^2}{2\pi} \int_0^{\pi} \frac{1 - \cos 2\theta}{2} d\theta \\ &= \frac{V_m^2}{4\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{\pi} \\ &= \frac{V_m^2}{4\pi} \times \pi \\ V_{RMS}^2 &= \frac{V_m^2}{4} \\ V_{RMS} &= \frac{V_m}{2} \end{aligned}$$

Observation waveform

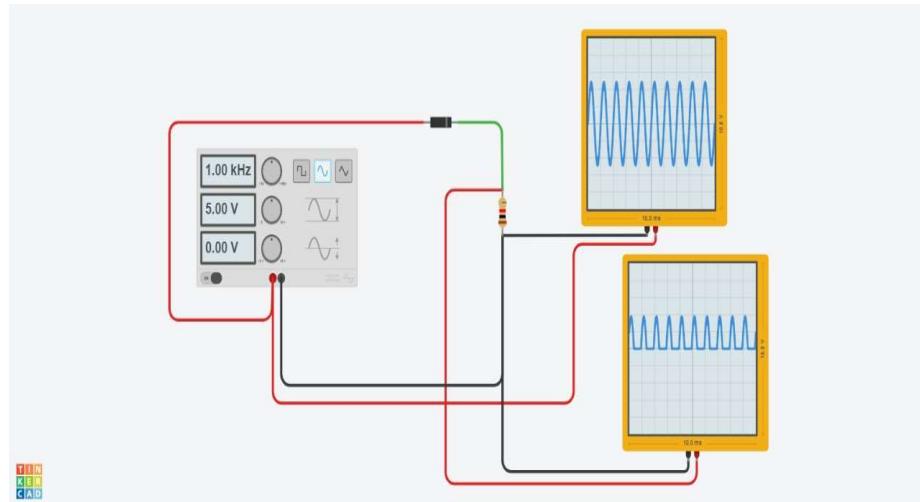




First Year (Semester I) B.Tech.


Full wave rectifier

Bridge Rectifier

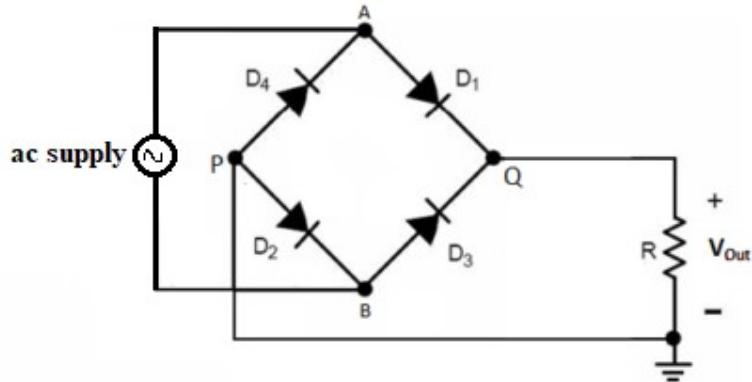

Theoretical Calculations:

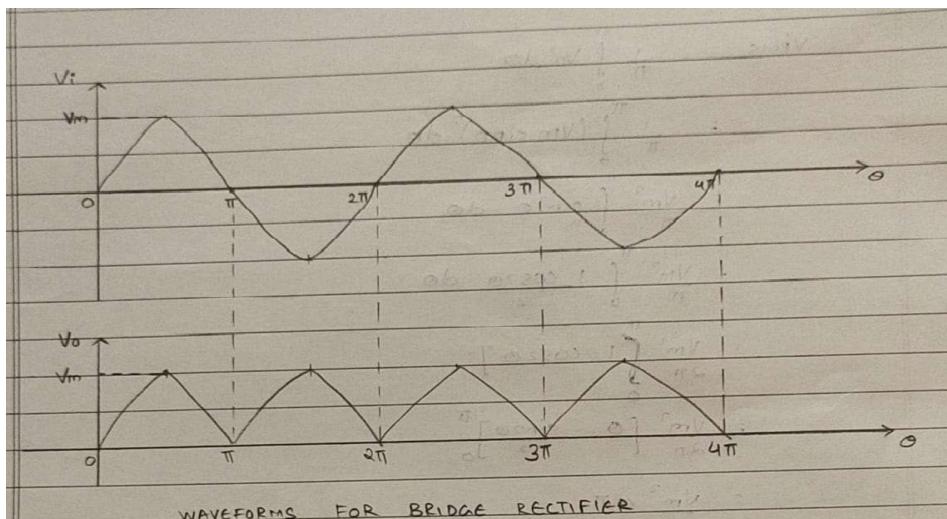RMS and Average Value of a voltage (derivation)



Mathematically, voltage waveforms can be described as

$$V_o = V_m \sin \theta \quad 0 < \theta < \pi$$

$$\begin{aligned} V_{avg} &= \frac{1}{\pi} \int_0^{\pi} V_o d\theta \\ &= \frac{1}{\pi} \int_0^{\pi} V_m \sin \theta d\theta \\ &= \frac{V_m}{\pi} \left[-\cos \theta \right]_0^{\pi} \end{aligned}$$


$$V_{avg} = \frac{2V_m}{\pi}$$



First Year (Semester I) B.Tech.

$$\begin{aligned} \bar{V}_{\text{rms}}^2 &= \frac{1}{\pi} \int_0^{\pi} V_0^2 d\theta \\ &= \frac{1}{\pi} \int_0^{\pi} (V_m \sin \theta)^2 d\theta \\ &= \frac{V_m^2}{\pi} \int_0^{\pi} \sin^2 \theta \cdot d\theta \\ &= \frac{V_m^2}{\pi} \int_0^{\pi} \frac{1 - \cos 2\theta}{2} \cdot d\theta \\ &= \frac{V_m^2}{2\pi} \int_0^{\pi} [1 - \cos 2\theta] d\theta \\ &= \frac{V_m^2}{2\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{\pi} \\ &= \frac{V_m^2}{2\pi} \times \pi \\ \therefore \bar{V}_{\text{rms}} &= \frac{V_m^2}{2} \\ \therefore V_{\text{rms}} &= \frac{V_m}{\sqrt{2}} \end{aligned}$$

Observation waveform

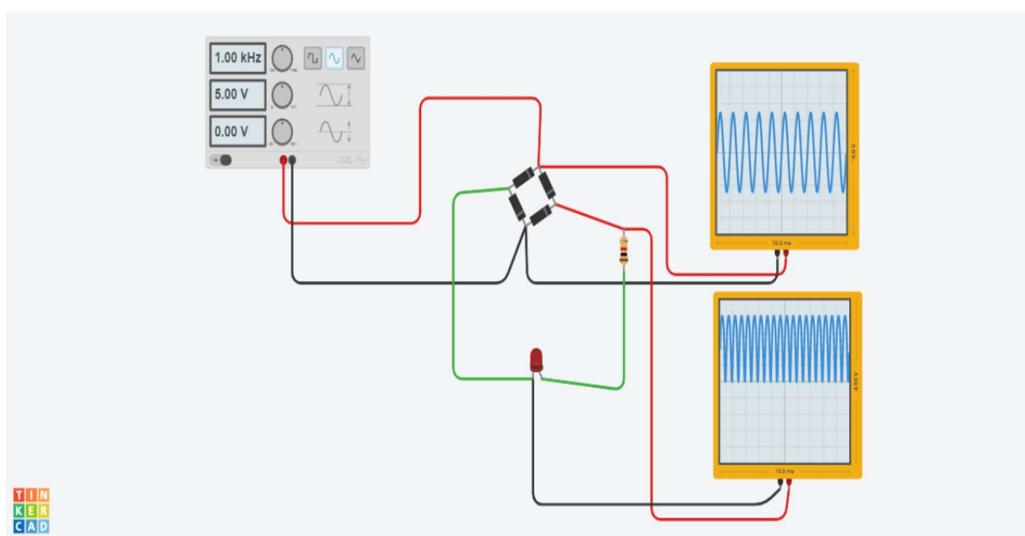



First Year (Semester I) B.Tech.

Conclusion:

- The circuits are made using an online simulation tool, Tinkercad
- This experiment helped us study the waveforms generated by a half wave and full wave (bridge) rectifier by implementing the circuit and making measurements using an oscilloscope.



First Year (Semester I) B.Tech.

Basic Electrical and Electronics Engineering

Experiment No : 07
Clipper and Clamper Circuit


Name : Ayush Jain

SAP No. : 60004200132

Date of performance : 17/4/2021


Signature of teacher-in-charge : _____

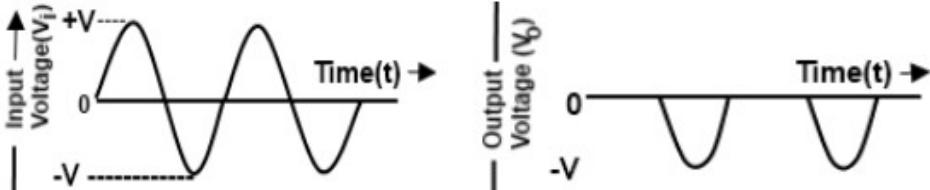

Aim:	To design clipper and clamper circuit .
Apparatus:	Online simulation tools (Suggested Tinkercad)
Theory:	<p>Clipper circuit</p> <p>The Clipper circuit that is intended to attenuate positive portions of the input signal can be termed as a Positive Clipper.</p> <p>Positive Clipper circuit:</p> <p>A Clipper circuit in which the diode is connected in series to the input signal and that attenuates the positive portions of the waveform, is termed as Positive Series Clipper.</p> <p>The diode will conduct until the supply voltage is less than the battery potential. As battery potential dominates the supply voltage, the signal appears at the positive half of output waveform. But as the supply voltage exceeds the battery potential, the diode is now reverse biased. Resultantly no further current will flow through the diode.</p>  <p>Negative clipper circuit</p> <p>As we can see in the circuit shown above, the diode is reverse bias due to both supply voltage and battery potential. This cuts off the complete positive half of the input waveform.</p> <p>But during the negative half cycle of the input waveform, the diode is in forward biased condition due to supply voltage but is reverse biased by the battery potential.</p> <p>Here also initially when battery dominates the supply voltage, the diode is in reverse biased condition. But, as the supply voltage becomes greater than the battery potential, the diode will automatically come in forward biased condition. Thus, the signal starts to appear at the output.</p>



First Year (Semester I) B.Tech.

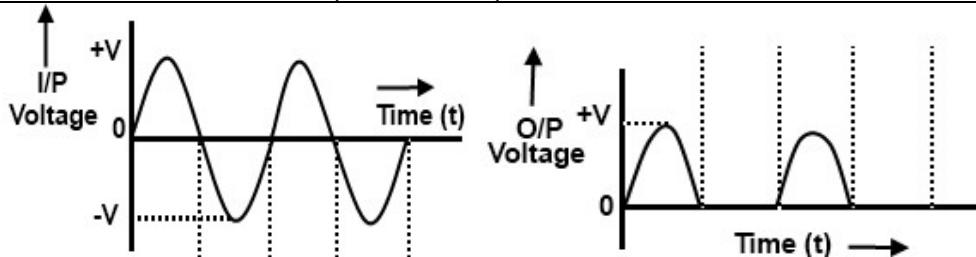

Clamper circuit

A Clamper Circuit is a circuit that adds a DC level to an AC signal. Actually, the positive and negative peaks of the signals can be placed at desired levels using the clamping circuits. As the DC level gets shifted, a clamper circuit is called as a **Level Shifter**.

Clamper circuits consist of energy storage elements like capacitors. A simple clamper circuit comprises of a capacitor, a diode, a resistor and a dc battery if required.

Clamper Circuit

A Clamper circuit can be defined as the circuit that consists of a diode, a resistor and a capacitor that shifts the waveform to a desired DC level without changing the actual appearance of the applied signal.

In order to maintain the time period of the wave form, the **tau** must be greater than, half the time period dischargingtimeofthecapacitorshouldbeslow.dischargingtimeofthecapacitor shouldbeslow.

$$\tau = RC$$

Where

- R is the resistance of the resistor employed
- C is the capacitance of the capacitor used

The time constant of charge and discharge of the capacitor determines the output of a clamper circuit.

- In a clamper circuit, a vertical shift of upward or downward takes place in the output waveform with respect to the input signal.
- The load resistor and the capacitor affect the waveform. So, the discharging time of the capacitor should be large enough.

Positive Clamper Circuit


A Clamping circuit restores the DC level. When a negative peak of the signal is raised above to the zero level, then the signal is said to be **positively clamped**.

A Positive Clamper circuit is one that consists of a diode, a resistor and a capacitor and that shifts the output signal to the positive portion of the input



First Year (Semester I) B.Tech.

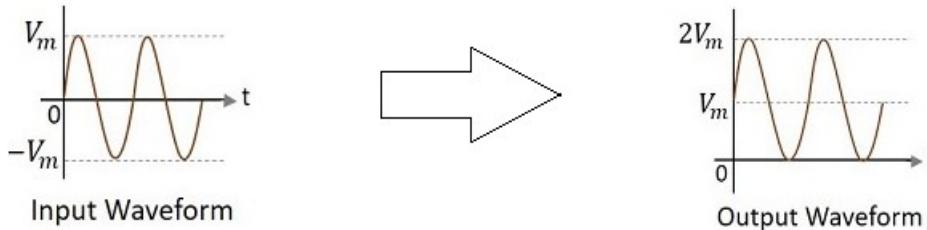signal. The figure below explains the construction of a positive clamper circuit.




Negative Clamper

A Negative Clamper circuit is one that consists of a diode, a resistor and a capacitor and that shifts the output signal to the negative portion of the input signal. The figure below explains the construction of a negative clamper circuit.

During the positive half cycle, the capacitor gets charged to its peak value v_m . The diode is forward biased and conducts. During the negative half cycle, the diode gets reverse biased and gets open circuited. The output of the circuit at this moment will be

$$V_0 = V_i + V_m$$

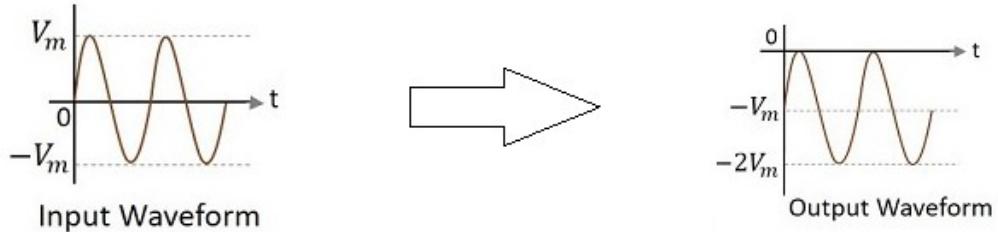Hence the signal is negatively clamped as shown in the above figure. The output signal changes according to the changes in the input, but shifts the level according to the charge on the capacitor, as it adds the input voltage.



Circuit Diagram:

Clipper circuit

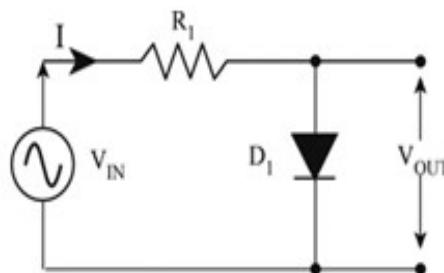


Fig 1. Positive clipper circuit



First Year (Semester I) B.Tech.


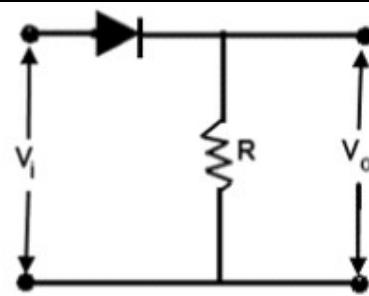


Fig 2. Negative clipper circuit


Observation waveform

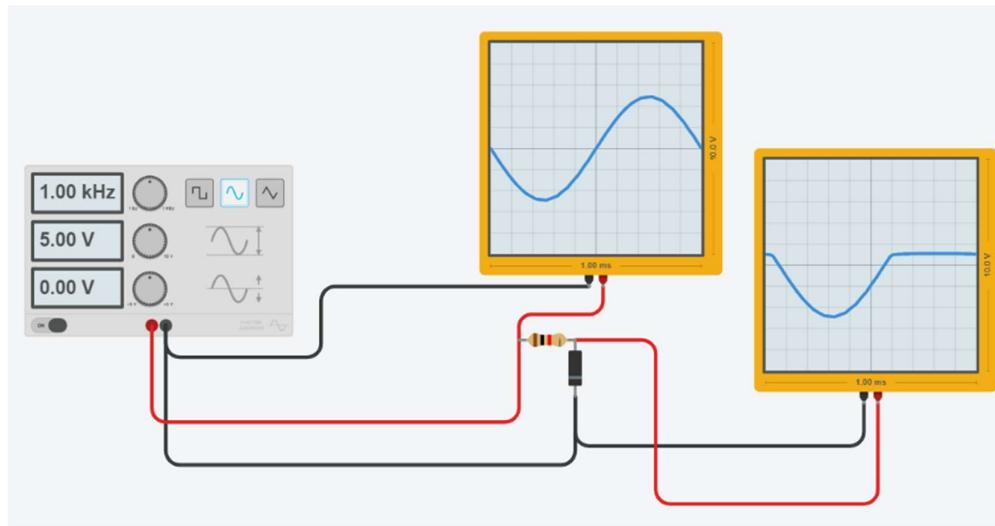

Positive Clipper

Clamper circuit

Circuit Diagram

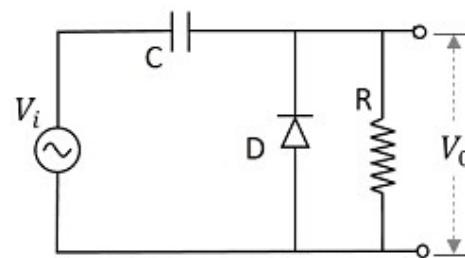



First Year (Semester I) B.Tech.

Fig 3. Positive Clamper Circuit



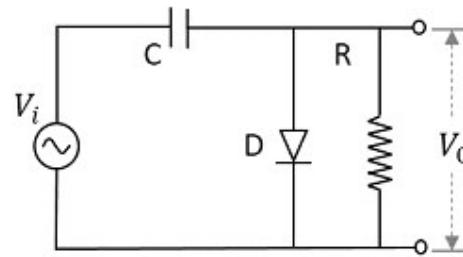


Fig 4. Negative Clamper Circuit

Observation waveform

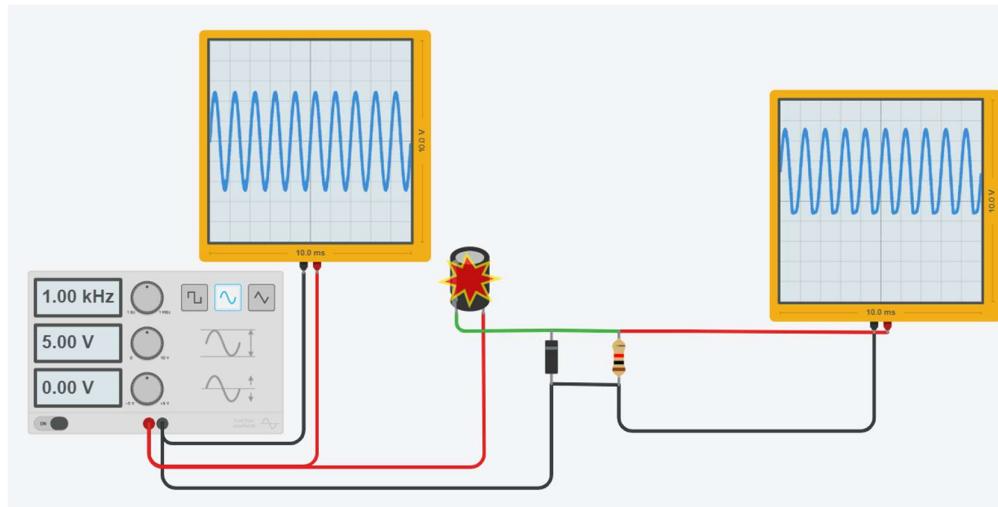

Positive Clamper

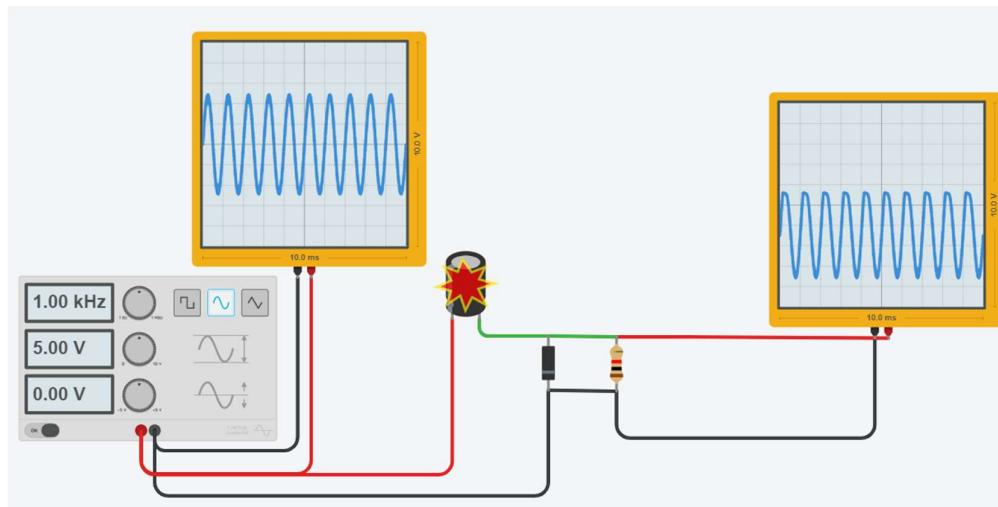

Negative Clamper



First Year (Semester I) B.Tech.

Conclusion

- This Experiment helped us study the waveforms generated by a clipper and clamper.
- This Experiment was performed by implementing the circuit and taking readings in an online simulation tool, TinkerCad.