



Shri Vile Parle Kelavani Mandal's

DWARKADAS J. SANGHVI COLLEGE OF ENGINEERING

(Autonomous College Affiliated to the University of Mumbai)

NAAC Accredited with "A" Grade (CGPA : 3.18)



First Year (Semester I) B.Tech.

Basic Electrical and Electronics Engineering

Experiment No. : 03

Superposition Theorem

Name : Ayush Jain

SAP No. : 60004200132

Date of performance : 20/3/2021

Signature of teacher-in-charge : _____




First Year (Semester I) B.Tech.

Aim:	To determine current and voltage value in a circuit using superposition theorem.
Apparatus :	Online simulation tools (Suggested Tinker cad)
Theoretical Analysis:	<div data-bbox="495 619 1299 997"></div> <p>Fig. 1(a) Current across 40ohm resistor</p> <p><u>Theoretical Calculations:</u> Current through 40ohm resistor</p>

First Year (Semester I) B.Tech.

Fig 1(a): Current across 40Ω resistor

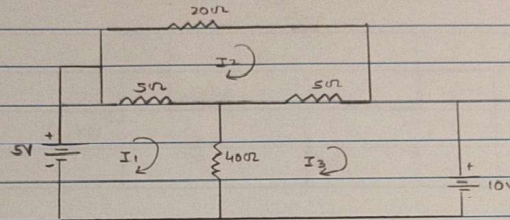

KVL in loop 1,

$$5 - 45I_1 + 5I_2 + 40I_3 = 0$$

$$\therefore -9I_1 + I_2 + 8I_3 = -1 \quad \text{--- (i)}$$

KVL in loop 2,

$$-30I_2 + 5I_1 + 5I_3 = 0$$

$$\therefore I_1 - 6I_2 + I_3 = 0 \quad \text{--- (2)}$$

KVL in loop 3,

$$-45I_3 + 40I_1 + 5I_2 - 10 = 0$$


$$8I_1 + I_2 - 9I_3 = 2 \quad \text{--- (3)}$$

On solving eq. (i), (ii) and (iii)

$$I_1 = -0.662 \text{ A}, \quad I_2 = -0.25 \text{ A}, \quad I_3 = -0.838 \text{ A}$$

$$\therefore I_{40\Omega} = I_3 - I_1 = 0.838 - 0.662 = 0.176 \text{ A}$$
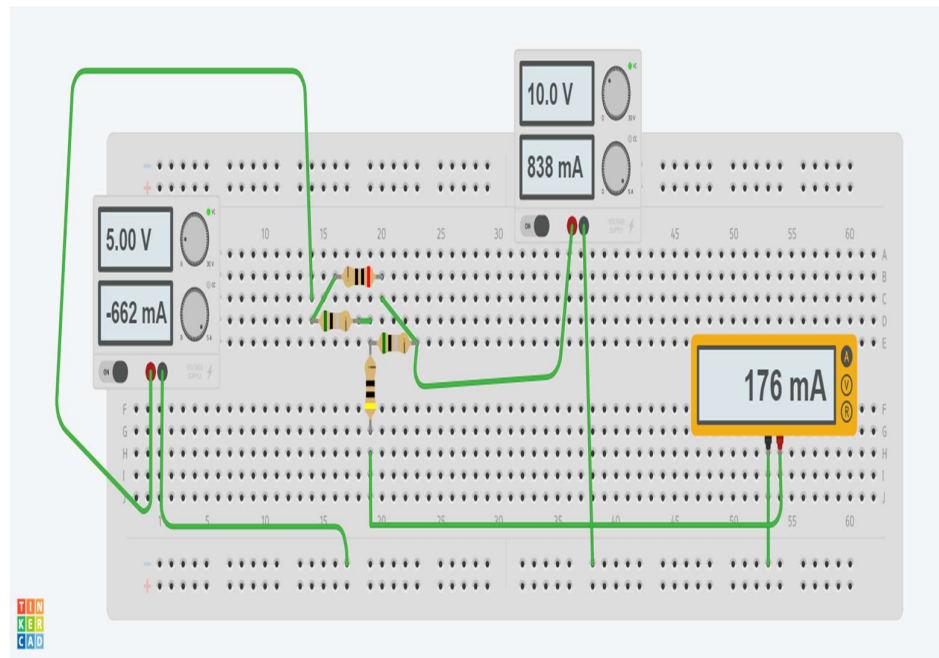
$$\therefore I_{40\Omega} = 176 \text{ mA}$$





First Year (Semester I) B.Tech.


Case 1: Consider 10V voltage source active.

KVL to loop 1,
 $-45I_1 + 5I_2 + 40I_3 = 0$
 $\therefore -9I_1 + I_2 + 8I_3 = 0 \quad (1)$

KVL to loop 2,
 $-30I_2 + 5I_1 + 5I_3 = 0$
 $\therefore I_1 - 6I_2 + I_3 = 0 \quad (2)$

KVL to loop 3,
 $-45I_3 + 40I_1 + 5I_2 - 10 = 0$
 $\therefore 8I_1 + I_2 - 9I_3 = 2 \quad (3)$

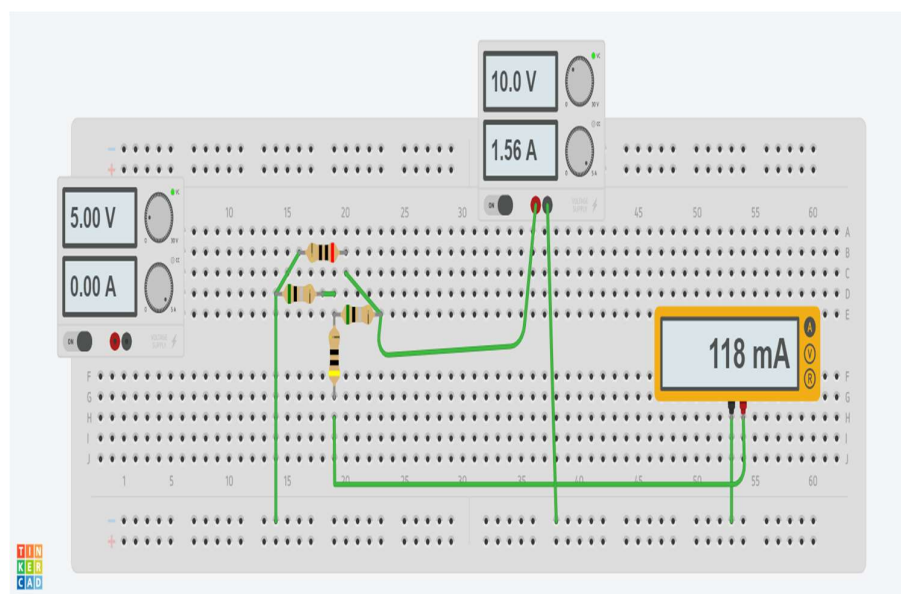On solving (i), (ii) and (3),
 $I_1 = -1.441 \text{ A}, I_2 = -0.5 \text{ A}, I_3 = -1.559 \text{ A}$
 $I_{40\Omega} = I_2 - I_1 = 1.559 - 1.441 = 0.118 \text{ A}$
 $\therefore I_{40\Omega} = 118 \text{ mA} \quad (4)$





First Year (Semester I) B.Tech.

Case 2 : 5V source is active.

KVL in loop 1,

$$-45I_1 + 5 + 5I_2 + 40I_3 = 0$$
$$-9I_1 + I_2 + 8I_3 = -1 \quad (1)$$


KVL in loop 2,

$$-30I_2 + 5I_1 + 5I_3 = 0$$
$$\therefore I_1 - 6I_2 + I_3 = 0 \quad (2)$$

KVL in loop 3,

$$-45I_3 + 40I_1 + 5I_2 = 0$$
$$8I_1 + I_2 - 9I_3 = 0 \quad (3)$$

Solving (1), (2) and (3),
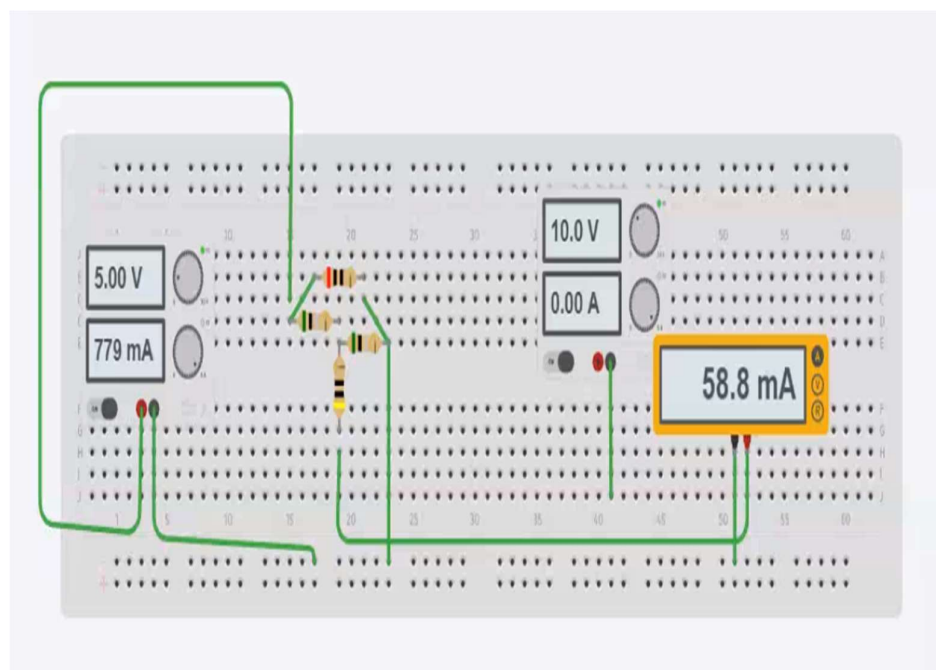
$$I_1 = 0.779 \text{ A}, \quad I_2 = 0.25 \text{ A}, \quad I_3 = 0.720 \text{ A}$$
$$I'_{40\Omega} = I_1 - I_3 = 0.059 \text{ A}$$
$$\therefore I'_{40\Omega} = 59 \text{ mA} \quad (\downarrow)$$




First Year (Semester I) B.Tech.

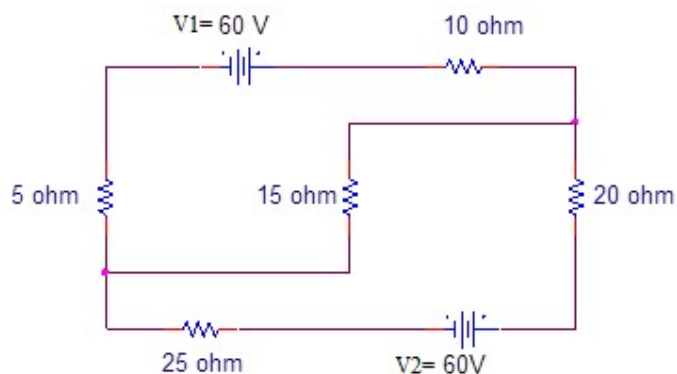



Fig. 1(b) Voltage across 15 ohm resistor

Theoretical Calculations:

Voltage across 15ohm resistor

First Year (Semester I) B.Tech.

Fig 1(b) Voltage across 15Ω resistor,

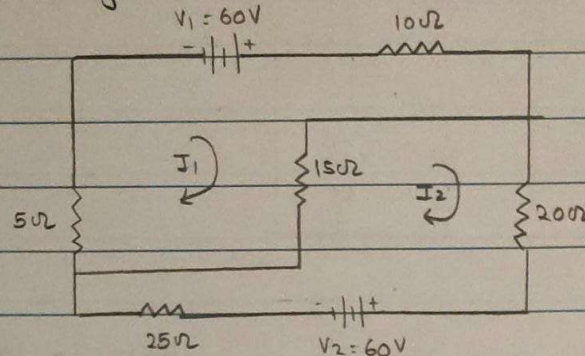

KVL in loop 1,

$$-30I_1 + 15I_2 + 60 = 0$$

$$\therefore -2I_1 + I_2 + 4 = 0$$

$$\therefore 2I_1 - I_2 = 4 \quad \text{--- (i)}$$

KVL in loop 2,

$$\therefore -60I_2 + 15I_1 - 60 = 0$$

$$\therefore -4I_2 + I_1 - 4 = 0$$

$$I_1 - 4I_2 = 4 \quad \text{--- (2)}$$


Solving (i) and (ii)

$$\therefore I_1 = 1.714 \text{ A}, \quad I_2 = -0.571 \text{ A}$$

$$\therefore I_{15\Omega} = i_1 - i_2 = 2.285 \text{ A}$$

$$\therefore V_{15\Omega} = I_{15\Omega} \cdot 15 = 34.3 \text{ V}$$
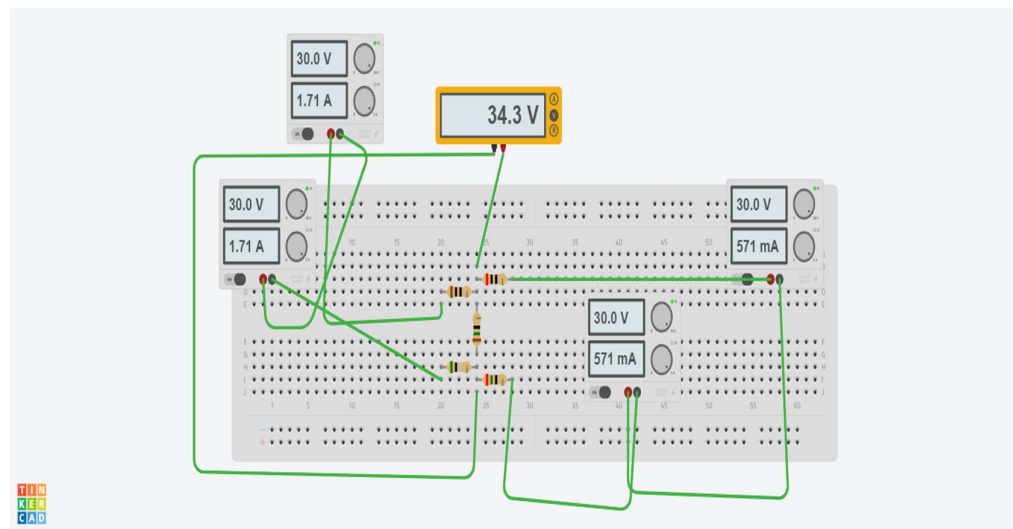
$$\therefore V_{15\Omega} = 34.3 \text{ V}$$





First Year (Semester I) B.Tech.

Consider 60 V marked V_2 as active.

KVL in loop 1,
 $-30I_1 + 15I_2 = 0$
 $-2I_1 + I_2 = 0 \quad \text{--- (1)}$


KVL in loop 2,
 $-60I_2 + 15I_1 = 60$
 $I_1 - 4I_2 = 4 \quad \text{--- (2)}$

\therefore On solving (1) and (2),
 $I_1 = -0.571 \text{ A} \quad , \quad I_2 = -1.1428 \text{ A}$

$\therefore I_{15\Omega} = I_2 - I_1 = 0.571 \text{ A}$

$\therefore V_{15\Omega} = I_{15\Omega} \times 15 = 0.571 \times 15$

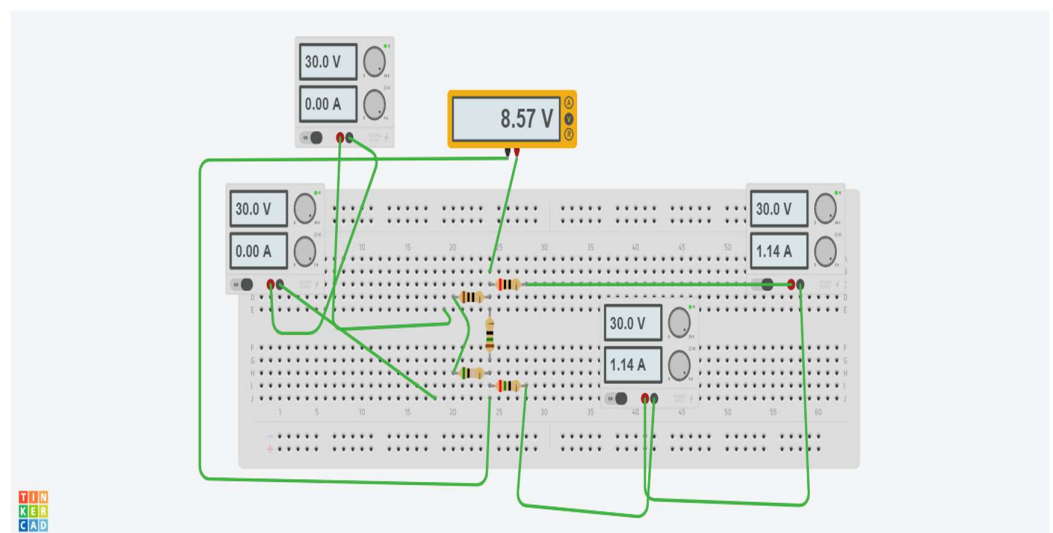
$\therefore V_{15\Omega} = 8.57 \text{ V}$





First Year (Semester I) B.Tech.

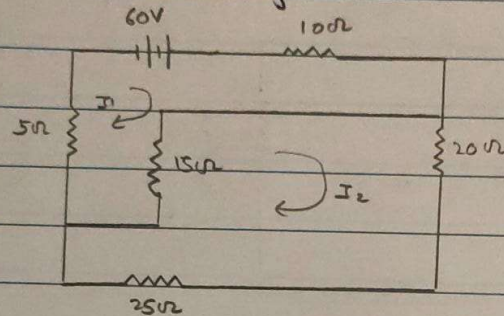Consider 60V voltage source marked V_1 as active.



KVL in loop 1,

$$-30I_1 + 15I_2 + 60 = 0$$

$$\therefore 2I_1 - I_2 = 4 \quad \text{--- (i)}$$

$$I_1 = 2.286 \text{ A}$$

$$I_2 = 0.571$$

$$\therefore I''_{15\Omega} = 2.286 - 0.571 = 1.715 \text{ A}$$


$$\therefore V''_{15\Omega} = 1.715 \times 15 = 25.7 \text{ V}$$

$$\therefore V''_{15\Omega} = 25.7 \text{ V}$$

KVL in loop 2

$$-60I_2 + 15I_1 = 0$$

$$\therefore I_1 - 4I_2 = 0$$

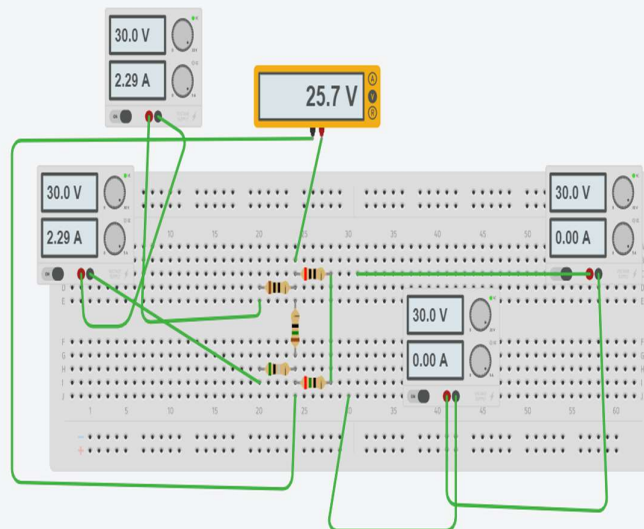



Shri Vile Parle Kelavani Mandal's

DWARKADAS J. SANGHVI COLLEGE OF ENGINEERING

(Autonomous College Affiliated to the University of Mumbai)

NAAC Accredited with "A" Grade (CGPA : 3.18)



First Year (Semester I) B.Tech.

	Active Voltage source	Theoretical values, $I_{40\Omega}$	Practical values, $I_{40\Omega}$
Observation Table	When 5V active	59 mA	58.8mA =59mA
	When 10V active	118mA	118mA

	Active Voltage source	Theoretical values, $V_{15\Omega}$	Practical values, $V_{15\Omega}$
Observation Table	When V1 active	25.7 V	25.7 V
	When V2 active	8.57 V	8.57 V

Conclusion:

- The Practical values have been attained by using online simulation tool Tinkercad.
- We used Superposition theorem to find the theoretical value of voltage and current.
- The theoretical and practical values are equal to each other.