

## **Virtual Lab**

### **Characteristics of Zener Diode (Expt. 04)**

**Name: Ayush Jain**

**SAP ID: 60004200132**

**Div: J1**

**Branch: Computer Engineering**

#### **Aim:**

To draw the static current-voltage (I-V) characteristics of a junction diode.

#### **Apparatus:**

Zener Diode, resistor, variable DC power supply, milliammeter, voltmeter, Rheostat and wire.


#### **Theory:**

A diode, in electronics, is a two terminal electronic component with an asymmetric transfer characteristics, with low resistance to current flow in one direction and high resistance to current flow in the other direction. A semi-conductor diode is the most common type diode, which is a piece of semi-conductor material with a p-n junction connected to two terminals.

A diode allow electric current to pass in forward direction and block current in reverse direction. The behaviour of a diode in a circuit is given by its I-V characteristics. The shape of the curve is determined by the transport of charge carriers through the depletion layer that exist at the p-n junction. When a p-n junction is first cretaed, diffusion of holes and electrons take place through the junction. As recombination proceeds, more ions are created at the junction and a built-in potential is developed at the depletion zone.

If a voltage of same polarity as that of built-in potential is applied across the junction, depletion zone acts as an insulator, preventing significant current flow through the junction. This is the reverse bias phenomenon.

### Diagram:

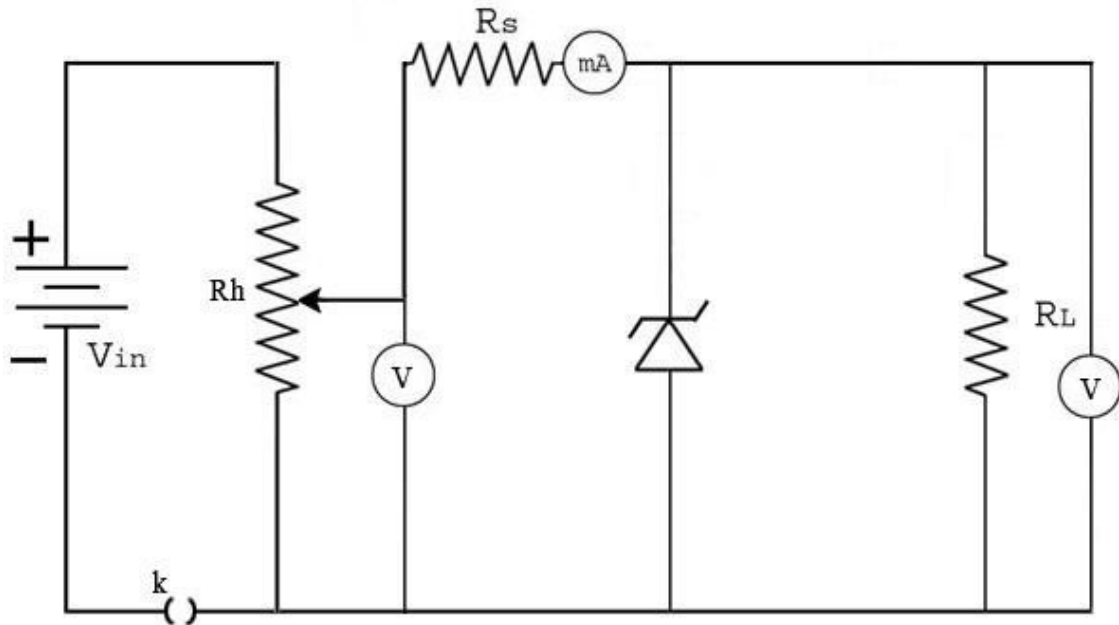

### Working Process:

- **Insert Key Button:** This is used to insert key on the switch connected with battery. This key is only activated when the connection is perfect.

**Choose Zener Diode:** This combo box is used to select different zener diodes having different zener voltage

**Series Resistance:** Value of the Series Resistance can be directly input here.

#### **Slider**

**Rheostat value:** Rheostat can be controlled by using this slider



**Load Resistance:** Value of load resistance can be set or change by using this slider



#### **Button**


**Reset Button:** To reset all the connections

- Using the circuit diagram, identify the connections in the given platform.
- Click one end node of the battery and drag to the next position, where we want to connect the wire.

## Observations:

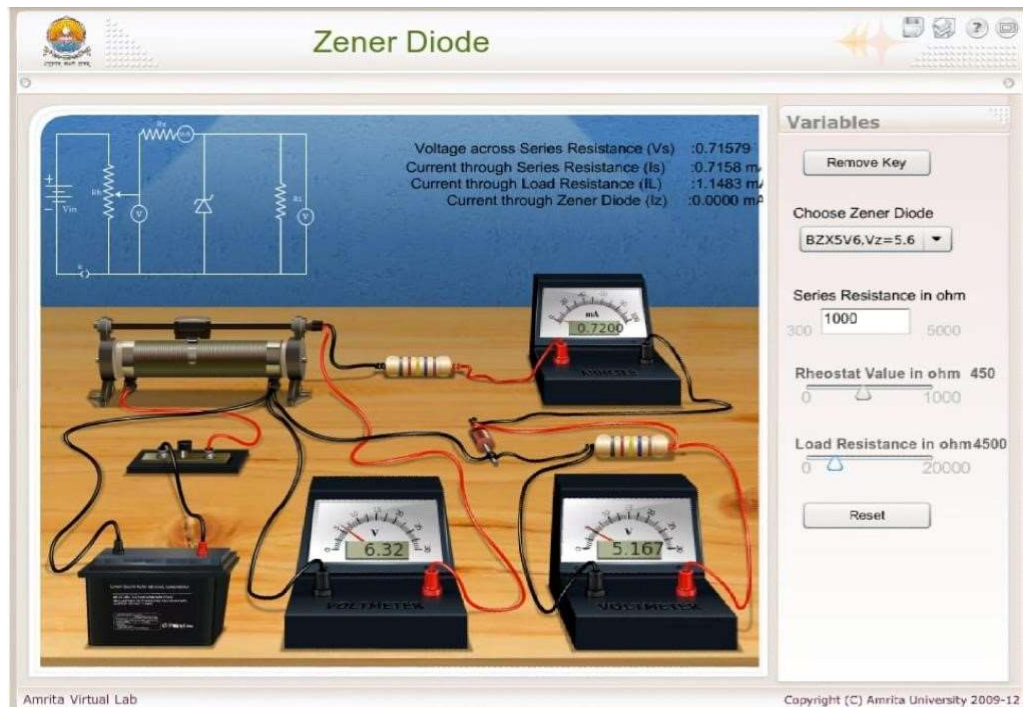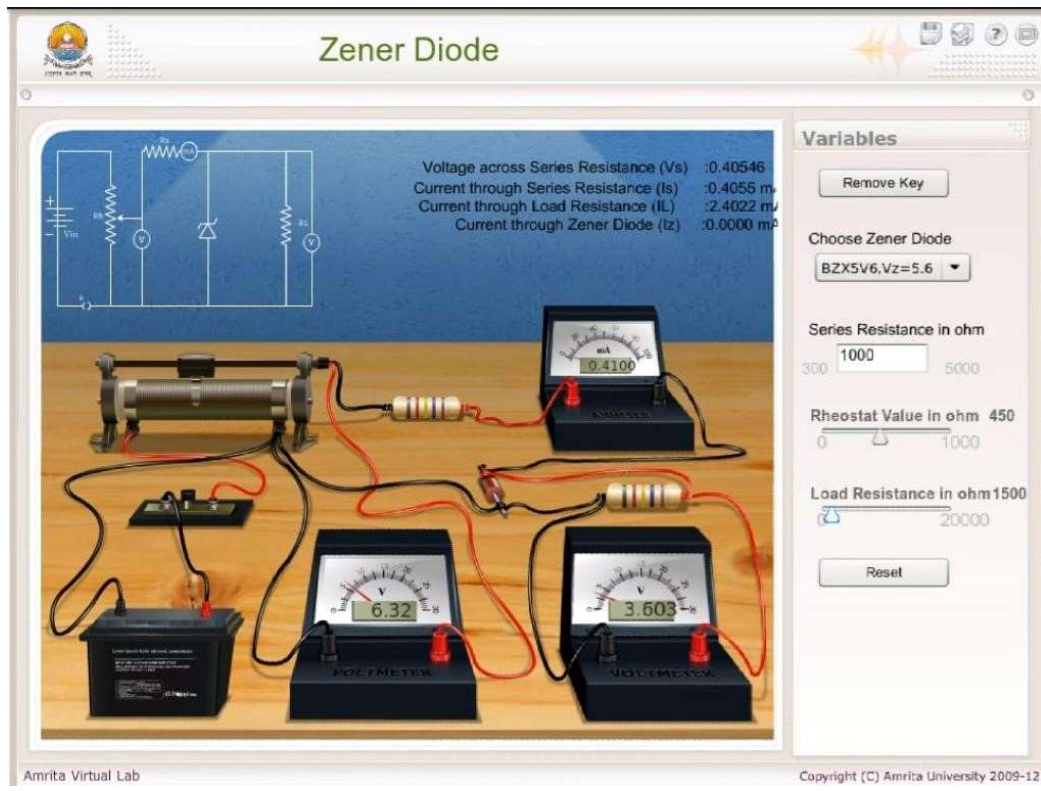

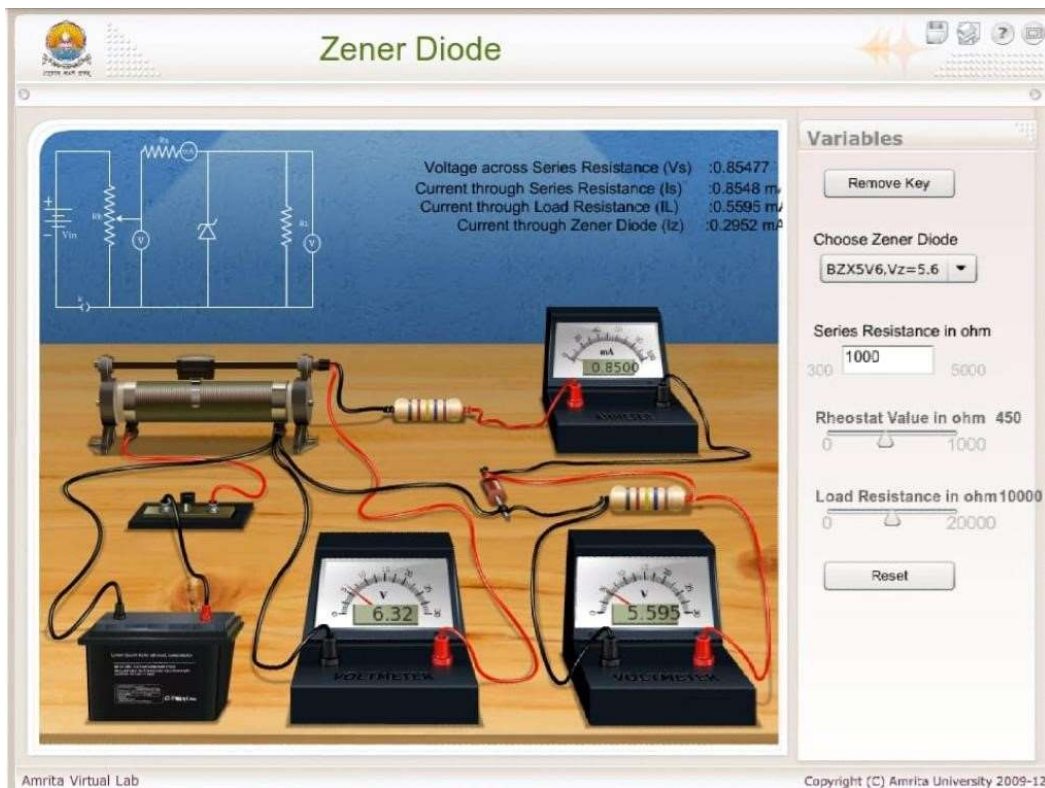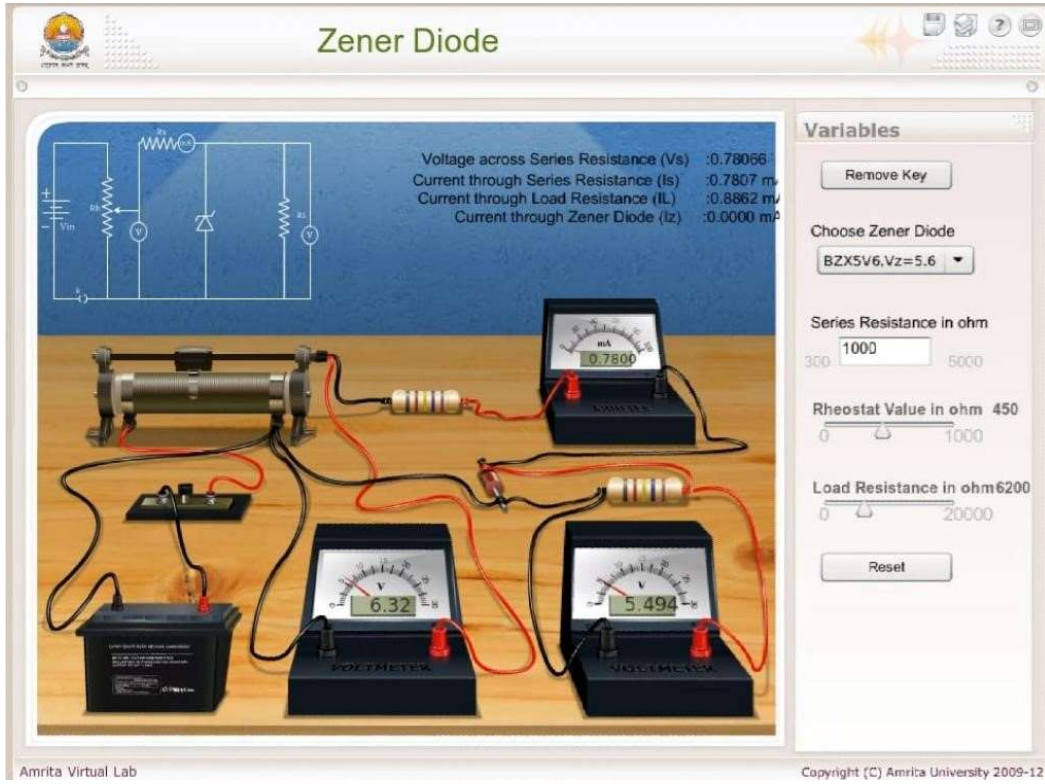

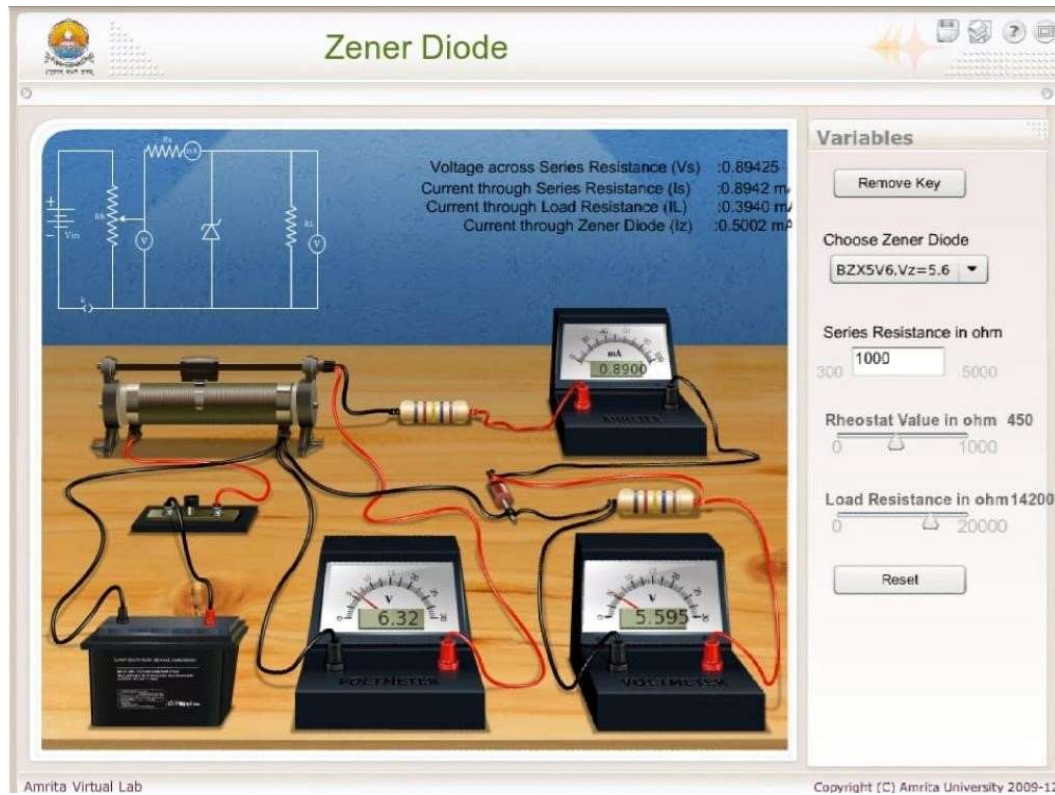

**Result:** Hence the properties and characteristics of a Zener diode are successfully studied.