



Shri Vile Parle Kelavani Mandal's

DWARKADAS J. SANGHVI COLLEGE OF ENGINEERING

(Autonomous College Affiliated to the University of Mumbai)

NAAC Accredited with "A" Grade (CGPA : 3.18)



First Year (Semester I) B.Tech.

Basic Electrical and Electronics Engineering

Experiment No. : 01

DC Circuit Analysis

Name : Ayush Jain

SAP No. : 60004200132

Date of performance : 6/3/2021

Signature of teacher-in-charge : _____



First Year (Semester I) B.Tech.

Aim:	To determine resistor, voltage and current value in a circuit.
Apparatus :	Online simulation tools (Tinkercad)
Theoretical Analysis:	<div data-bbox="568 567 1169 903"></div> <p style="text-align: right;">read</p> <p style="text-align: center;">Fig. 1(a) Resistor equivalent across X and Y</p> <p><u>Theoretical Calculations:</u></p> <p>Resistor equivalent across X and Y</p> <div data-bbox="454 1092 1364 1848"></div>



First Year (Semester I) B.Tech.



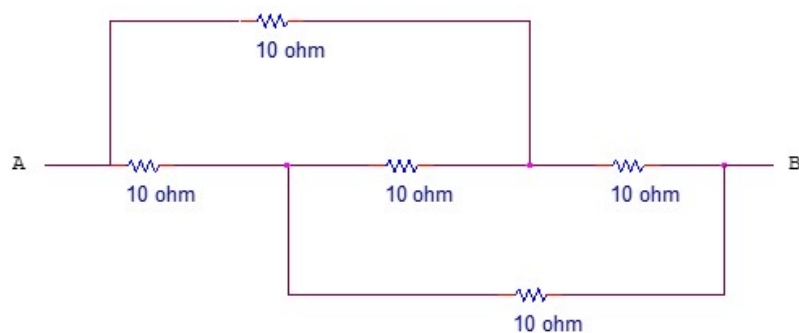


Fig. 1(b) Resistor equivalent across A and B

Theoretical Calculations:

Resistor equivalent across A and B

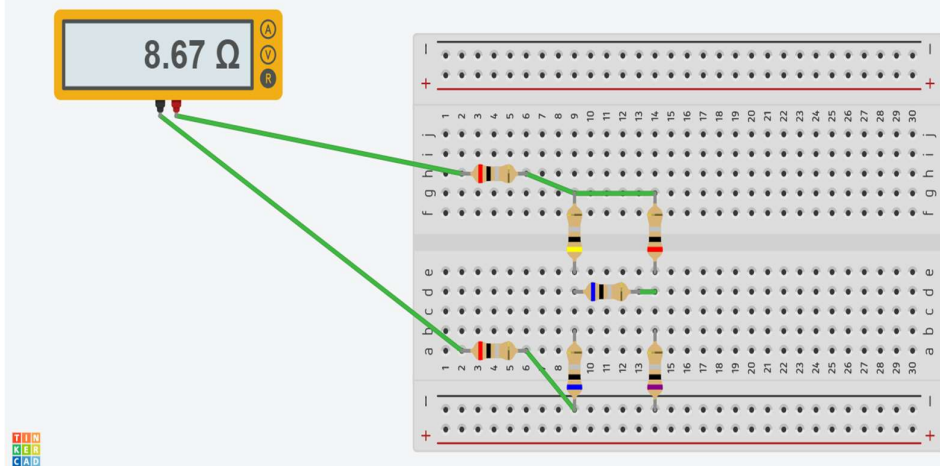

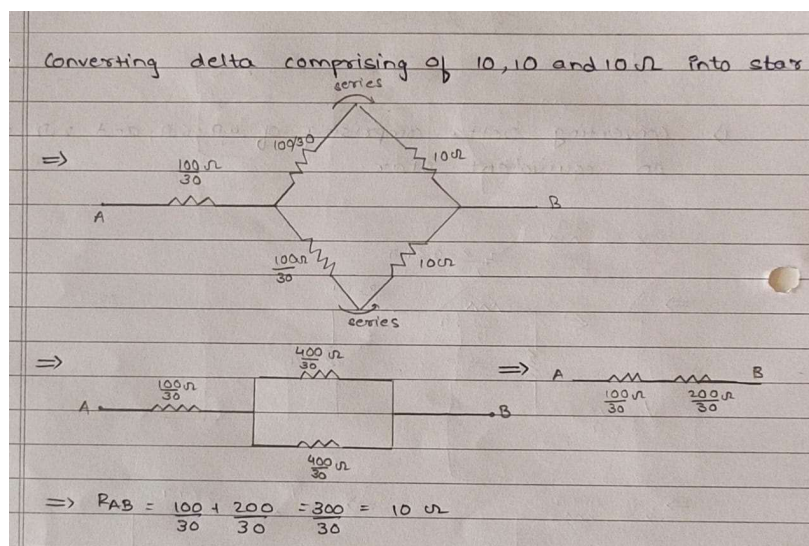

First Year (Semester I) B.Tech.

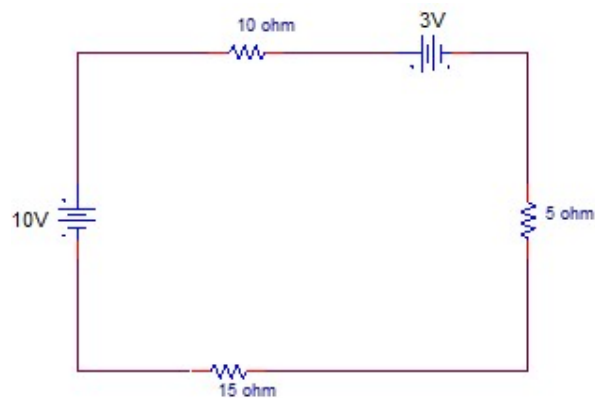
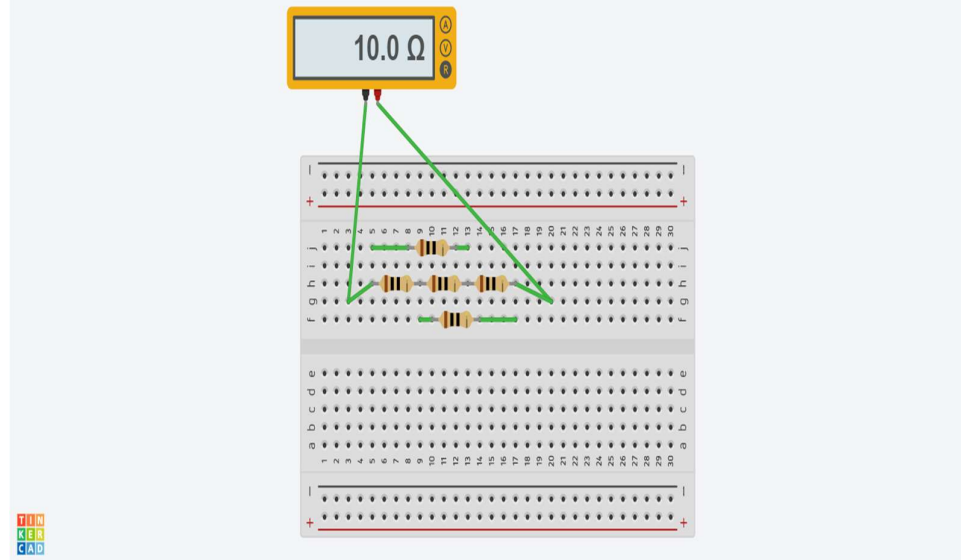


Fig. 1(c) Current in the circuit

Theoretical Calculations:



Current in the circuit

Applying KVL in loop,

$$10 - 10I - 3 - 5I - 15I = 0$$
$$-30I + 7 = 0$$
$$\therefore 30I = 7$$
$$I = \frac{7}{30} = 0.233A$$




First Year (Semester I) B.Tech.

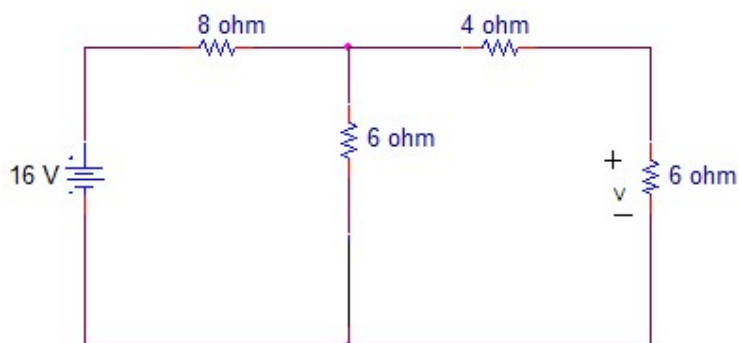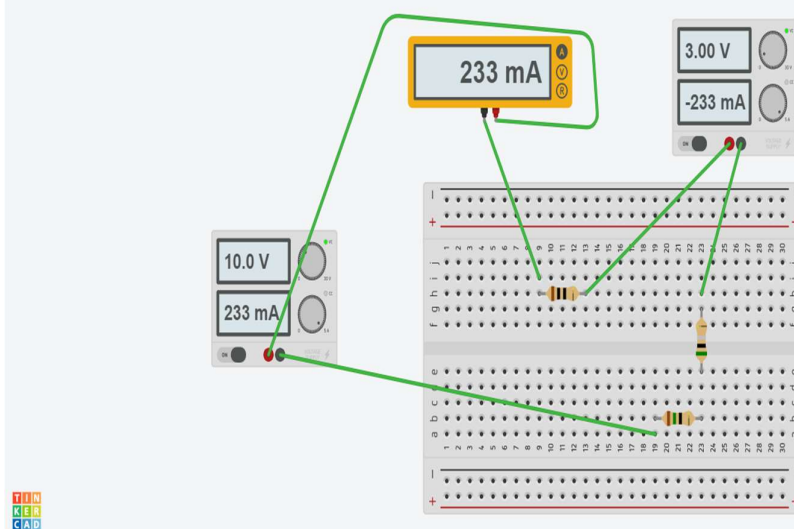


Theoretical Calculations:

Voltage across 6ohm

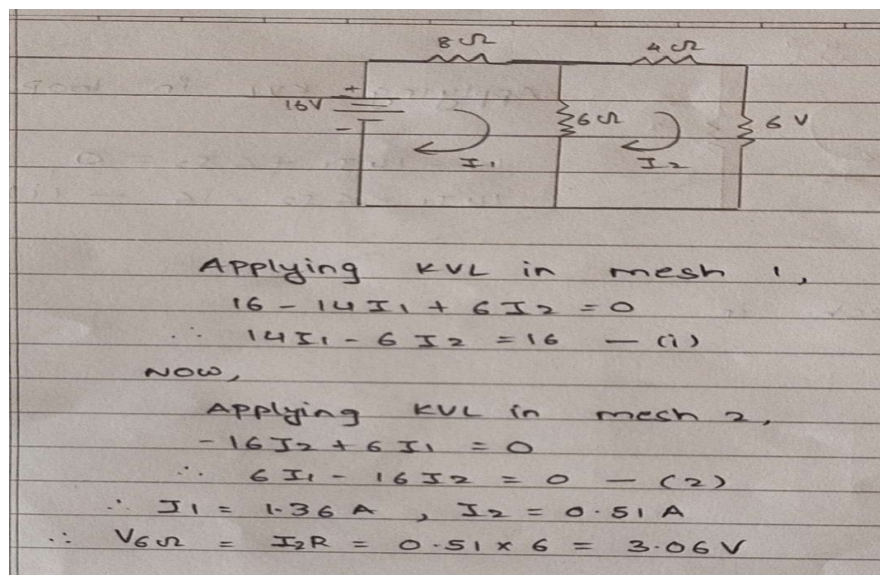



First Year (Semester I) B.Tech.

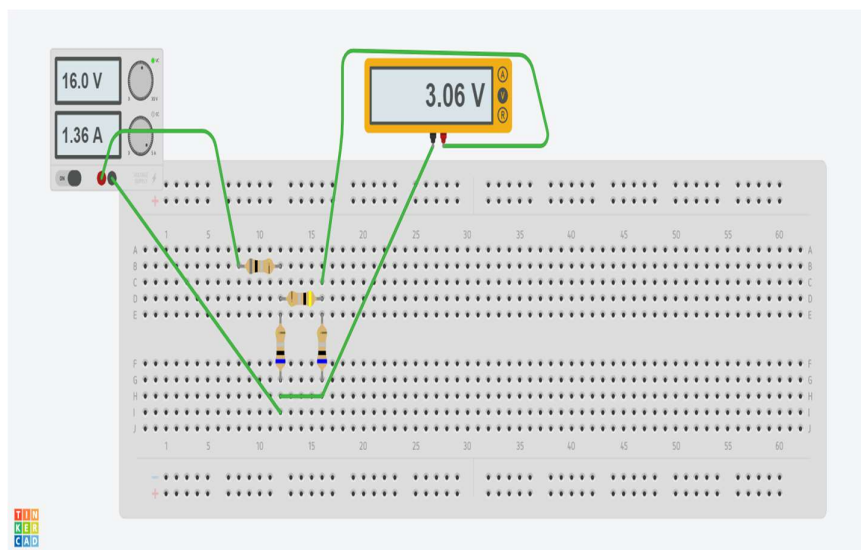

		Theoretical values	Practical values
Observation Table	Equivalent resistor R_{XY} (Fig 1.a)	8.67Ω	8.67Ω
	Equivalent resistor R_{AB} (Fig 1.b)	10Ω	10Ω
	Current in the circuit I (Fig 1.c)	0.233A	0.233A
	Voltage $V_{6\Omega}$ (Fig 1.d)	3.06V	3.06V

Conclusion:

1. We used Star-Delta transformation to simplify the circuit.
2. The practical values has been attained using an online simulator tool, Tinkercad
3. The theoretical values and practical values are equal to each other.