

Digital Electronics

Experiment 7

Name: Ayush Jain

SAP ID: 60004200132

Div.: B1

Branch: Computer Engineering

Aim:

To analyse the truth table and working of 1x4 De-Multiplexer by using 3-input NAND and 1-input NOT logic gate ICs and 4x1 Multiplexer by using 3-input AND, 3input OR, and 1-input NOT logic gate ICs.

Theory:

The function of a multiplexer is to select the input of any 'n' input lines and feed that to one output line. The function of a de-multiplexer is to inverse the function of the multiplexer and the shortcut forms of the multiplexer.


1) Multiplexer:

Multiplexer is a device that has multiple inputs and a single line output. The select lines determine which input is connected to the output, and also to increase the amount of data that can be sent over a network within certain time. It is also called a data selector.

4x1 Multiplexer

4x1 Multiplexer has four data inputs I_3 , I_2 , I_1 & I_0 , two selection lines S_1 & S_0 and one output Y . The block diagram of 4x1 Multiplexer is shown in the following figure. One of these 4 inputs will be connected to the output based on the combination of inputs present at these two selection lines. Truth table of 4x1 Multiplexer is shown below.


Block Diagram:

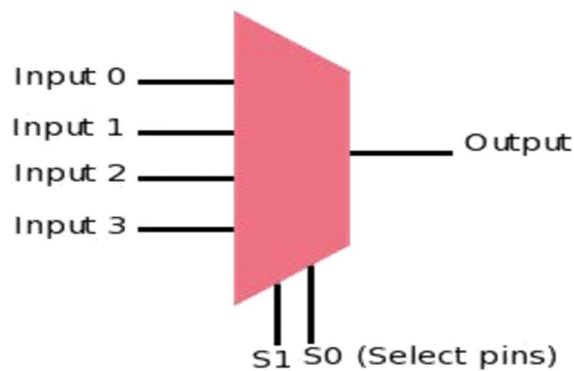

Truth Table:

Selection Lines		Output
S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Tinkercad:

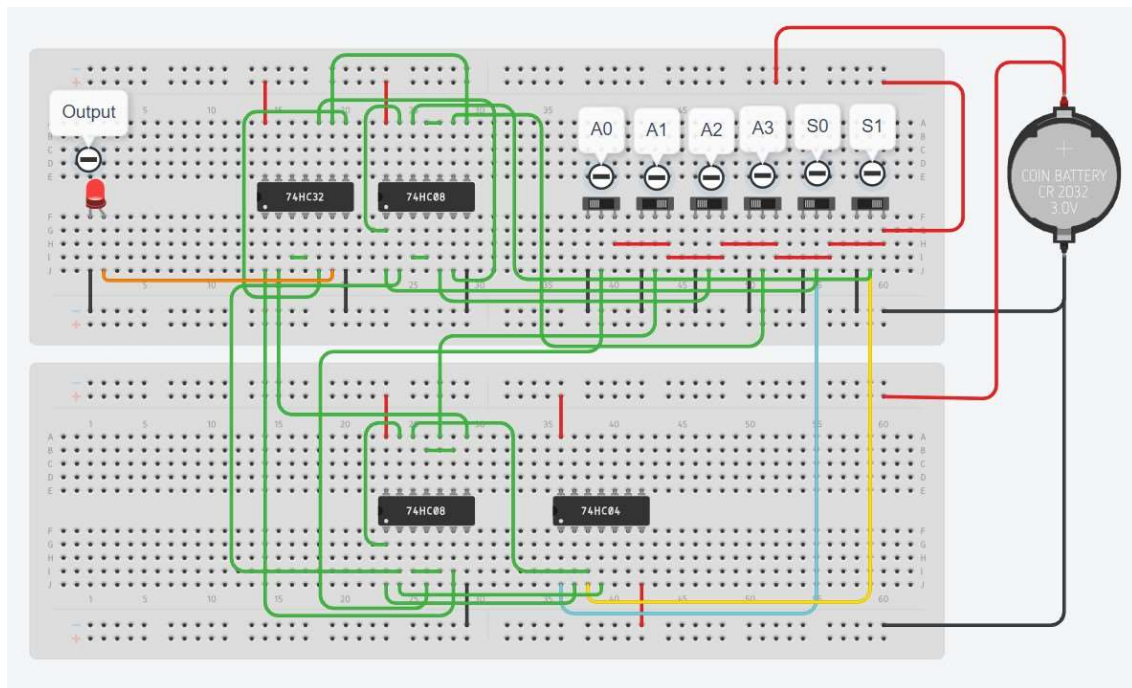

Multiplexer using AND, NOT, OR gates with inputs $S_0 = 0$, $S_1 = 1$ that activates the A1 input


2) De-multiplexer:

De-multiplexer is also a device with one input and multiple output lines. It is used to send a signal to one of the many devices. The main difference between a multiplexer and a de-multiplexer is that a multiplexer takes two or more signals and encodes them on a wire, whereas a de-multiplexer does reverse to what the multiplexer does.

1x4 De-multiplexer:

1x4 De-Multiplexer has one input I, two selection lines, S_1 & S_0 and four outputs Y_3 , Y_2 , Y_1 & Y_0 . The block diagram of 1x4 De-Multiplexer is shown in the following figure.


Block Diagram:

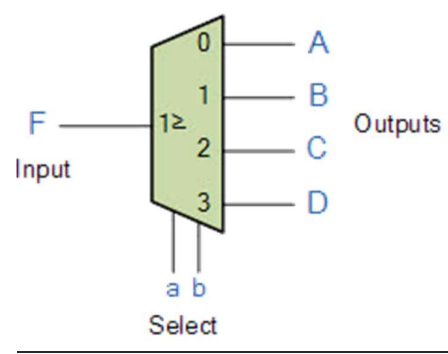

Truth Table:

Selection Inputs		Outputs			
S ₁	S ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

Tinkercad:

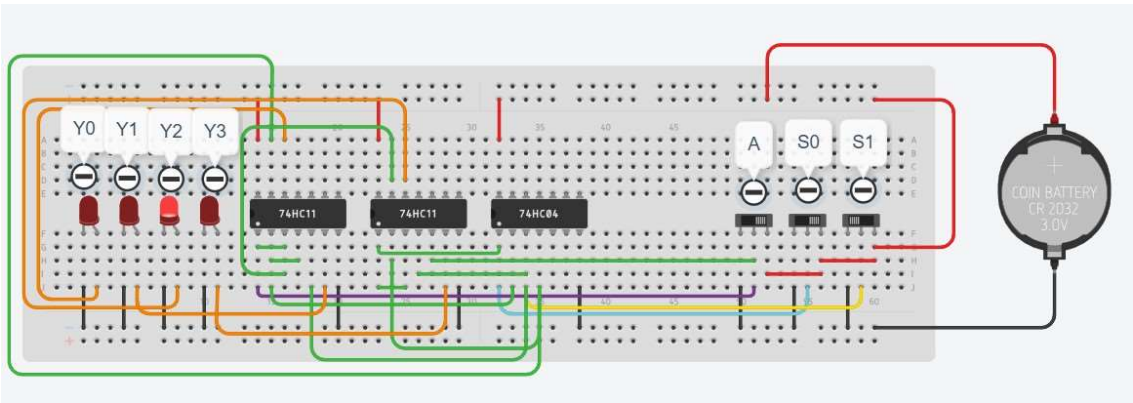

De-multiplexer using AND, NOT gates with inputs S0 = 1, S1 = 0