



Shri Vile Parle Kelavani Mandal's

DWARKADAS J. SANGHVI COLLEGE OF ENGINEERING

(Autonomous College Affiliated to the University of Mumbai)

NAAC Accredited with "A" Grade (CGPA : 3.18)



First Year (Semester I) B.Tech.

Basic Electrical and Electronics Engineering

Experiment No : 06

Rectifier Circuit



Name : Ayush Jain

SAP No. : 60004200132

Date of performance :10/04/2021

Signature of teacher-in-charge : _____

**First Year (Semester I) B.Tech.**

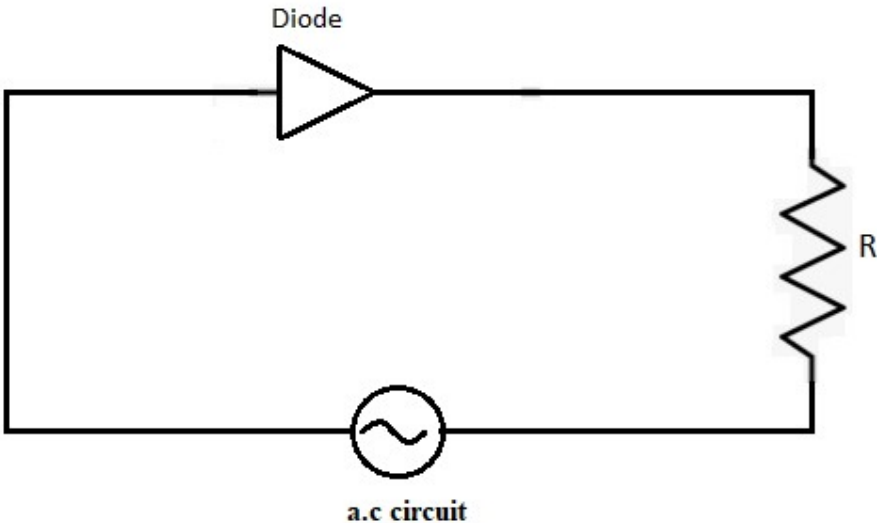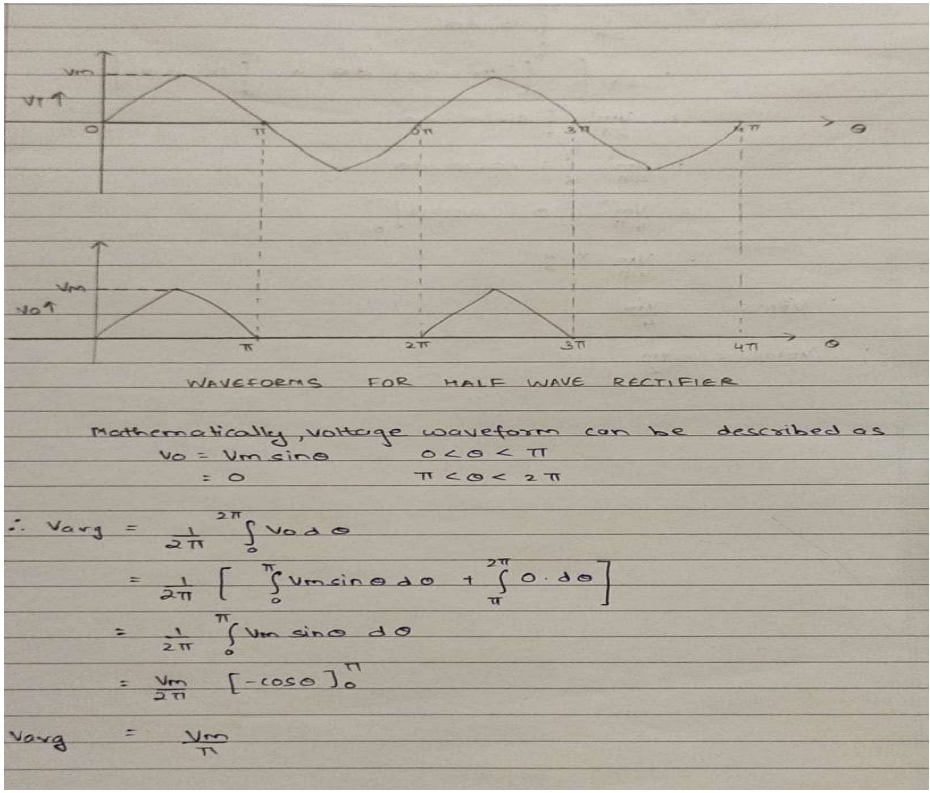
Aim:	To design Half wave and full wave rectifier.
Apparatus:	Online simulation tools (Suggested Tinkercad)
Theoretical Analysis:	<p><u>Half Wave Rectifier</u></p> <p><u>Circuit Diagram</u></p>  <p>Fig LCR series resonance</p> <p><u>Theoretical Calculations:</u></p> <p>RMS and Average Value of a voltage (derivation)</p>  <p>Mathematically, voltage waveform can be described as</p> $V_o = V_m \sin \theta \quad 0 < \theta < \pi$ $= 0 \quad \pi < \theta < 2\pi$ $\therefore V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V_o d\theta$ $= \frac{1}{2\pi} \left[\int_0^{\pi} V_m \sin \theta d\theta + \int_{\pi}^{2\pi} 0 d\theta \right]$ $= \frac{1}{2\pi} \int_0^{\pi} V_m \sin \theta d\theta$ $= \frac{V_m}{2\pi} [-\cos \theta]_0^{\pi}$ $V_{avg} = \frac{V_m}{\pi}$



First Year (Semester I) B.Tech.

$$\begin{aligned}(V_{RMS})^2 &= \frac{1}{2\pi} \int_0^{2\pi} V_o^2 d\theta \\&= \frac{1}{2\pi} \left[\int_0^{\pi} (V_m \sin\theta)^2 d\theta + \int_{\pi}^{2\pi} 0 \cdot d\theta \right] \\&= \frac{V_m^2}{2\pi} \int_0^{\pi} \sin^2\theta \cdot d\theta \\&= \frac{V_m^2}{2\pi} \int_0^{\pi} \frac{1 - \cos 2\theta}{2} \cdot d\theta \\&= \frac{V_m^2}{4\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{\pi} \\&= \frac{V_m^2}{4\pi} \times \pi \\V_{RMS}^2 &= \frac{V_m^2}{4} \\V_{RMS} &= \frac{V_m}{2}\end{aligned}$$


Observation waveform

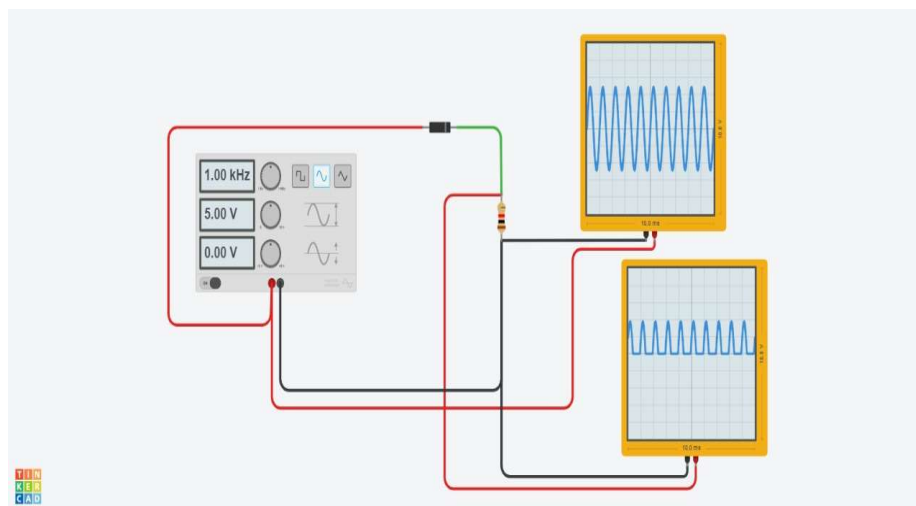

First Year (Semester I) B.Tech.


Full wave rectifier

Bridge Rectifier

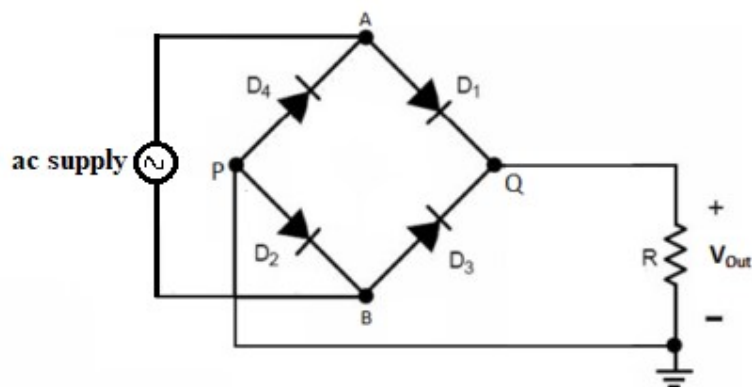

Theoretical Calculations:

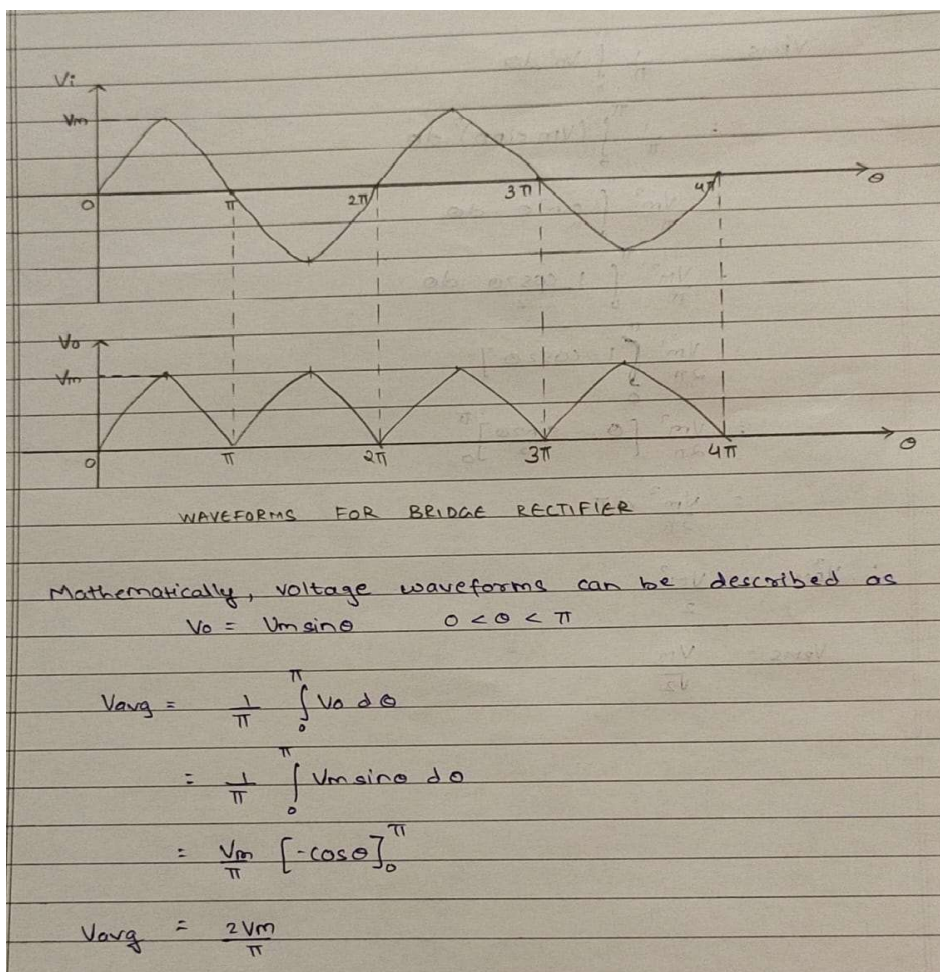RMS and Average Value of a voltage (derivation)






First Year (Semester I) B.Tech.

$$\begin{aligned} V_{RMS}^2 &= \frac{1}{\pi} \int_0^{\pi} V_o^2 d\theta \\ &= \frac{1}{\pi} \int_0^{\pi} (V_m \sin\theta)^2 d\theta \\ &= \frac{V_m^2}{\pi} \int_0^{\pi} \sin^2\theta \cdot d\theta \\ &= \frac{V_m^2}{\pi} \int_0^{\pi} \frac{1 - \cos 2\theta}{2} d\theta \\ &= \frac{V_m^2}{2\pi} \int_0^{\pi} [1 - \cos 2\theta] \\ &= \frac{V_m^2}{2\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{\pi} \\ &= \frac{V_m^2}{2\pi} \times \pi \\ \therefore V_{RMS}^2 &= \frac{V_m^2}{2} \\ \therefore V_{RMS} &= \frac{V_m}{\sqrt{2}} \end{aligned}$$

Observation waveform

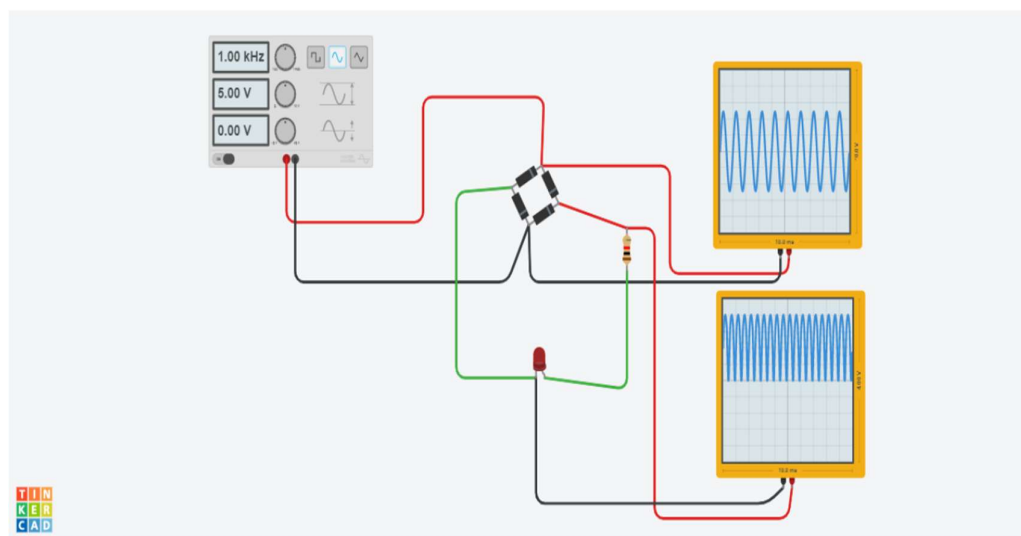



First Year (Semester I) B.Tech.

Conclusion:

- The circuits are made using an online simulation tool, Tinkercad
- This experiment helped us study the waveforms generated by a half wave and full wave (bridge) rectifier by implementing the circuit and making measurements using an oscilloscope.