

Digital Electronics

Experiment 1

Name: Ayush Jain

SAP ID: 60004200132

Div: B1


Branch: Computer Engineering

Aim:

Verification and interpretation of truth table for AND, OR, NOT, NAND, NOR, Ex-OR, Ex-NOR gates.

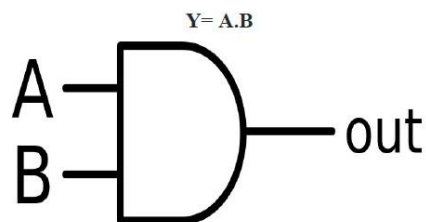1. AND Gate

Theory: The AND gate is an electronic circuit that gives a high output (1) only if all its inputs are high. A dot (.) is used to show the AND operation i.e. $A.B$ or can be written as AB



Output:


Verification of truth table for AND gate



TRUTH TABLE					Print
Serial No.	A	B	Output	Remarks	
1	1	1	1	Correct	
2	1	0	0	Correct	
3	0	1	0	Correct	
4	0	0	0	Correct	

Reset

Tinkercad:

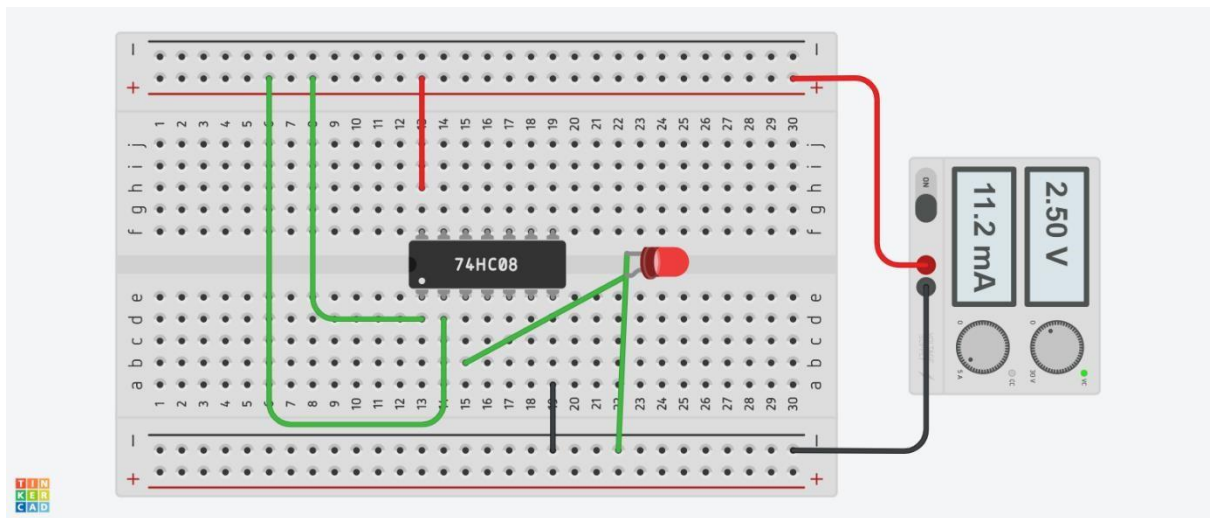


AND gate for inputs 1 and 1

2. OR Gate


Theory: The OR gate is an electronic circuit that gives a high output (1) if one or more of its inputs are high. A plus (+) is used to show the OR operation.

$$Y=A+B$$

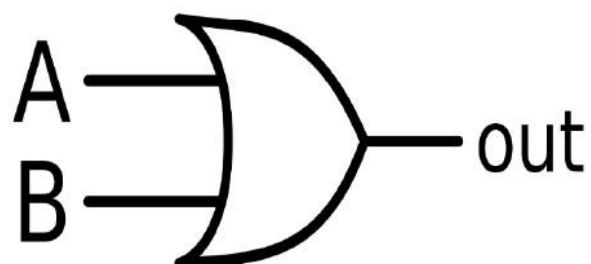

Output:


Verification of truth table for OR gate

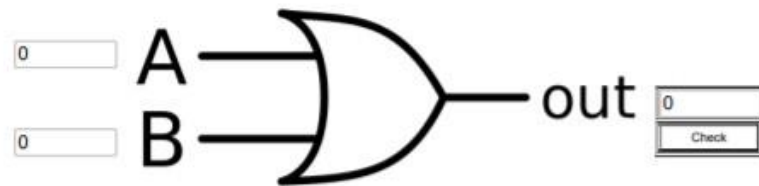

TRUTH TABLE				Print
Serial No.	A	B	Output	Remarks
1	1	1	1	Correct
2	1	0	1	Correct
3	0	1	1	Correct
4	0	0	0	Correct

Reset

Tinkercad:

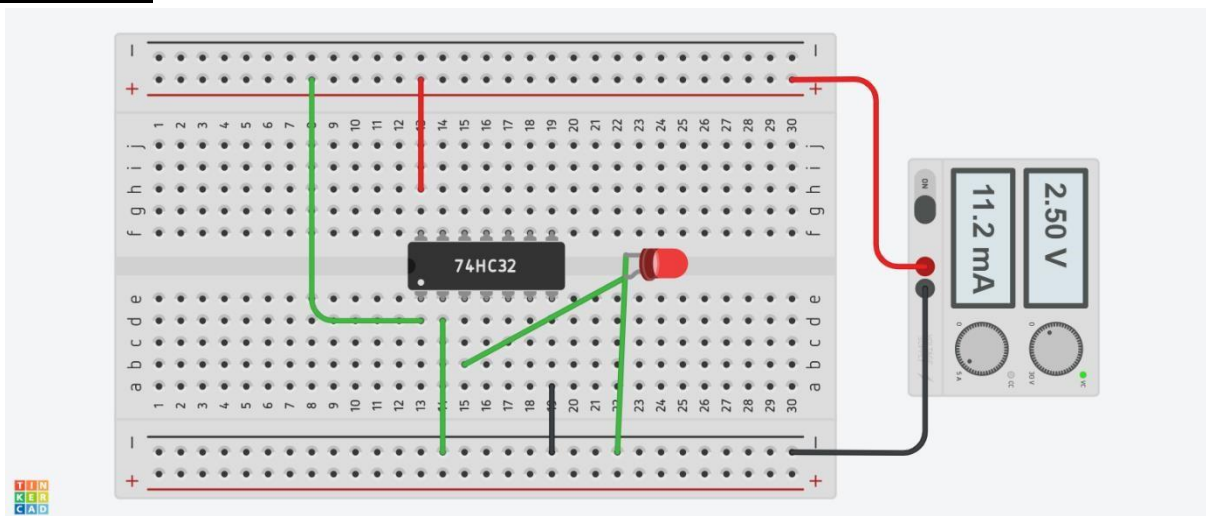


OR GATE for inputs 1 and 0

3.

NOT Gate


Theory: The NOT gate is an electronic circuit that produces an inverted version of the input at its output. It is also known as an inverter. If the input variable is A, the inverted output is known as NOT A. This is also shown as A' or A with a bar over the top, as shown at the outputs.

$$Y = A'$$

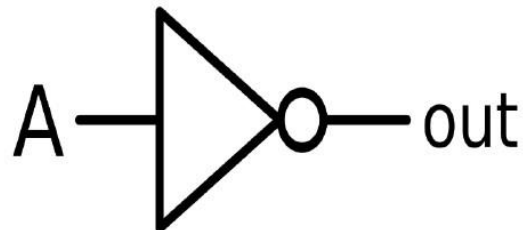

Output:


Verification of truth table for NOT gate

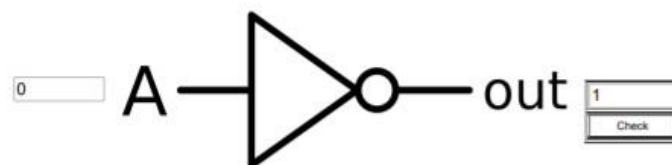

Reset

TRUTH TABLE				Print
Serial No.	A	Output	Remarks	
1	1	0	Correct	
2	0	1	Correct	

Tinkercad:

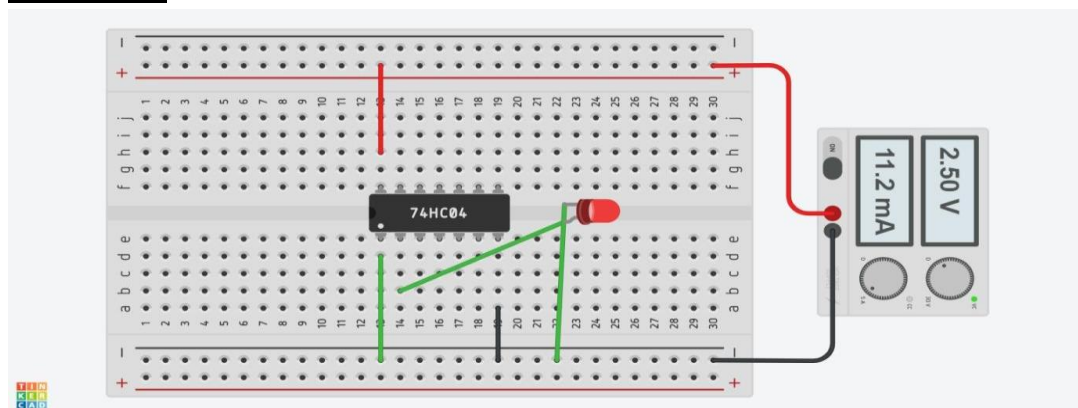


NOT Gate for input 0

4.

NAND gate


Theory: This is a NOT-AND gate which is equal to an AND gate followed by a NOT gate. The outputs of all NAND gates are high if any of the inputs are low. The symbol is an AND gate with a small circle on the output. The small circle represents inversion.

$$Y = (A.B)'$$

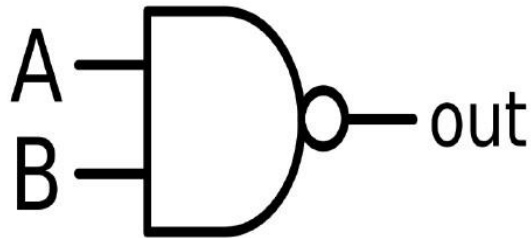

Output:

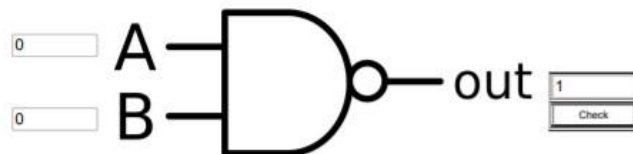
Verification of truth table for NAND gate



TRUTH TABLE				Print
Serial No.	A	B	Output	Remarks
1	1	1	0	Correct
2	1	0	1	Correct
3	0	1	1	Correct
4	0	0	1	Correct

Reset

Tinkercad:

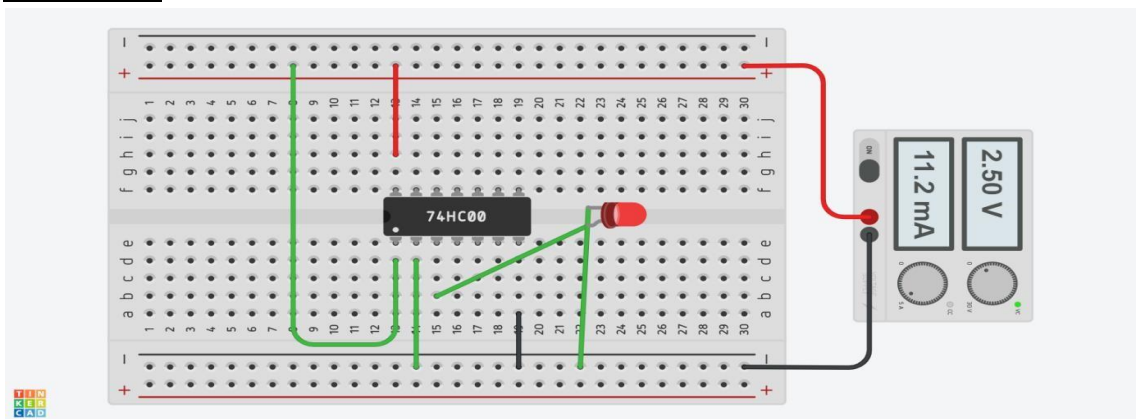


NAND Gate for inputs 1 and 0

5.

NOR gate


Theory: This is a NOT-OR gate which is equal to an OR gate followed by a NOT gate. The outputs of all NOR gates are low if any of the inputs are high. The symbol is an OR gate with a small circle on the output. The small circle represents inversion.

$$Y = (A+B)'$$

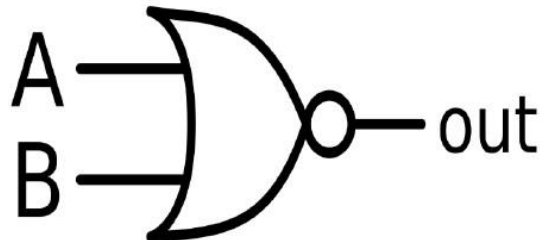

Output:


Verification of truth table for NOR gate

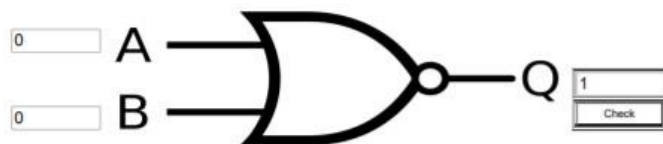

TRUTH TABLE					Print
Serial No.	A	B	Output	Remarks	
1	1	1	0	Correct	
2	1	0	0	Correct	
3	0	1	0	Correct	
4	0	0	1	Correct	

Reset

Tinkercad:

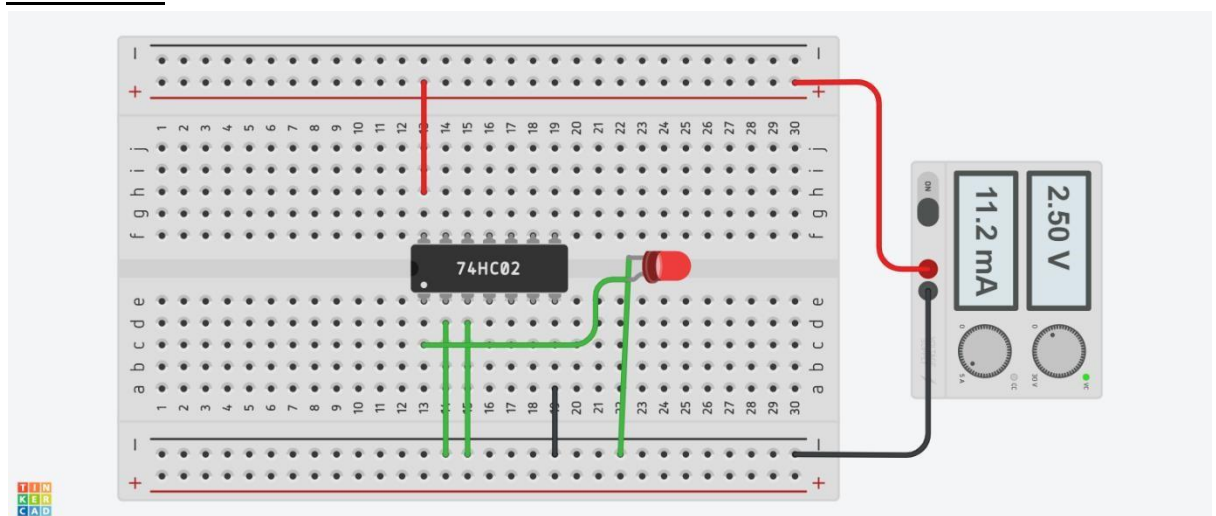


NOR gate for input 0 and 0

6.

EX-OR gate


Theory: The 'Exclusive-OR' gate is a circuit which will give a high output if either, but not both of its two inputs are high. An encircled plus sign (\oplus) is used to show the Ex-OR operation. Ex-OR gate is created from AND, NAND and OR gates. The output is high only when both the inputs are different.

$$Y = A \oplus B$$

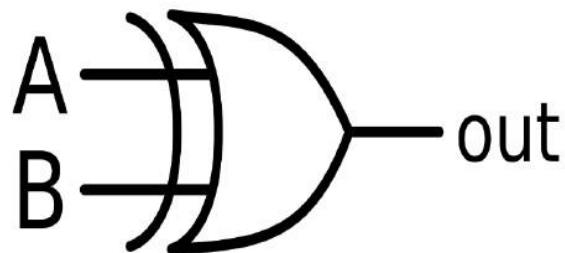

Output:


Verification of truth table for XOR gate

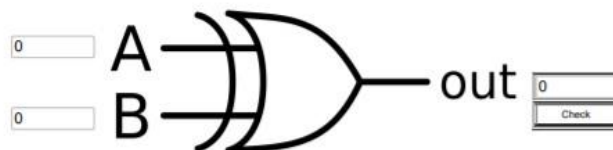

TRUTH TABLE					Print
Serial No.	A	B	Output	Remarks	
1	1	1	0	Correct	
2	1	0	1	Correct	
3	0	1	1	Correct	
4	0	0	0	Correct	

Reset

Tinkercad:

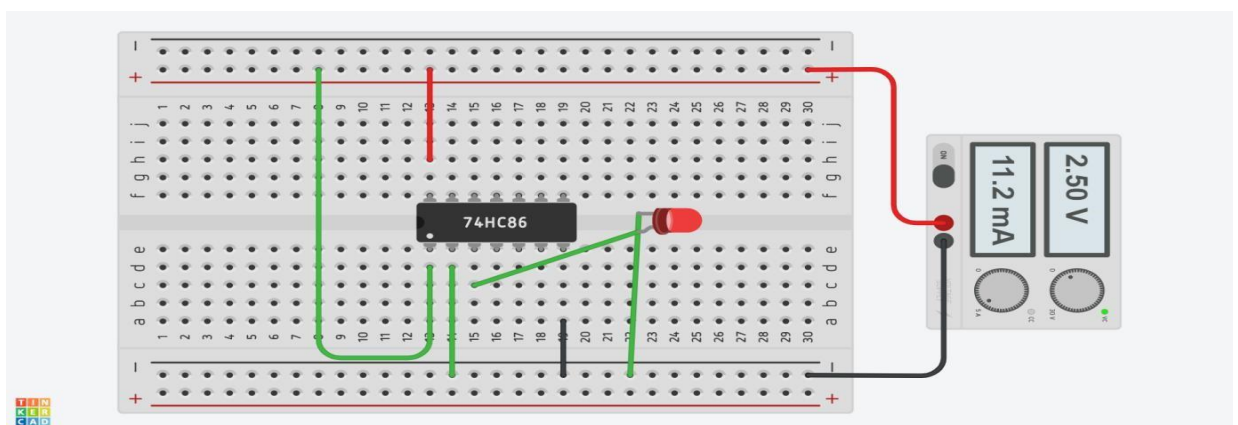

XOR gate for inputs 1 and 0

7.