



28/05/2021


SAP ID - 60004260132
Name - AYUSH JAIN
Div - J1

MAEER's MIT

BCE

Q. 1

→ (a)

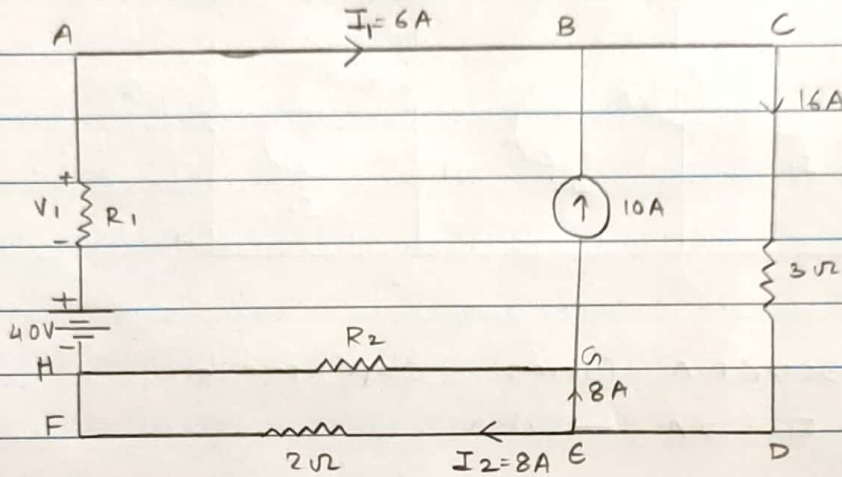

Applying KCL at B,

$$I_1 + 10 - 16 = 0$$

$$I_1 = 6A$$

Now,

~~Applying KVL in ABCDEFA,~~

$$40 - 6R_1 - 16(3)$$

Applying KCL at point E,

$$I_2 + 8 = 16$$

$$I_2 = 8A$$

Applying KVL in loop ABCDEFA,

$$40 + V_1 - 16 \times 3 - 2(8) = 0$$

$$40 + V_1 - 48 - 16 = 0$$


$$V_1 = 48 + 16 - 40$$

$$V_1 = 24V$$



Q. 1

→ b)

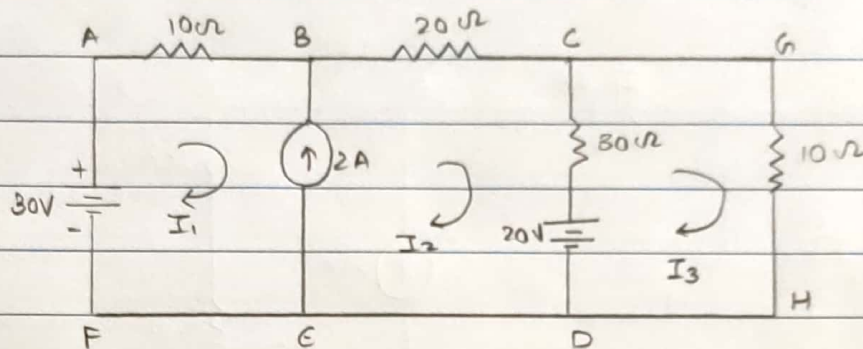

Loop ABCDEFA forms supermesh.

$$\therefore I_2 - I_1 = 2A \quad \text{--- (1)}$$

Mesh equation for CDEHC,

$$-40I_3 + 30I_2 + 20 = 0$$

$$\therefore 30I_2 - 40I_3 = -20 \quad \text{--- (2)}$$

Supermesh equation for ABCDEFA,

$$-10I_1 - 50I_2 + 30I_3 - 20 + 30 = 0$$

$$\therefore -10I_1 - 50I_2 + 30I_3 = -10 \quad \text{--- (3)}$$

Solving (1), (2) and (3) equation we get,

$$I_1 = -0.8A$$

$$I_2 = 1.2A$$


$$I_3 = 1.4A$$




Q. 2

→ a)

Delta to star transformation

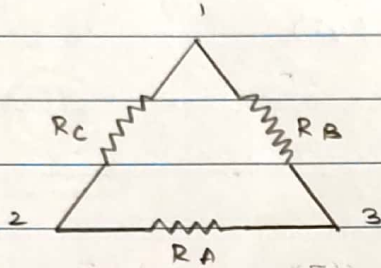

Delta

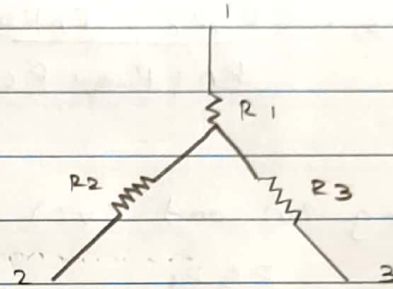

Star

The resistance between terminals 1 and 2 in delta transformation is : $\frac{R_C(R_A + R_B)}{R_A + R_B + R_C}$... (i)

Resistance between terminal (1) and (2) in star transformation, : $R_1 + R_2$... (ii)

Since, two networks are electrically equivalent

$$R_1 + R_2 = \frac{R_C(R_A + R_B)}{R_A + R_B + R_C} \dots (iii)$$

Similarly,

$$R_2 + R_3 = \frac{R_A(R_B + R_C)}{R_A + R_B + R_C} \dots (iv)$$

$$R_3 + R_1 = \frac{R_B(R_A + R_C)}{R_A + R_B + R_C} \dots (v)$$



Subtracting (iii) and (iv)

$$R_1 - R_3 = \frac{R_B R_C}{R_A + R_B + R_C} \dots (vi)$$

Adding (v) and (vi)

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$$

Similarly,

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$

Now, For star to delta transformation,

Multiplying $R_1 R_2$,

$$R_1 R_2 = \frac{R_A R_B R_C^2}{(R_A + R_B + R_C)^2} \dots (vii)$$

multiplying $R_2 R_3$,

$$R_2 R_3 = \frac{R_A^2 R_B R_C}{(R_A + R_B + R_C)^2} \dots (viii)$$

multiplying $R_3 R_1$,

$$R_3 R_1 = \frac{R_A R_B^2 R_C}{(R_A + R_B + R_C)^2} \dots (ix)$$



Adding (vii), (viii) and (ix),

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_A R_B R_C (R_A + R_B + R_C)}{(R_A + R_B + R_C)^2}$$

$$= \frac{R_A R_B R_C}{R_A + R_B + R_C}$$


$$= R_A R_1 = R_B R_2 = R_C R_3$$

$$\text{Hence, } R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Q. 2
→ b)

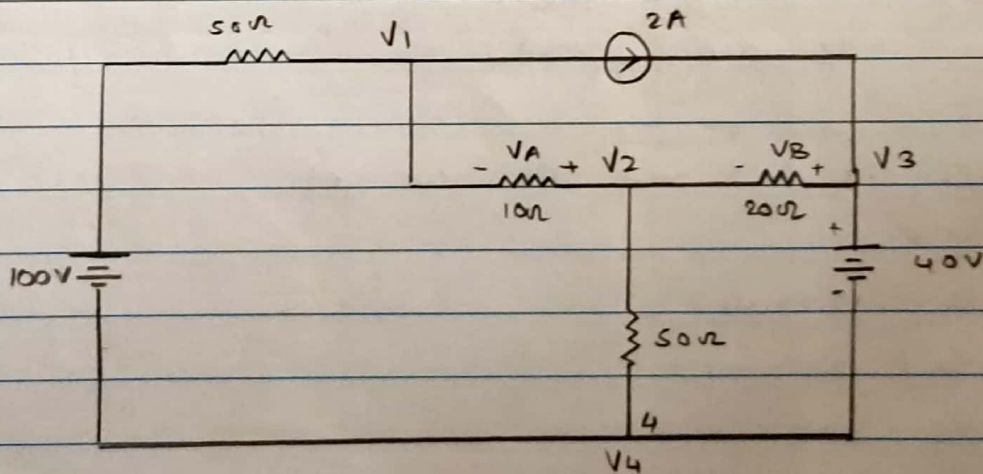

V_1, V_2, V_3, V_4 are nodes where $V_4 = 0V$



Applying KCL at node 1

$$\frac{V_1 - 100}{50} + \frac{V_1 - V_2}{10} + 2 = 0$$

$$\therefore 0.12 V_1 - 0.1 V_2 = 0 \quad \text{--- (1)}$$

Applying KCL at node 2,

$$\frac{V_2 - V_1}{10} + \frac{V_2}{50} + \frac{V_2 - V_3}{20} = 0$$

$$\therefore -0.1 V_1 + 0.17 V_2 - 0.05 V_3 = 0 \quad \text{--- (2)}$$

Since node 3 is directly connected to voltage source of 40V.

$$\therefore V_3 = 40V \quad \text{--- (3)}$$

Solving (i), (ii) and (iii) we get

$$V_1 = 19.230V$$

$$V_2 = 23.07V$$


$$V_3 = 40V$$

$$\therefore V_a = V_2 - V_1 = 23.07 - 19.23 = 3.84V$$

$$V_B = V_3 - V_2 = 40 - 23.07 = 16.93V$$



Q.4

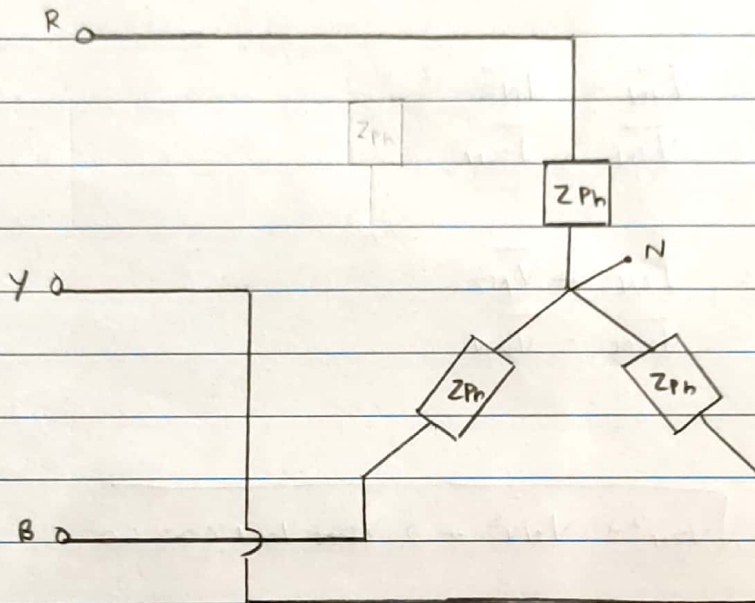

3 PHASE STAR CONNECTION

⇒ Relation between line voltage and phase voltage.

$$\text{Let } V_{RN} = V_{YN} = V_{BN} = V_{ph}$$

where V_{ph} indicates the rms value of phase voltage.

$$\bar{V}_{RN} = V_{ph} \angle 0^\circ$$

$$\bar{V}_{YN} = V_{ph} \angle -120^\circ$$

$$\bar{V}_{BN} = V_{ph} \angle -240^\circ$$

$$\text{Let } \bar{V}_{RY} = \bar{V}_{YB} = \bar{V}_{BR} = V_L$$

where V_L is rms value of line voltage.

∴ Applying KVL,

$$\bar{V}_{RY} = \bar{V}_{RN} + \bar{V}_{NY}$$

$$= \bar{V}_{RN} - \bar{V}_{YN}$$



Similarly,

$$\begin{aligned}\overline{V_{YB}} &= \overline{V_{YN}} + \overline{V_{NB}} \\ &= \overline{V_{YN}} - \overline{V_{BN}}\end{aligned}$$

$$\begin{aligned}\overline{V_{BR}} &= \overline{V_{BN}} + \overline{V_{NR}} \\ &= \overline{V_{BN}} - \overline{V_{RN}}\end{aligned}$$

Now,

$$V_{RY} = \sqrt{V_{RN}^2 + V_{NY}^2 + 2 V_{RN} V_{NY} \cos 60}$$

$$\therefore V_L = \sqrt{V_{Ph}^2 + V_{Ph}^2 + 2 V_{Ph}^2 \cos 60}$$

$$\therefore \boxed{V_L = \sqrt{3} V_{Ph}}$$

Thus, in a star connected three-phase system,

 $V_L = \sqrt{3} V_{Ph}$ and line voltages lead respective voltage by 30° .


⇒ Relation between line current and phase current.

From the diagram, it is clear that line current is equal to the phase current.

$$\therefore \boxed{I_L = I_{Ph}}$$




⇒ Phasor diagram (Lagging Power factor)

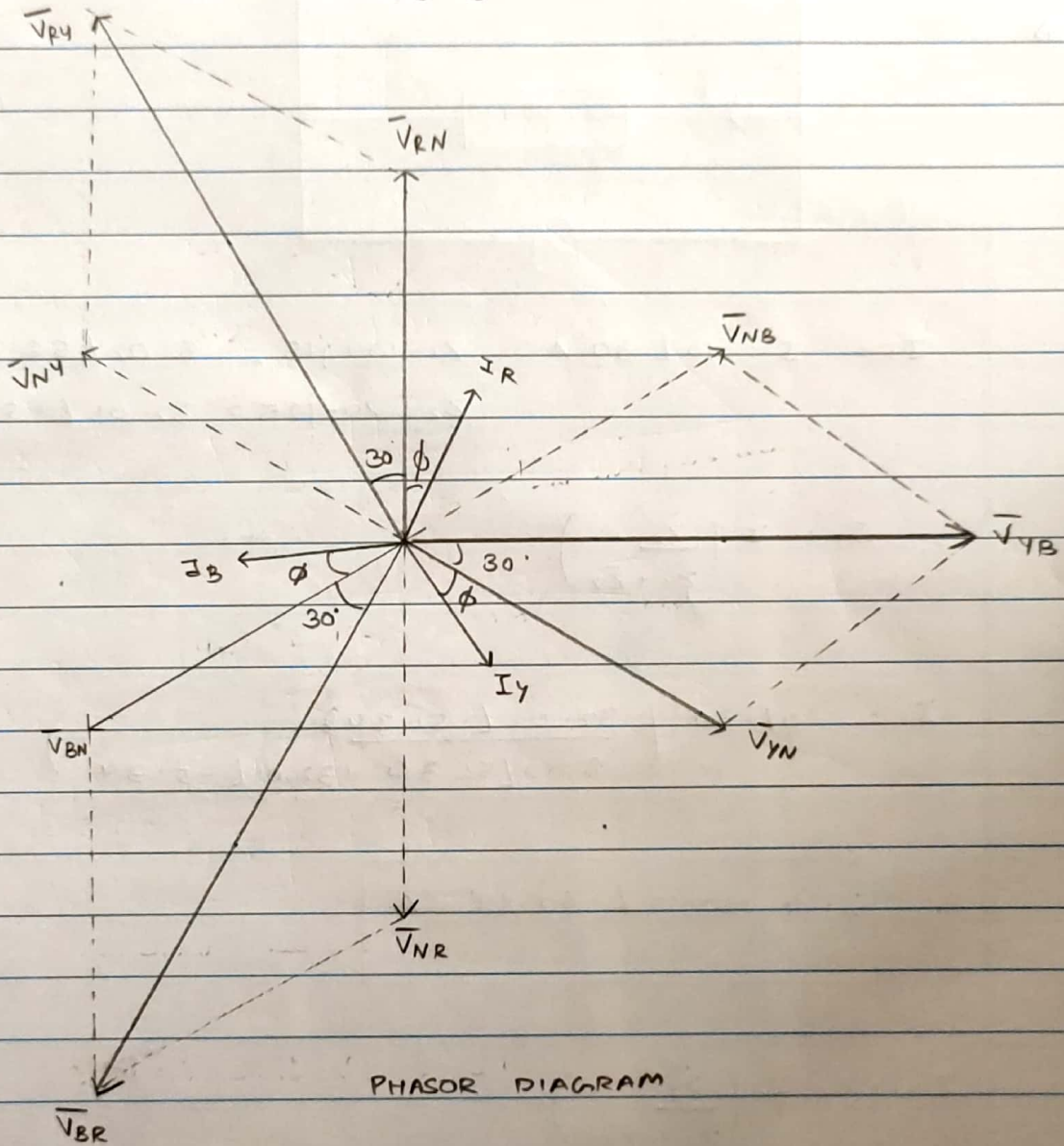



Q. 6
a)

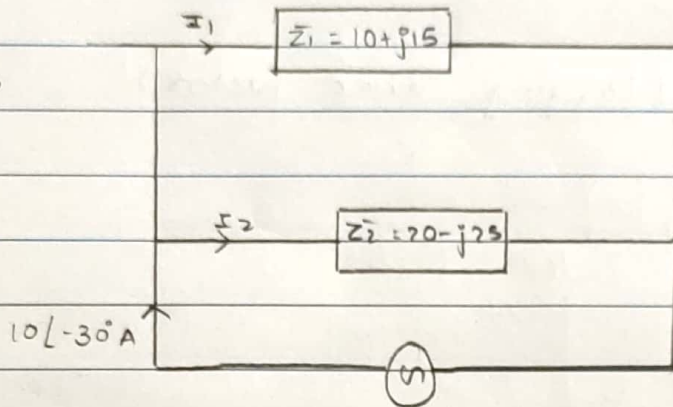

~~Given~~ $I = 10 \angle -30^\circ \text{ A}$, $Z_1 = 10 + j15 = 18.02 \angle 56.30^\circ$
 $Z_2 = 20 - j25 = 32.01 \angle -51.34^\circ$

$$\therefore I_1 = I \left(\frac{\bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} \right)$$

$$I_1 = 10 \angle -30^\circ \left(\frac{32.01 \angle -51.34^\circ}{18.02 \angle 56.30^\circ + 32.01 \angle -51.34^\circ} \right)$$

$$\therefore I_1 = 10.12 \angle -62.89^\circ \text{ A}$$

$$I_2 = I \left(\frac{\bar{Z}_1}{\bar{Z}_1 + \bar{Z}_2} \right)$$

$$I_2 = 10 \angle -30^\circ \left(\frac{18.02 \angle 56.30^\circ}{18.02 \angle 56.30^\circ + 32.01 \angle -51.34^\circ} \right)$$

$$I_2 = 5.697 \angle 44.74^\circ$$



$$Z_1 = 10 + j15$$
$$= R_1 + jX_L$$

$$R_1 = 10 \Omega$$

$$I_1 = 10.12 \text{ A}$$

Power loss will only due to resistance in Z_1 and Z_2

$$\therefore P_1 = I_1^2 R_1$$
$$= (10.12)^2 \times 10$$

$$\therefore P_1 = 1024.144 \text{ W}$$

$$I_2 = 5.699 \text{ A}, R_2 = 20$$

$$\therefore P_2 = I_2^2 R_2$$
$$= (5.699)^2 \times 20$$

$$P_2 = 649.572 \text{ W}$$




Q. 6

→ b)

Case (i)

$$I_1 = 8 \text{ A}$$
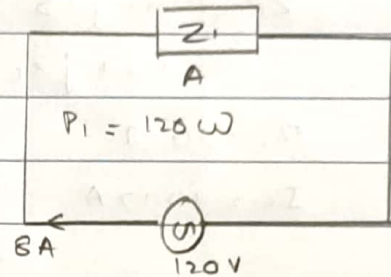
$$Z_1 = \frac{V}{I} = \frac{120}{8} = 15 \Omega$$



$$P_1 = 120 \text{ W}$$

$$\therefore I_1^2 R_1 = 120$$

$$\therefore R_1 = \frac{120}{8^2} = 1.875 \Omega$$

$$\therefore Z_1^2 = \sqrt{R^2 + X_L^2}$$

$$Z_1^2 = R^2 + X_L^2$$

$$15^2 = (1.875)^2 + X_L^2$$


$$X_L = 14.88 \Omega$$

$$\therefore Z_1 = 1.875 + j 14.88 = 15 \angle 82.81^\circ$$

Case (ii)

$$I_2 = 10 \text{ A}$$
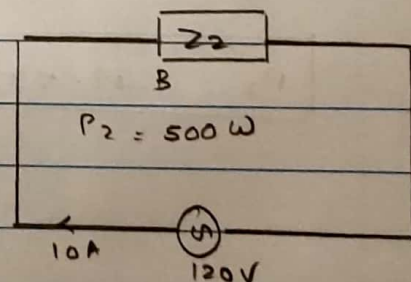
$$Z_2 = \frac{V}{I_2} = \frac{120}{10} = 12 \Omega$$



$$P_2 = 500 \text{ W}$$

$$I_2^2 R_2 = 500$$

$$10^2 R_2 = 500$$

$$\therefore R_2 = 5 \Omega$$



$$\therefore Z_2^2 = R_2^2 + X_{L2}^2$$

$$X_{L2}^2 = \sqrt{12^2 - 5^2}$$


$$X_{L2} = 10.90 \Omega$$

$$\therefore Z_2 = R_2 + jX_{L2}$$
$$= 5 + j10.90$$

$$Z_2 = 12 \angle 65.35^\circ$$

Now,

Case (iii)

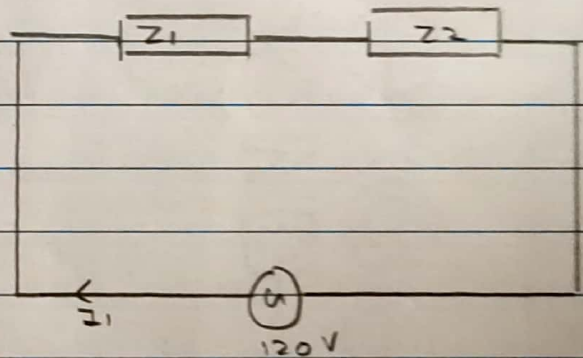

$$\bar{Z}_{eff} = \bar{Z}_1 + \bar{Z}_2$$
$$= 15 \angle 82.81^\circ + 12 \angle 65.35^\circ$$
$$= 26.69 \angle 75.05^\circ$$
$$= 6.88 + j25.788$$

$$\therefore Z_{eff} = 26.69$$

$$\therefore I = \frac{120}{Z_{eff}} = \frac{120}{26.69} = 4.496 A$$

$$\therefore \boxed{I = 4.496 A}$$



$$\begin{aligned}\text{Total Power} &= (4.496)^2 \times (6.88) \\ &= 139.072 \text{ W}\end{aligned}$$

\therefore

$$\boxed{\text{Total Power} = 139.072 \text{ W}}$$