



SAP ID - 60004200132

Name - Ayush Jain


Div - J

MAEER's MIT

BEE

### Term Test 1 Assignment.

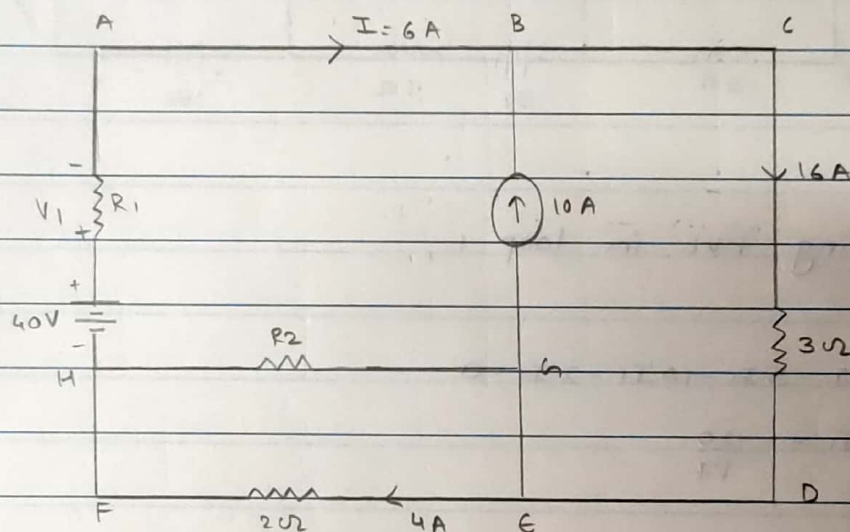1) Find the unknown voltage  $V_1$  in the circuit.



Applying KCL at B,

$$\therefore I + 10 - 16 = 0$$

$$\therefore I = 6 \text{ A}$$

NOW,

Applying KVL in ABCDEFA


$$40 - 6R_1 - 16(3) - 4(2) = 0$$

$$\therefore -6R_1 - 16 = 0$$

$$\therefore 6R_1 = -16$$

$$V_1 = -16 \text{ V} \quad \dots [V_1 = IR_1 = 6R_1]$$

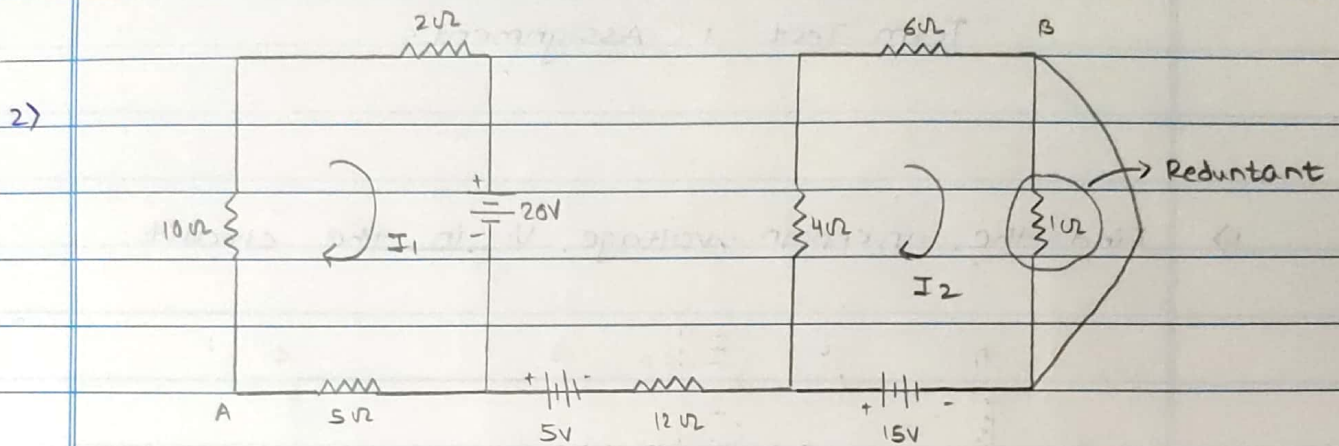$\therefore$  The unknown voltage  $V_1$  in the circuit is  $-16 \text{ V}$ .



Applying KVL in loop 1,

$$-20 - 5I_1 - 10I_1 - 2I_1 = 0$$

$$\therefore I_1 = \frac{-20}{17}$$

$$\therefore I_1 = -1.176 \text{ A} = 1.176 \text{ A} (\curvearrowright)$$

Applying KVL in loop 2,

$$15 - 4I_2 - 6I_2 = 0$$

$$\therefore I_2 = \frac{15}{10}$$

$$\therefore I_2 = 1.5 \text{ A} (\curvearrowleft)$$

Now,

Applying KVL from A to B,

$$V_A - 5(I_1) - 5 - 4I_2 - 6I_2 - V_B = 0$$

$$\therefore V_A - V_B = 5I_1 + 10I_2 + 5$$


$$\therefore V_{AB} = 5(1.176) + 10(1.5) + 5 = 25.88 \text{ V}$$

$\therefore$  The voltage  $V_{AB}$  is 25.88 V.





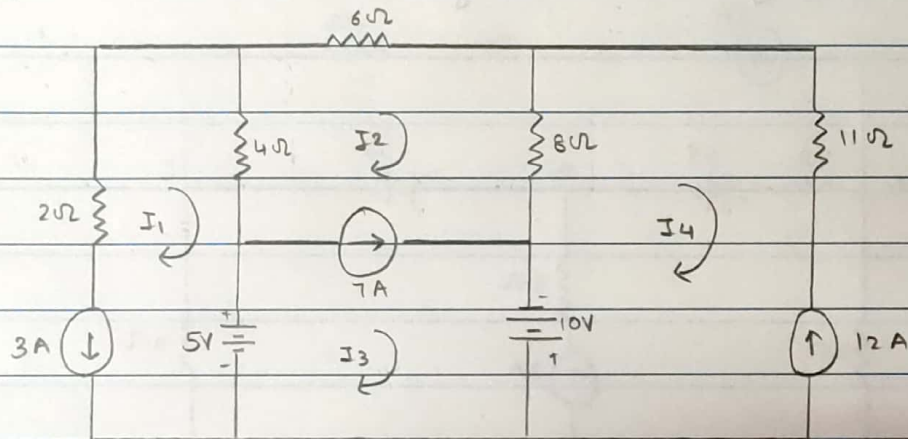3) Find current through the  $8\Omega$  resistance using mesh analysis.



∴ From given circuit,

$$I_1 = -3 \text{ A}, \quad I_4 = -12 \text{ A}$$

KVL at  
Apply a supermesh,

$$-4I_2 - 6I_2 - 8I_2 + 10 + 5 + 4I_1 + 8I_4 = 0$$

$$-18I_2 + 15 + 4(-3) + 8(-12) = 0$$

$$\therefore -18I_2 + 15 - 12 - 96 = 0$$

$$\therefore -18I_2 - 93 = 0$$

$$\therefore I_2 = \frac{-93}{18} = -5.167 \text{ A}$$

$$\therefore I_2 = 5.167 \text{ A (C)} \quad \text{---}$$


NOW,

$$I_{8\Omega} = I_4 - I_2$$

$$= 12 - 5.167 = 6.833 \text{ A}$$

∴ Current through  $8\Omega$  resistance is  $6.833 \text{ A}$ .

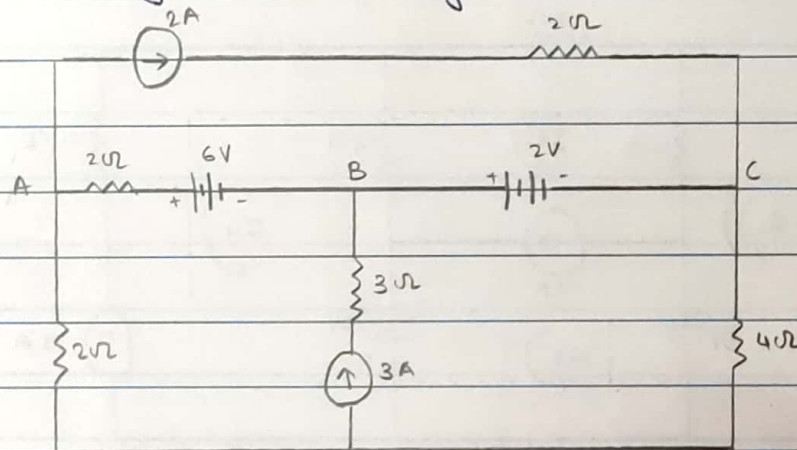- 4) Find the current through  $4\Omega$  resistor in the network shown using nodal analysis.



$$V_B - V_C = 2 \quad \text{--- (i)}$$

Applying KCL at node A,

$$\therefore \frac{V_A}{2} + \frac{V_A - 6 - V_B}{2} + 2 = 0$$

$$\therefore 2V_A - V_B = 2 \quad \text{--- (ii)}$$

Applying KCL at supernode,

$$\frac{V_B + 6 - V_A}{2} - 3 + \frac{V_C - 2}{4} = 0$$

$$\therefore -2V_A + 2V_B + V_C = 8 \quad \text{--- (iii)}$$

On solving (i), (ii) and (iii)



$$\therefore V_A = 4V, \quad V_B = 6V, \quad V_C = 4V$$

$$\therefore I_{4\Omega} = \frac{V_C}{4} = \frac{4}{4} = 1A \quad (\downarrow)$$

$\therefore$  Current through  $4\Omega$  resistor is  $1A$ .





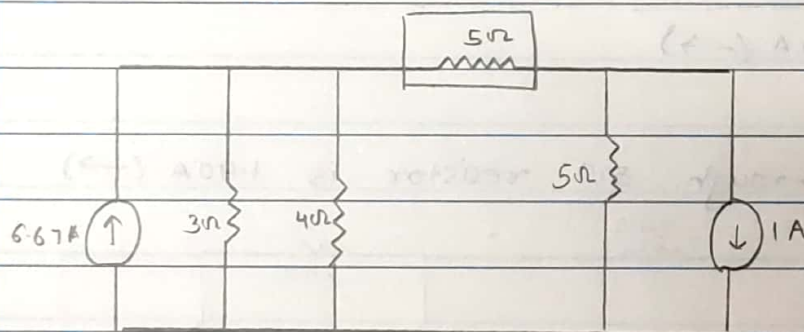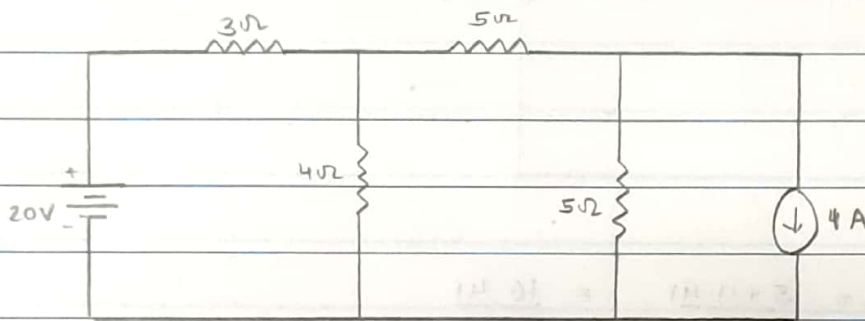
- 5) Calculate the direction and magnitude of the current through  $5\Omega$  resistor using source transformation.



Now,  $3\Omega$  is parallel to  $4\Omega$
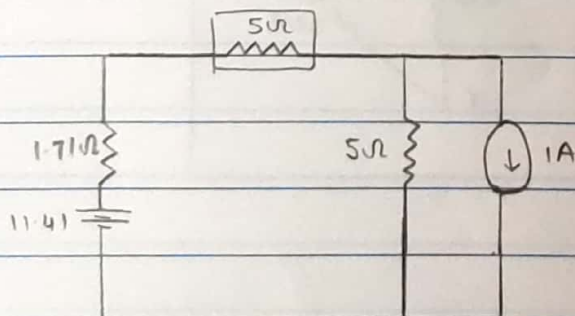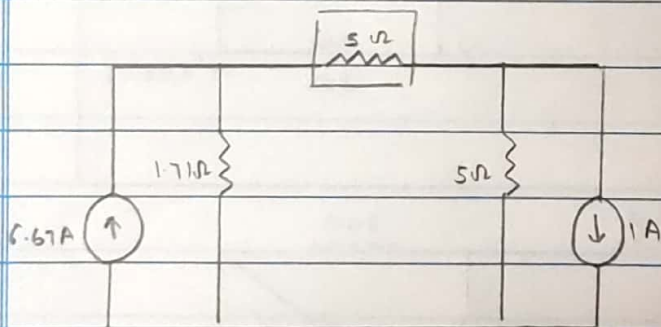
$$\therefore 3 \parallel 4 = 1.71\Omega$$





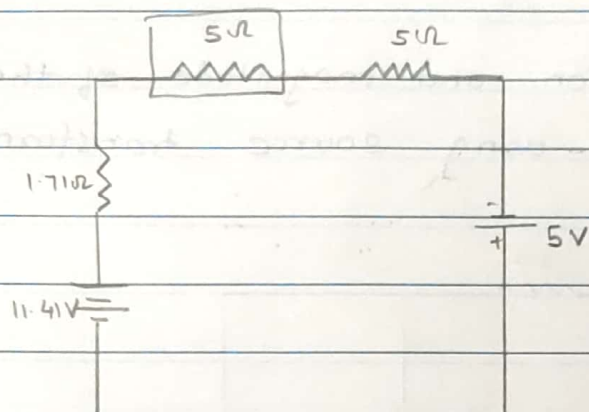

$$\therefore I_{5\Omega} = \frac{5 + 11.41}{5 + 5 + 1.71} = \frac{16.41}{11.71}$$

$$\therefore I_{5\Omega} = 1.40 \text{ A } (\rightarrow)$$

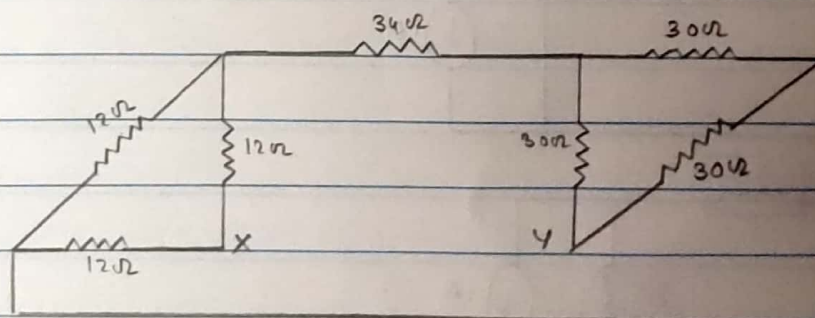
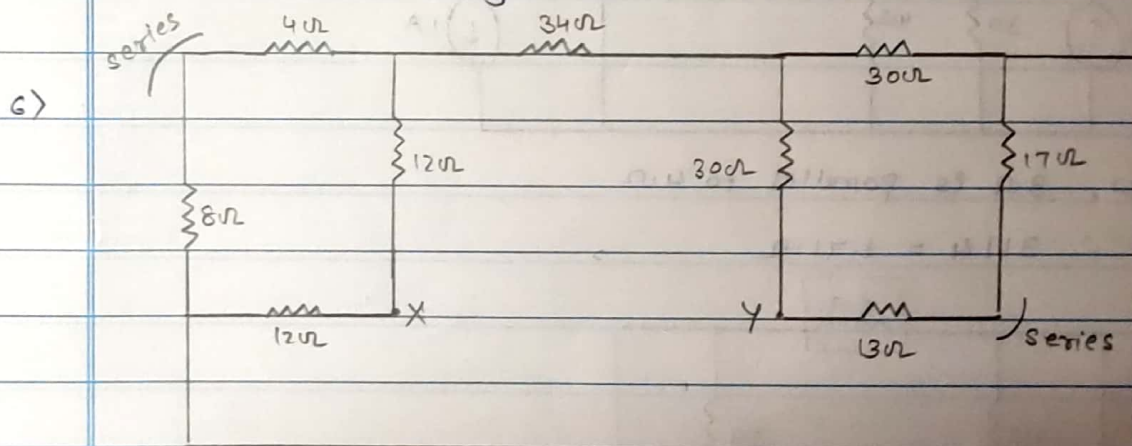
$\therefore$  Current through 5Ω resistor is 1.40 A ( $\rightarrow$ )








converting the deltas into star network,

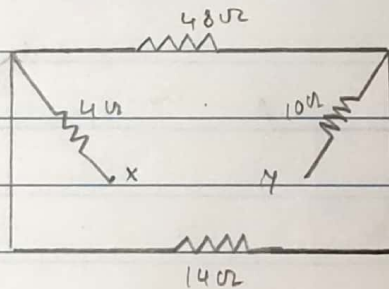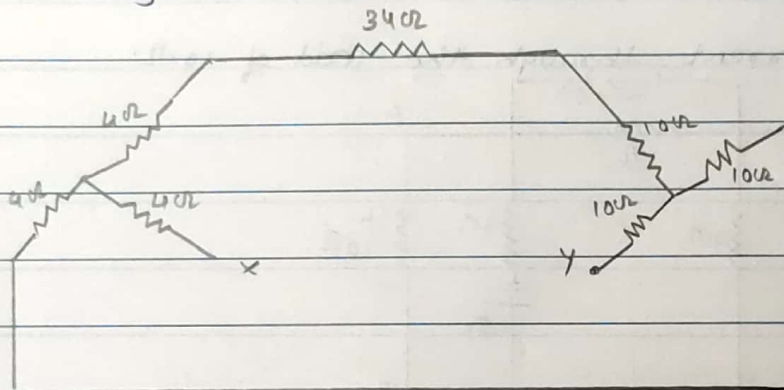

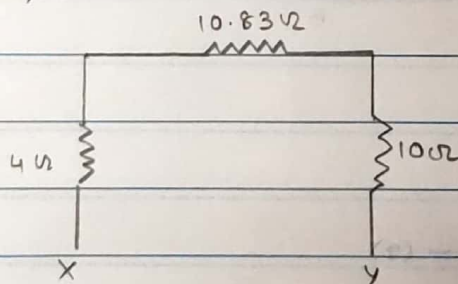Now,  $(48 \parallel 14)\Omega \therefore 48 \parallel 14 = 10.83\Omega$




$$\therefore R_{xy} = 4 + 10.83 + 10$$

$$\therefore R_{xy} = 24.83\Omega$$


$\therefore$  Equivalent network resistance between terminals X and Y is  $24.83\Omega$ .



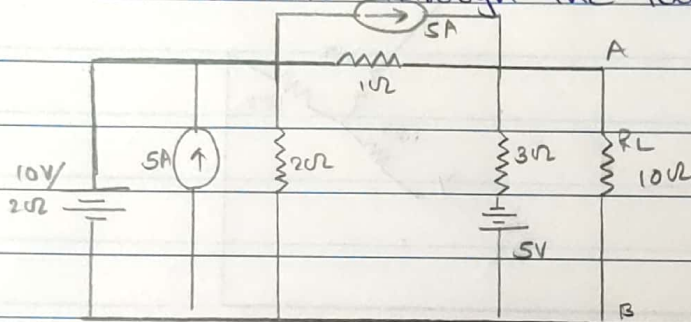- 7) Find the Thevenin's equivalent circuit across a-b and hence find the current through the load of  $10\Omega$ .



→

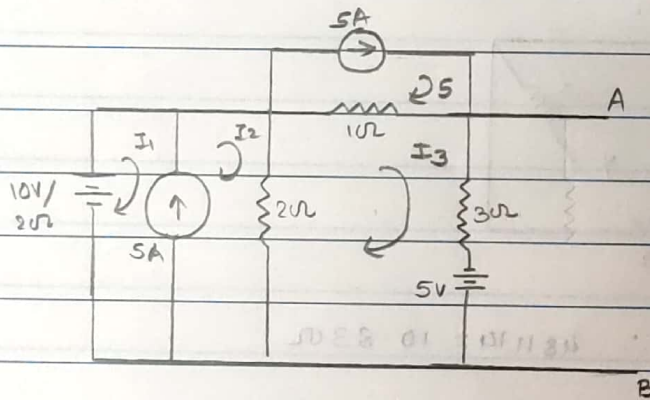

$$\therefore I_2 - I_1 = 5 \quad \text{--- (i)}$$

KVL in Supermesh,

$$10 - 2I_1 - 2I_2 + 2I_3 = 0 \quad \text{--- (2)}$$

KVL in loop 3,



$$10 - 6I_3 + 2I_2 = 0$$

$$\therefore I_2 - 3I_3 + 5 = 0 \quad \text{--- (3)}$$

On solving (i), (ii) and (iii)

$$I_1 = 2A, I_2 = 7A, I_3 = 4A.$$

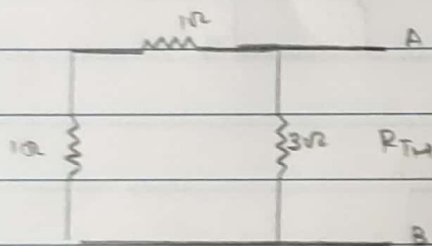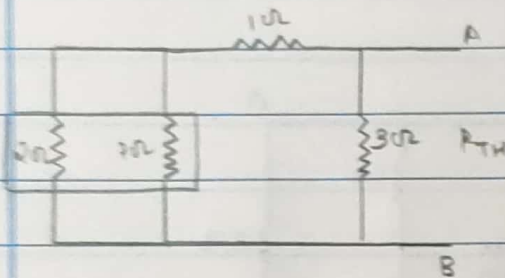

For  $R_{TH}$ ,

$$R_{TH} = (1+1) \parallel 3 = 2 \parallel 3 = 1.2 \Omega$$

$$\therefore R_{AB} = 1.2 \Omega$$


Now,

Applying KVL from A to B,

$$V_A - 3 \times 4 + 5 - V_B = 0$$

$$V_{AB} = 7V$$

$$\therefore V_{TH} = 7V$$


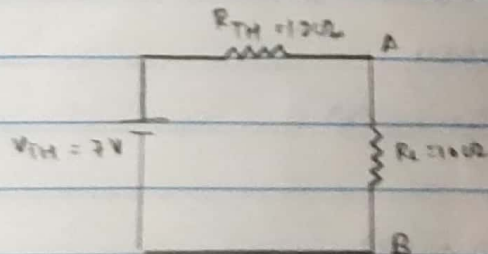
 $\therefore$  Thevenin's Equivalent Circuit,

$$\therefore I_{10\Omega} = \frac{7}{1.2+10} = \frac{7}{11.2} = 0.625 A (\downarrow)$$

 $\therefore$  Current through load of  $10 \Omega$  is  $0.625 A (\downarrow)$



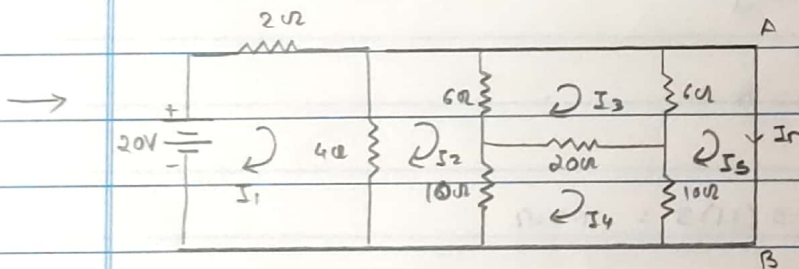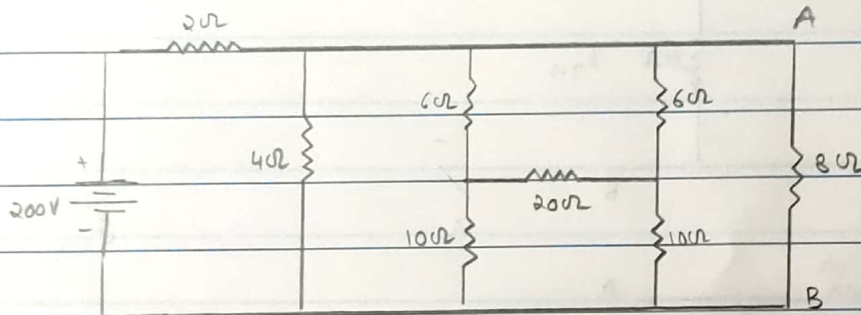- 8) Find the current through Norton's theorem through a load of  $8\Omega$ .



KVL in loop 1,

$$200 - 6I_1 + 4I_2 = 0$$

$$\therefore 3I_1 - 2I_2 = 100 \quad \text{--- (1)}$$

KVL in loop 2,

$$-20I_2 + 4I_1 + 6I_3 + 10I_4 = 0$$

$$-20I_2 + 4(2I_2 + 100) + 6I_3 + 10I_4 = 0$$

$$-60I_2 + 8I_2 + 400 + 18I_3 + 30I_4 = 0$$

$$\therefore 52I_2 = 400 + 18I_3 + 30I_4$$

$$\therefore 26I_2 = 200 + 9I_3 + 15I_4 \quad \text{--- (2)}$$

KVL in loop 3,

$$-32I_3 + 6I_2 + 20I_4 + 6I_5 = 0 \quad \text{--- (3)}$$

KVL in loop 4,

$$-40I_4 + 10I_2 + 20I_3 + 10I_5 = 0 \quad \text{--- (4)}$$



KVL in loop 5,


$$-16 I_5 + 10 I_4 + 6 I_3 = 0 \quad \text{--- (5)}$$

On solving equation (2), (3), (4) and (5),



$$I_3 = 100 \text{ A}, I_4 = 100 \text{ A}, I_5 = 100 \text{ A}$$


$$\therefore I_N = I_5 = 100 \text{ A}$$

For  $R_{TH}$ ,

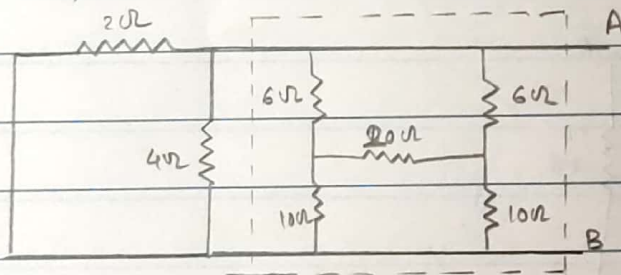

Converting the delta-into star network,

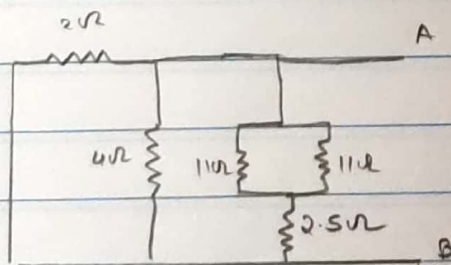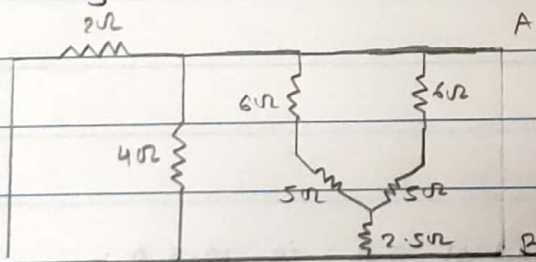

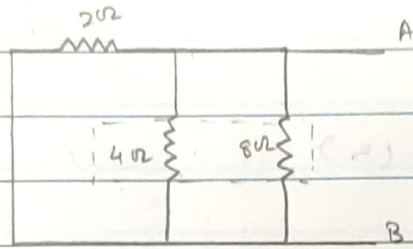


$$\therefore R_{AB} = (8 \parallel 4) + 2$$

$$\therefore R_{AB} = 1.142 \Omega$$

$$\therefore R_N = 1.142 \Omega$$

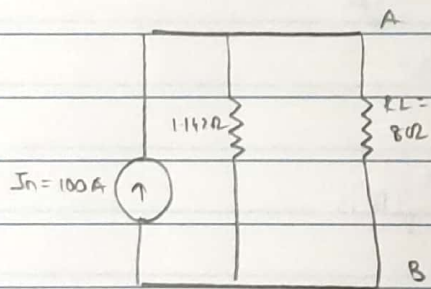$\therefore$  Norton's Equivalent circuit.



$$\therefore I_{8\Omega} = \frac{100 \times 1.142}{8 + 1.142}$$


$$I_{8\Omega} = 12.5 \text{ A}$$

$\therefore$  Current through a load of  $8\Omega$  is  $12.5 \text{ A}$ .





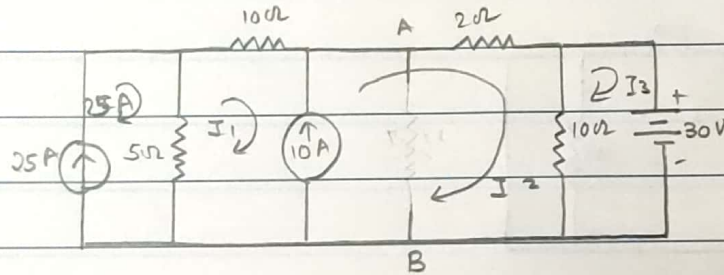9) Determine the maximum power delivered to  $R_L$ .



$$I_1 - I_2 = 10 \quad (1)$$

Applying KVL in supermesh,

$$-15I_1 - 12I_2 + 10I_3 + 5(25) = 0$$

$$\therefore 15I_1 + 12I_2 - 10I_3 = 125 \quad (2)$$

Applying KVL in loop,

$$-30 - 10I_3 + 10I_2 = 0$$

$$\therefore 10I_2 - 10I_3 = 30 \quad (3)$$

$\therefore$  On solving (1), (2) and (3)

$$I_1 = 4.41 \text{ A}, \quad I_2 = 14.41 \text{ A}, \quad I_3 = 11.41 \text{ A}$$

Now,


Applying KVL from A to B,

$$V_A - 2I_2 - 10I_3 + 10I_2 - V_B = 0$$

$$V_{AB} = 12I_2 - 10I_3$$

$$\therefore V_{AB} = 58.822 \text{ V}$$

$$\therefore V_{TH} = 58.822 \text{ V}$$

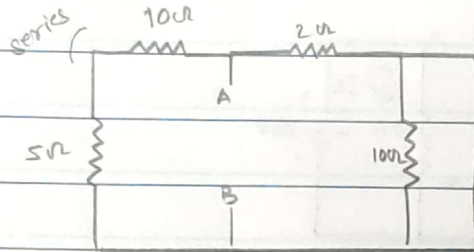For  $R_{TH}$ ,

$$\therefore R_{AB} = (10+5) \parallel 100 = (15 \parallel 100)$$

$$\therefore R_{AB} = 1.764\Omega$$


$$\therefore R_{TH} = 1.764\Omega$$

$$\therefore P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{(58.822)^2}{4(1.764)}$$

$$\therefore P_{max} = 490.366 \text{ W}$$

$\therefore$  Maximum Power delivered to load  $R_L$  is  $490.366 \text{ W}$ .


- 10) Determine the current through  $10\Omega$  resistor in the network shown Superposition theorem.

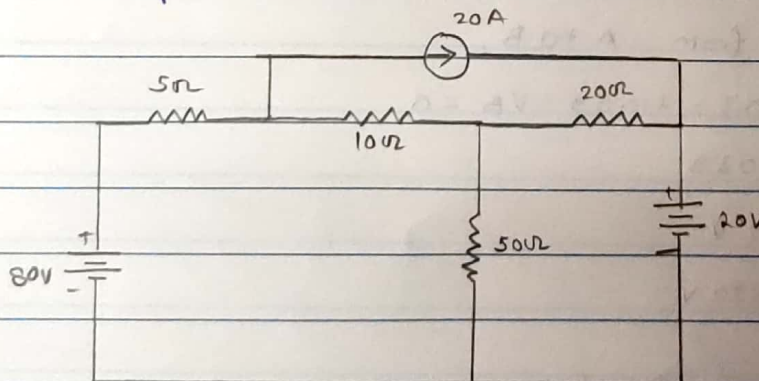





Case 1 : when only 80V source is active.

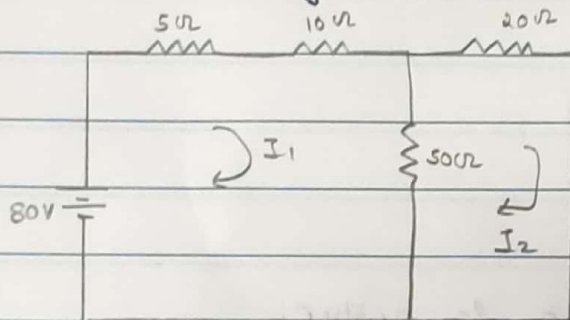

KVL in loop 1,

$$80 - 65I_1 + 50I_2 = 0$$

$$\therefore 65I_1 - 50I_2 = 80 \quad (i)$$

KVL in loop 2,


$$50I_1 - 70I_2 = 0 \quad (2)$$

On solving equations (i) and (ii),

$$I_1 = 2.73 \text{ A}, \quad I_2 = 1.95 \text{ A}$$

$$\therefore I_{10\Omega} = 2.73 \text{ A} (\rightarrow)$$

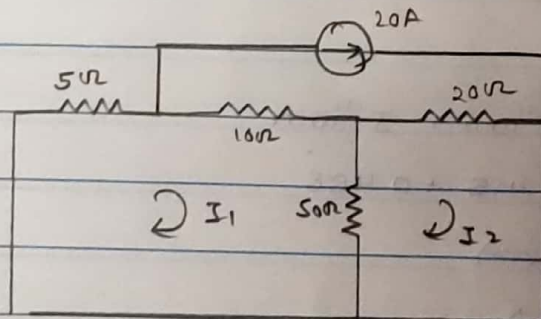Case 2 : When 20A current source is active.



KVL in loop 1,

$$65I_1 - 50I_2 = 200 \quad (i)$$

KVL in loop 2,

$$50I_1 - 70I_2 = -400 \quad (2)$$




On solving,

$$I_1 = 16.585 \text{ A}, I_2 = 17.561 \text{ A}$$

$$\therefore I''_{10\Omega} = 20 - 16.585$$

$$I''_{10\Omega} = 3.415 \text{ A} (\leftarrow)$$

Case 3: When 20V source is active.

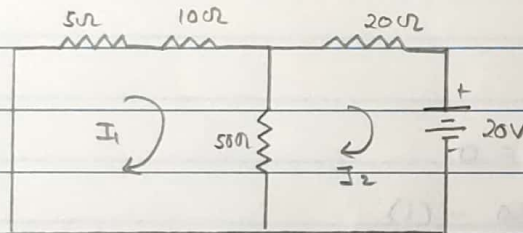

KVL in loop 1,

$$-65I_1 + 50I_2 = 0 \quad \text{--- (1)}$$

KVL in loop 2,

$$-70I_2 + 50I_1 = 20 \quad \text{--- (2)}$$

On solving,

$$I_1 = -0.488 \text{ A}, I_2 = -0.634 \text{ A}$$

$$\therefore I'''_{10\Omega} = 0.488 \text{ A} (\leftarrow)$$

$$\begin{aligned} \therefore I_{10\Omega} &= I_{10\Omega}' + I''_{10\Omega} + I'''_{10\Omega} \\ &= -2.73 + 3.415 + 0.488 \end{aligned}$$

$$I_{10\Omega} = 1.171 \text{ A} (\leftarrow)$$

$$I_{10\Omega} = 1.171 \text{ A} (\leftarrow)$$

$\therefore$  Current through 10Ω resistor is 1.171A ( $\leftarrow$ )