



Shri Vile Parle Kelavani Mandal's

DWARKADAS J. SANGHVI COLLEGE OF ENGINEERING

(Autonomous College Affiliated to the University of Mumbai)

NAAC Accredited with "A" Grade (CGPA : 3.18)



First Year (Semester I) B.Tech.

Basic Electrical and Electronics Engineering

Experiment No. : 04

Thevenins and Nortons Theorem




Name : Ayush Jain

SAP No. : 60004200132

Date of performance : 27/03/2021

Signature of teacher-in-charge : _____


**First Year (Semester I) B.Tech.**

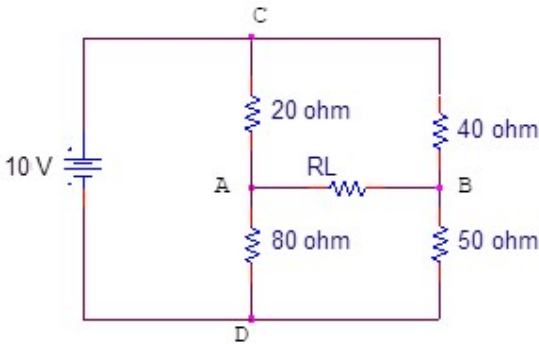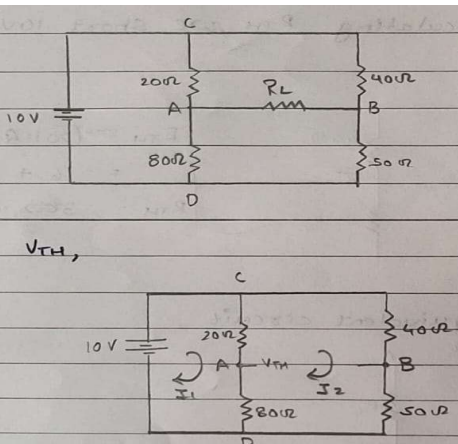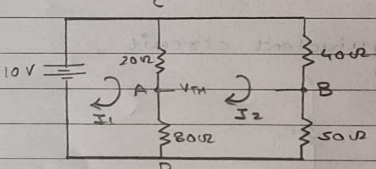Aim:	To determine resistor, voltage and current value in a circuit.
Apparatus :	Online simulation tools (Suggested Tinkercad)
Theoretical 1 Analysis:	<p>Thevenins Theorem</p>  <p>Fig. 1(a) Voltage across RL load resistor value 10ohm, 20ohm, 30ohm</p> <p>Theoretical Calculations:</p>  <p>For V_{TH},</p>  <p>KVL in loop 1, $-100 I_1 + 100 I_2 + 10 = 0$ $10 I_1 - 10 I_2 = 1 \quad \text{--- (i)}$</p> <p>KVL in loop 2, $-190 I_2 + 100 I_1 = 0$ $10 I_1 - 19 I_2 = 0 \quad \text{--- (2)}$</p> <p>On solving (i) and (ii) $I_1 = 0.211 \text{ A} \quad I_2 = 0.111 \text{ A}$</p> <p>KVL to find V_{TH}, $V_A + 20(I_1 - I_2) - 40 I_2 - V_B = 0$ $V_A - V_B = 2.44$ $\therefore V_{TH} = V_{AB} = 2.44 \text{ V}$</p>




First Year (Semester I) B.Tech.

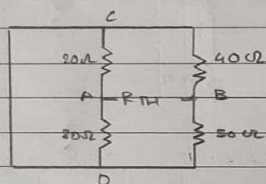Now, for calculating R_{TH} , we short 10V source.



$$\begin{aligned} \therefore R_{TH} &= (20 \parallel 30) + (40 \parallel 50) \\ &= 16 + 22.2 \\ R_{TH} &= 38.2 \Omega \end{aligned}$$

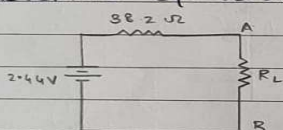\therefore Thevenin's equivalent circuit,



When $R_L = 10 \Omega$


$$\therefore V_{10\Omega} = \frac{2.44 \times 10}{48.2} = 0.507 \text{ V} = 507 \text{ mV}$$

When $R_L = 20 \Omega$,

$$V_{20\Omega} = \frac{2.44 \times 20}{58.2} = 0.838 \text{ V} = 838 \text{ mV}$$



When $R_L = 30 \Omega$,
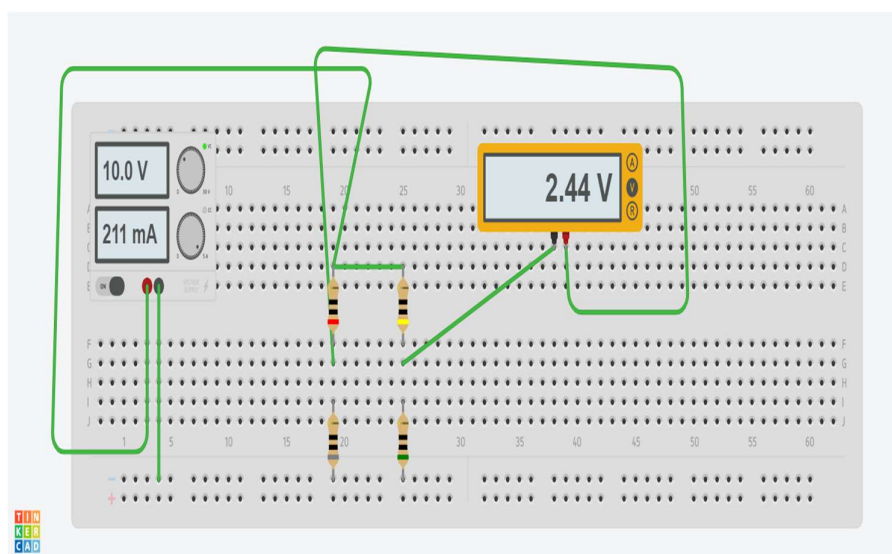
$$V_{30\Omega} = \frac{2.44 \times 30}{68.2} = 1.07 \text{ V}$$





First Year (Semester I) B.Tech.

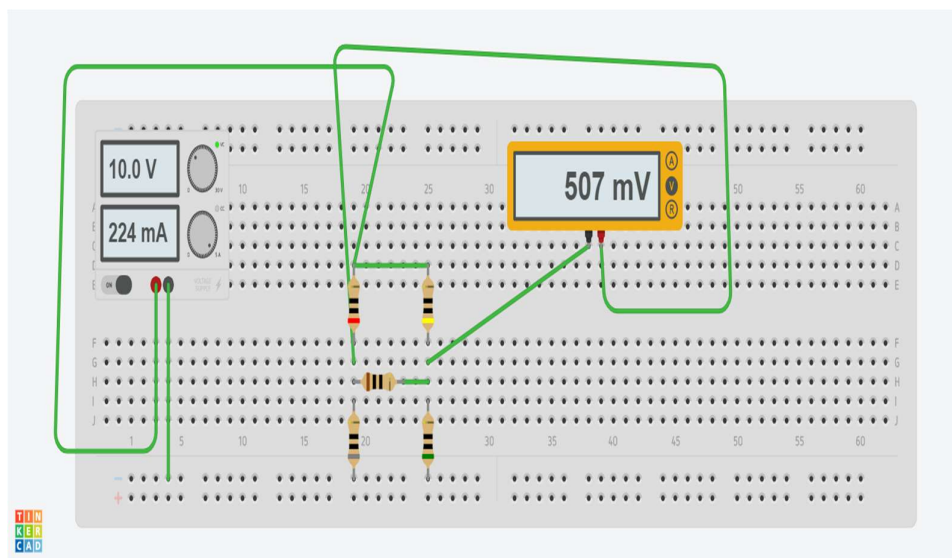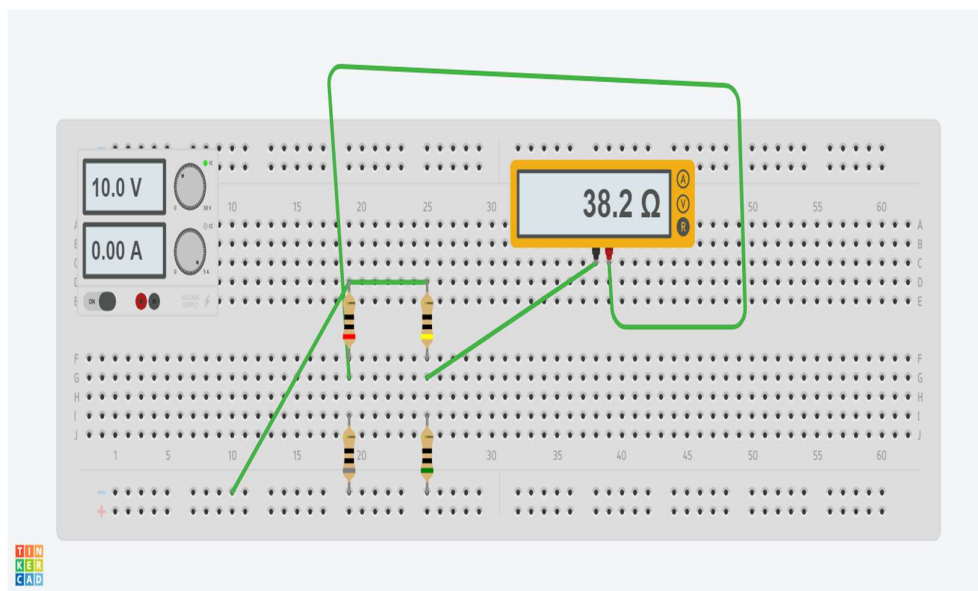



First Year (Semester I) B.Tech.

Nortons Theorem

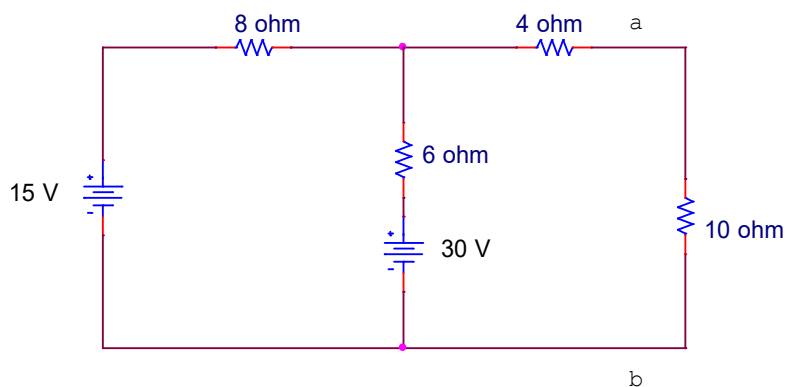


Fig. 1(b) Voltage across across a and b

Theoretical Calculations:

For I_N ,

KVL in loop 1,

$$-14I_1 + 6I_2 + 15 - 30 = 0$$
$$\therefore -14I_1 + 6I_2 = 15 \quad (1)$$

Solving (1) and (2)

$$\therefore I_1 = 0.286A$$

KVL in loop 2,


$$-10I_2 + 6I_1 + 30 = 0$$
$$\therefore 6I_1 - 10I_2 = -30 \quad (2)$$
$$I_2 = 3.17A$$

$\therefore I_N = 3.17A$



First Year (Semester I) B.Tech.


For R_N , short 15 V and 30 V sources.

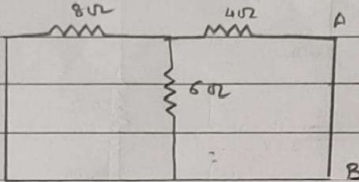

$$\therefore R_N = (8 \parallel 16) + 4 = 7.43 \Omega$$

$$\therefore R_N = 7.43 \Omega$$

\therefore Norton's equivalent circuit,

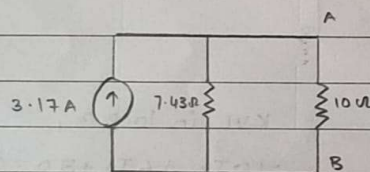


$$\therefore I_{10\Omega} = \frac{3.17 \times 7.43}{17.43}$$

$$= 1.35 \text{ A}$$



\therefore voltage across a and B = $V_{AB} = 1.35 \times 10$

$$\therefore V_{AB} = 13.5 \text{ V}$$

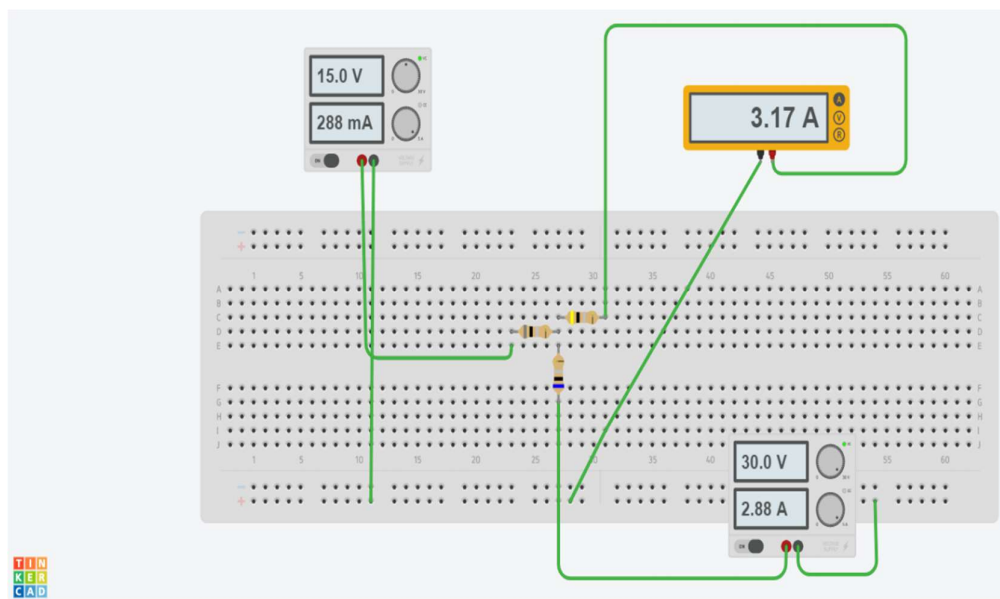



First Year (Semester I) B.Tech.

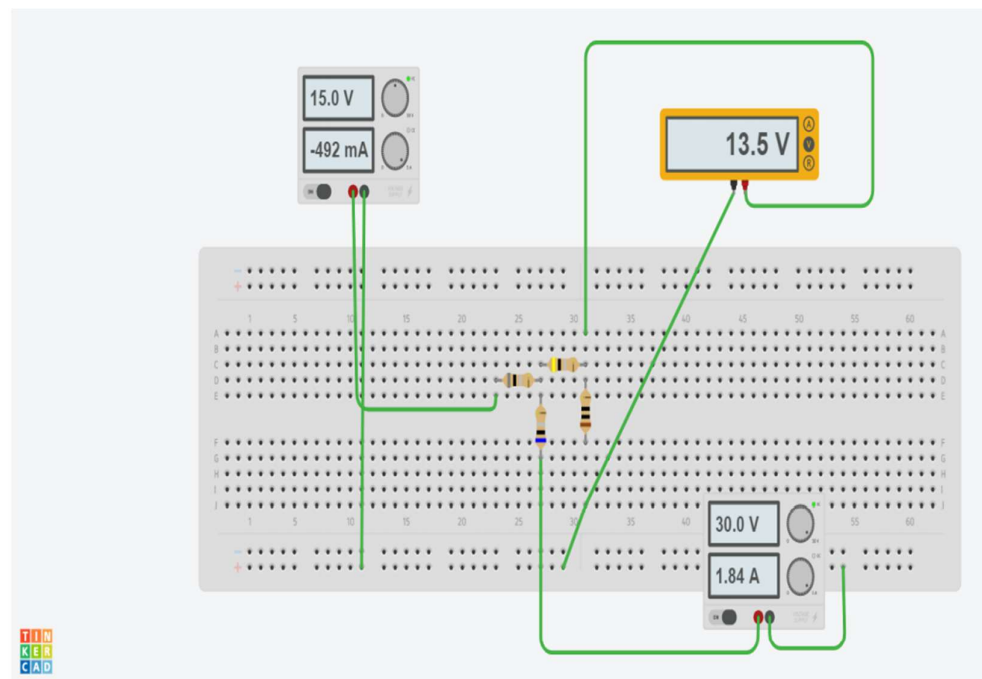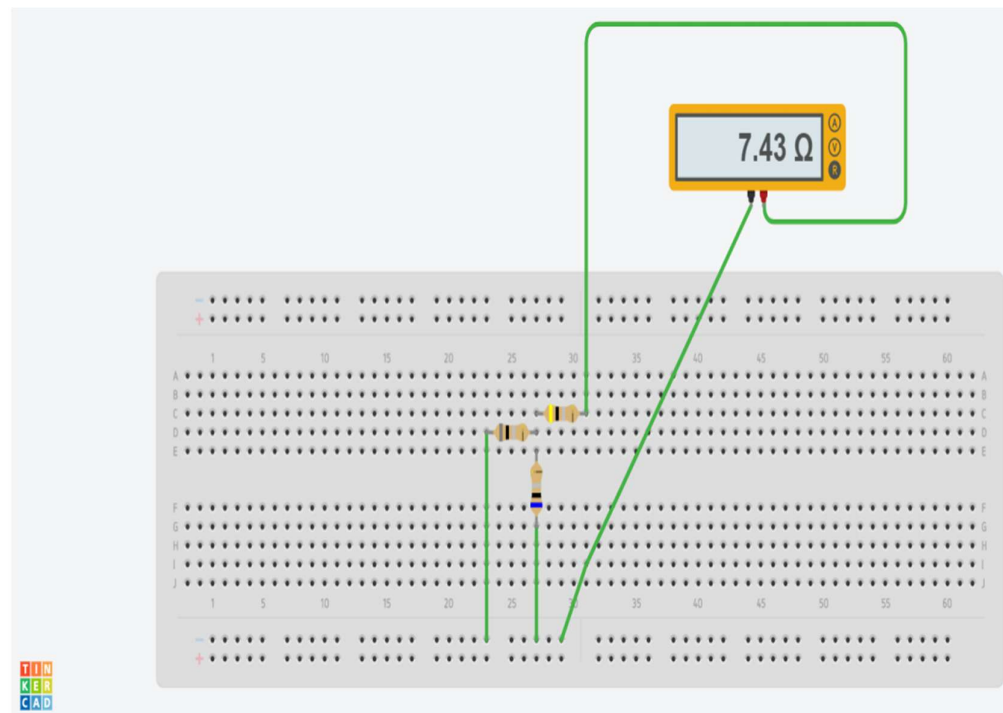

**First Year (Semester I) B.Tech.**

--	--

		Theoretical values	Practical values
Observation Table	Thevenins Voltage, V_{TH}	2.44V	2.44V
	Equivalent resistor, R_{TH}	38.2 ohm	38.2 ohm
	Voltage $V_{10\Omega}$	507 mV	507mV
	Voltage $V_{20\Omega}$	838 mV	838 mV
	Voltage $V_{30\Omega}$	1.07 mV	1.07 mV

		Theoretical values	Practical values
Observation Table	Nortons Current, I_N	3.17 A	3.17 A
	Equivalent resistor, R_N	7.43 ohm	7.43 ohm
	Voltage $V_{10\Omega}$	13.5 V	13.5 V

Conclusion:

- The Practical values has been attained using online simulation tool Tinkercad.
- Thevenins and Nortons Theorems are used to determine the values of current, resistance and voltage.
- The Theoretical and Practical values are equal to each other