

Basic Electrical and Electronics Engineering


Experiment No. : 05
AC Circuit Analysis



Name : Ayush Jain

SAP No. : 60004200132

Date of performance : 03 | 04 | 2021

Signature of teacher-in-charge : _____

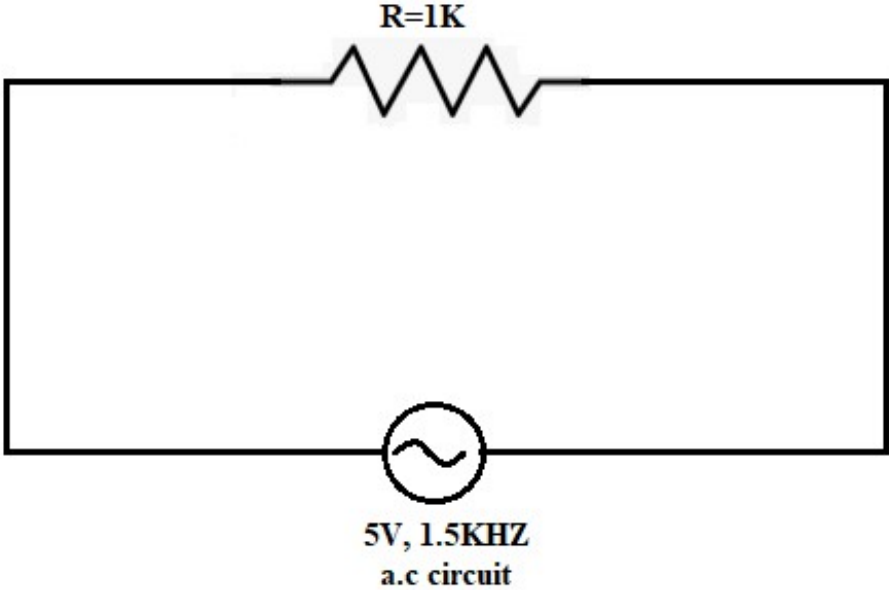Aim:	A.C through 1) Resistor 2) R-L Series circuit 3) R-C Series circuit										
Apparatus:	Online simulation tools (Suggested Tinkercad)										
Theoretical Analysis:	<div><p><i>Fig. 1(a) A.C through resistor</i></p><p><u>Theoretical Calculations:</u></p><p>$V=IZ$</p><p>Since $Z=R$</p><p>$I=V/R$</p><p>Table 1</p><table><tr><th>Sr. No.</th><th>Frequency</th><th>Current</th><th>Voltage</th><th>Resistance</th></tr><tr><td>1.</td><td>1000Hz</td><td>1mA</td><td>5V</td><td>1K ohm</td></tr></table></div>	Sr. No.	Frequency	Current	Voltage	Resistance	1.	1000Hz	1mA	5V	1K ohm
Sr. No.	Frequency	Current	Voltage	Resistance							
1.	1000Hz	1mA	5V	1K ohm							

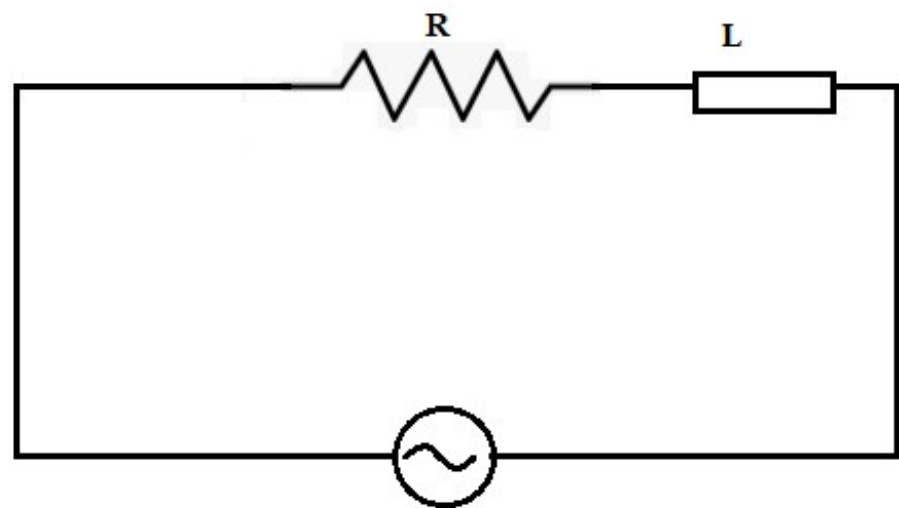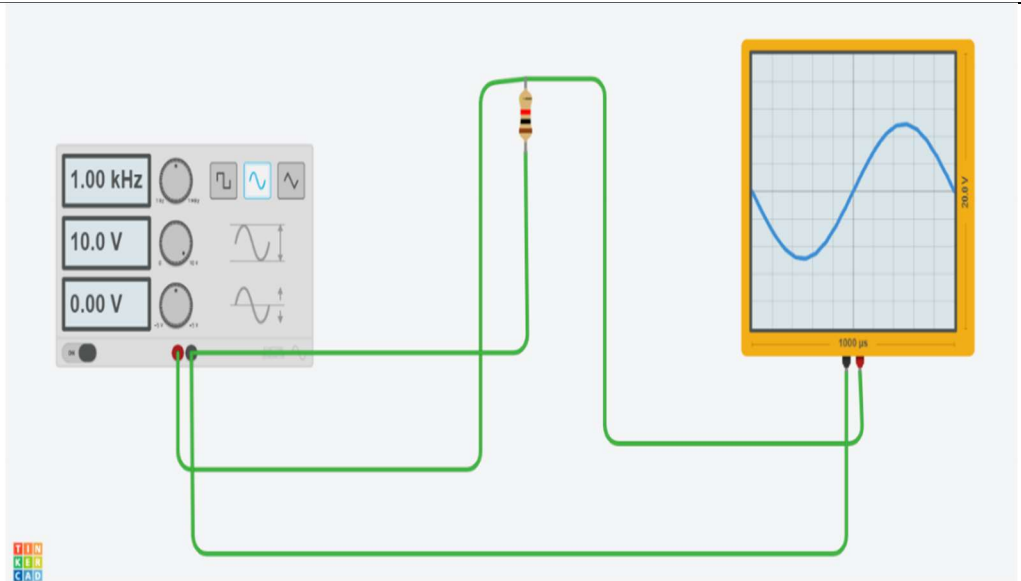

a.c circuit

Fig. 1(b) R-L Series circuit

Theoretical Calculations:

~~Fig~~
R-L series circuit. ($L = 100 \text{ mH}$, $f = 50 \text{ Hz}$, $V = 5 \text{ V}$
 $X_L = 2\pi fL = 31.42 \Omega$)

Theoretical Table

Sr. No.	R	Z	I	V _R	V _L	V _T
	(Ω)	(Ω)	(A)	(V)	(V)	(V)
1.	100 Ω	104.82	0.048	4.8	1.51	5
2.	50 Ω	59.05	0.085	4.25	2.67	5
3.	10 Ω	32.97	0.152	1.52	4.78	5

Theoretical calculations =

i) when $R = 100 \Omega$,
 $Z = \sqrt{R^2 + X_L^2} = 104.82 \Omega$
 $V_R = IR = 4.8 \text{ V}$
 $V_L = IX_L = 1.51 \text{ V}$
 $V_T = \sqrt{V_R^2 + V_L^2} = 5 \text{ V}$

ii) when $R = 50 \Omega$
 $Z = \sqrt{R^2 + X_L^2} = 59.05 \Omega$
 $V_R = IR = 4.25 \text{ V}$
 $V_L = IX_L = 2.67 \text{ V}$
 $V_T = \sqrt{V_R^2 + V_L^2} = 5 \text{ V}$

iii) when $R = 10 \Omega$
 $Z = \sqrt{R^2 + X_L^2} = 32.97 \Omega$
 $V_R = IR = 1.52 \text{ V}$
 $V_L = IX_L = 4.78 \text{ V}$
 $V_T = \sqrt{V_R^2 + V_L^2} = 5 \text{ V}$

Practical Calculations Table:

Sr. No.	Resistance	Current	V _R	V _L	V _T
1.	100 ohm	47 mA	4.7 V	1.5 V	4.93 V
2.	50 ohm	82 mA	4.1 V	2.5 V	4.80 V
3.	10 ohm	150 mA	1.4 V	4.4 V	4.63 V

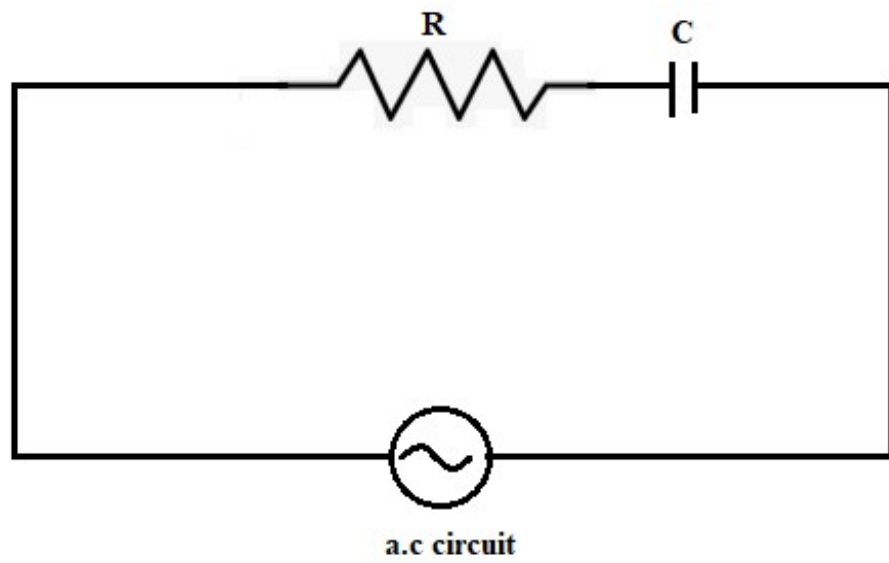
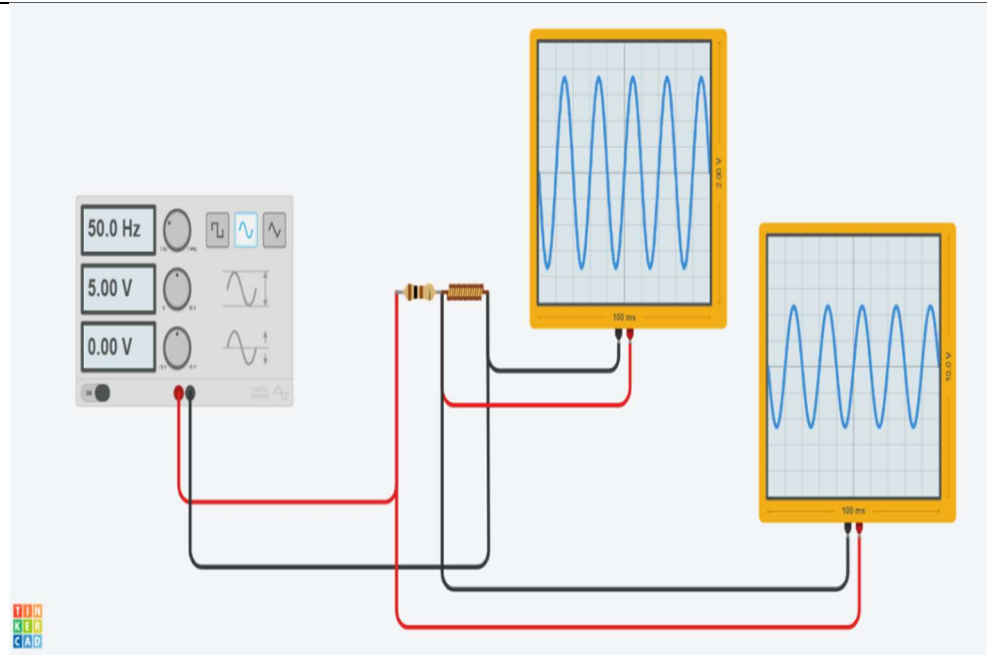


Fig. 1(c) R-C Series circuit

R-C series circuit:

$$[C = 0.1 \mu F, f = 50 \text{ Hz}, V = 5 \text{ V}]$$

$$X_C = \frac{1}{2\pi fC} = 3183 \Omega$$

Table

Sr. No.	R	Z (Ω)	I (mA)	V _R (V)	V _C (V)	V _T (V)
1.	100 K Ω	104943	0.0476	4.76	1.52	5
2.	50 K Ω	59272	0.0844	4.22	2.69	5
3.	10 K Ω	33365	0.1499	1.50	4.77	5

Theoretical calculations:

1) When R = 100 K Ω

$$Z = \sqrt{R^2 + X_C^2} = 104943 \Omega$$

$$V_R = IR = 4.76 \text{ V}$$

$$V_C = IX_C = 1.52 \text{ V}$$

$$V_T = \sqrt{V_R^2 + V_C^2} = 5 \text{ V}$$

2) When R = 50 K Ω

$$Z = \sqrt{R^2 + X_C^2} = 59272 \Omega$$

$$V_R = IR = 4.22 \text{ V}$$

$$V_C = IX_C = 2.69 \text{ V}$$

$$V_T = \sqrt{V_R^2 + V_C^2} = 5 \text{ V}$$

3) When R = 10 K Ω

$$Z = \sqrt{R^2 + X_C^2} = 33365 \Omega$$


$$V_R = IR = 1.50 \text{ V}$$

$$V_C = IX_C = 4.77 \text{ V}$$

$$V_T = \sqrt{V_R^2 + V_C^2} = 5 \text{ V}$$

Practical Calculations Table:

Sr. No.	Resistance	Current	V _R	V _C	V _T
1.	100 K ohm	0.045 mA	4.5 V	1.44 V	4.72 V
2.	50 K ohm	0.084 mA	4.2 V	2.7 V	4.99 V
3.	10 K ohm	0.146 mA	1.46 V	4.6 V	4.826 V

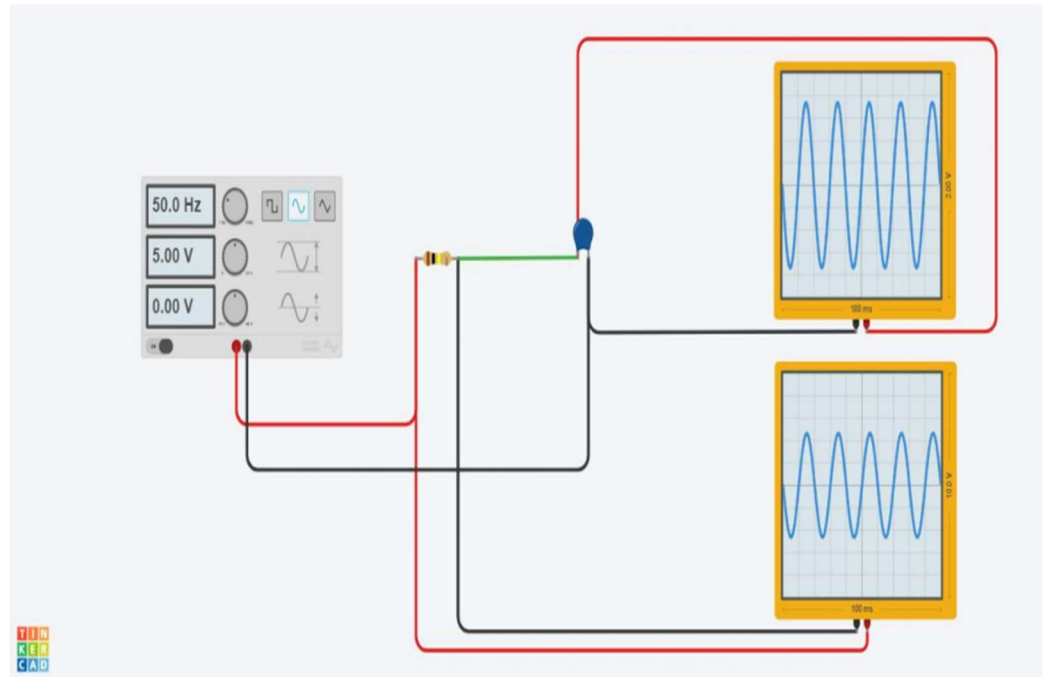

Conclusion:

- **We applied properties and formulae of pure R, series R-L and series R-C circuit for theoretical calculations.**
- **The practical values have been attained using an online simulation tool, Tinkercad.**
- **The theoretical and measured values are almost equal to each other.**